

## Return loss

power of the signal returned / reflected by discontinuity in transmission line is known by return loss.

$$R_L (\text{dB}) = 10 \log_{10} \frac{P_i}{P_r}$$

$$F = \frac{V_r}{V_i} = \frac{\text{Amp. reflected wave}}{\text{Amp. Incident wave}}$$

$$\Gamma = \frac{Z_L - Z_s}{Z_L + Z_s}$$

$$R_L \text{ in dB} = -20 \log |F|$$

(60+31)  
Line were terminated  $Z_L = 37 \Omega$   $Z_0 = 37 \Omega$  no matter

How many section are there

### Inductance loading of Telephone cables

\* In distortionless lines with distributed parameters what long lines suffered by frequency and Delay Distortion.

to achieve the distortionless condition to increase the  $\frac{L}{c}$  by lumped inductor in the line. This type of inductance is called loading the line.

\* For submarine cable the the loading is obtained by winding the cable with high permeability Permalloy.

### Physical significance of equation infinite line

Sending end current of a line of length has

$$R = \sqrt{\frac{L}{C}}$$

$$I = I_R \cosh \sqrt{Z_0} s + \frac{E_R}{Z_0} \sinh \sqrt{Z_0} s$$

$$I_s = I_R \left( \cosh \sqrt{Z_0} l + \frac{E_R}{Z_0} \sinh \sqrt{Z_0} l \right)$$

If line is terminated  $Z_R = Z_0$

$$I_s = I_R (\cosh \sqrt{Z_0} l + \sinh \sqrt{Z_0} l)$$

$$\frac{I_s}{I_R} = e^{\sqrt{Z_0} l} = e^{rl}$$


$V_{\text{RF}}$  on dissipation umline or adist from the end

$$E = \frac{ER(z_R + z_0)}{2z_R} (e^{j\beta s} + k e^{-js})$$

$$\gamma = \alpha + j\beta$$

$$\alpha R = 0, \alpha z_0 = 0$$
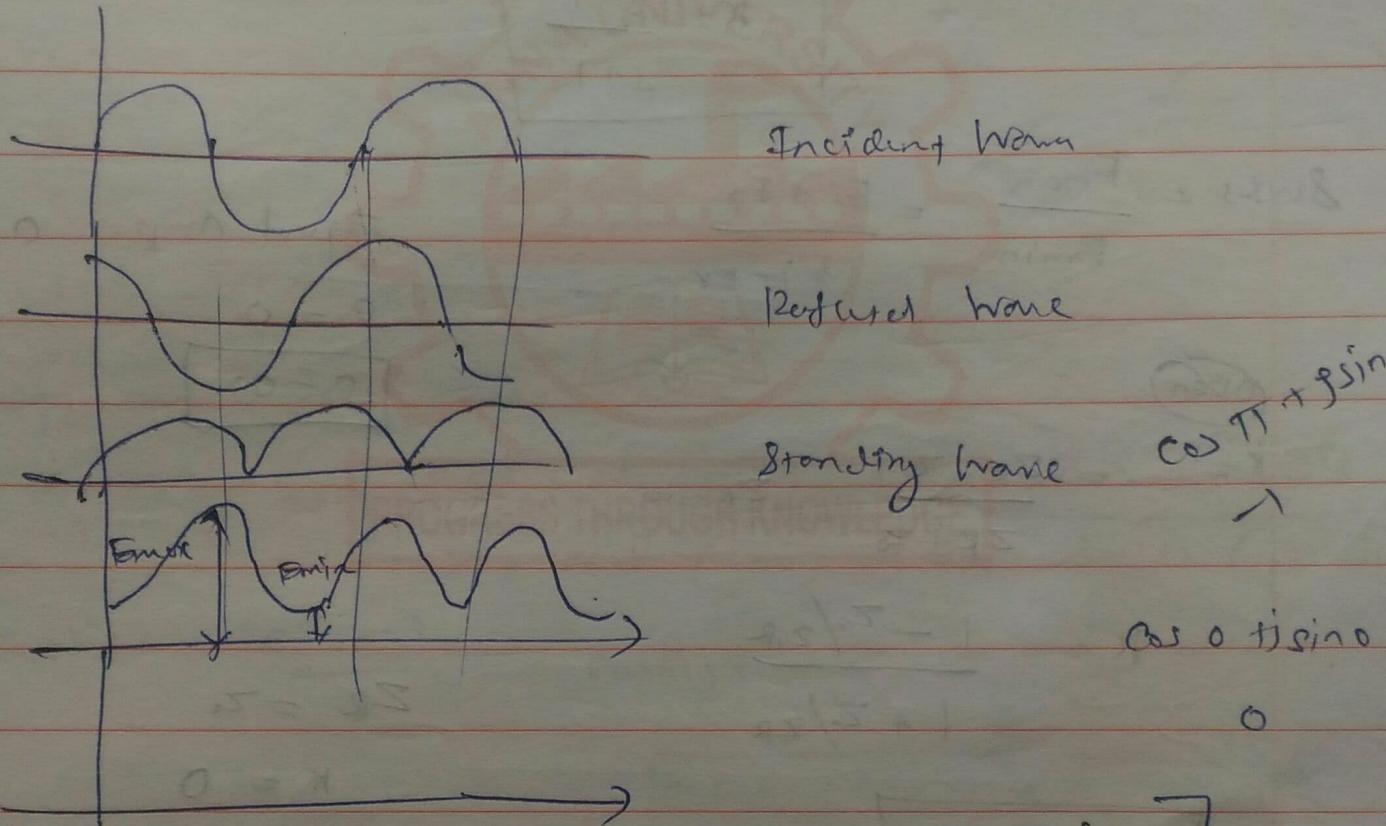
$$E = \frac{ER(z_R + z_0)}{2z_R} [e^{j\beta s} + k e^{-js}]$$



$$E_{\text{max}} = \frac{ER(z_R + z_0)}{2z_R} [e^{j\beta s} + |k| e^{-js}]$$

Max amplitude

$$E_{\text{max}} = \frac{ER(z_R + z_0)}{2z_R} (1 + |k|)$$

min. over Both out of phase

$$E_{\text{min}} = \frac{ER(z_R + z_0)}{2z_R} (1 - |k|)$$

$$VSWR = \frac{E_{max}}{E_{min}} = \frac{1+k}{1-k}$$

$$\delta = \frac{1+k}{1-k}$$

$$\delta(1-k) = 1+k$$

$$\delta - \delta k = 1+k$$

$$\delta - 1 = k + \delta k$$

$$k = \frac{\delta - 1}{\delta + 1}$$

$$R_s = \frac{E_{max}}{E_{min}} = \frac{E_I + E_R}{E_I - E_R}$$

Equal Amps = 0

$$\delta = 0$$

$$\boxed{\delta = \infty}$$

Open

$$k_2 = \frac{Z_R - Z_0}{Z_R + Z_0} \quad Z_R = \infty$$

$$k_2 = \frac{1 - Z_0/Z_R}{1 + Z_0/Z_R}$$

$$Z_R = Z_0$$

$$k = 0$$

$$\boxed{k = 1}$$

$$Z_R = 0$$

$$\delta = 1$$

$$\boxed{\delta_{SWR} = 0}$$

$$\boxed{\delta = 1}$$

Short  $Z_R = 0$

$$k_2 = \frac{-Z_0}{Z_0}$$

$$\boxed{k = -1}$$


$$\tau = 0 \rightarrow 1$$

$$VSWR \rightarrow 1 \rightarrow \infty$$

ix'

V<sub>WR</sub>

0	0
0.1	1.22
0.2	1.5
0.3	1.85
0.4	2.3
0.5	3
0.6	4
0.7	5.6
0.8	9
0.9	19
1.0	oo

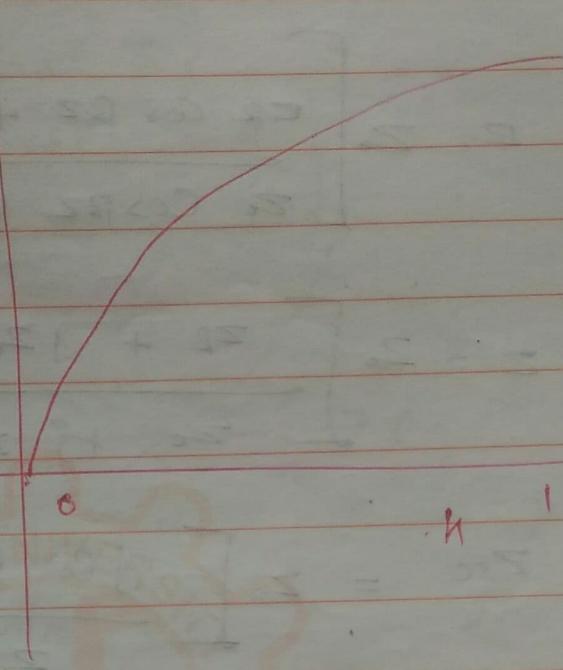

open and short circuited line

$$Z_L = Z_0 \left[ \frac{Z_R \cosh(j\beta z) + Z_0 \sinh(j\beta z)}{Z_0 \cosh(j\beta z) + Z_R \sinh(j\beta z)} \right]$$

$$\cosh jx = \frac{e^{jx} + e^{-jx}}{2}$$

$$\cosh jx = \frac{e^{jx} + e^{-jx}}{2}$$

$$\cosh jx = \frac{2 \cos x}{2} = \cos x$$

$$\sinh jx = \frac{e^{jx} - e^{-jx}}{2}$$

$$= \frac{\cos x + j \sin x - \cos x + j \sin x}{2}$$

$$\sinh jx = j \sin x$$

Q7.

$$Z_2 = Z_0 \left[ \frac{Z_R \cos \beta z + j Z_0 \sin \beta z}{Z_0 \cos \beta z + j Z_R \sin \beta z} \right]$$

$$z = Z_0 \left[ \frac{Z_R + j Z_0 \tan \beta z}{Z_0 + j Z_R \tan \beta z} \right]$$

$$Z_R = Z_0$$

$$\Leftrightarrow Z_{SC} = Z_0 \left[ \frac{j Z_0 \tan \beta z}{Z_0} \right]$$

$$Z_R = 0$$

$$Z_{SC} = Z_0 \left[ \frac{1 + j \frac{Z_0}{Z_R} \tan \beta z}{\frac{Z_0}{Z_R} + j \tan \beta z} \right]$$

$$Z_{SC} = j Z_0 \tan \beta z$$

Q8.

$$= \frac{1}{j \tan \beta z}$$

$$Z_0 = -j Z_0 \cot \beta z$$

Impedance of dissipation line


$$Z(l) = Z_0 \left[ \frac{Z_R + j Z_0 \tan \beta l}{Z_0 + j Z_C \tan \beta l} \right]$$

$$Z_{SC}(l) = j Z_0 \tan(\beta l)$$

$$Z = j \omega$$

$$Z_{sc}(\ell) \Rightarrow Z_0 \tan \beta \ell = x$$

$$\tan \beta \ell = \frac{x}{Z_0}$$

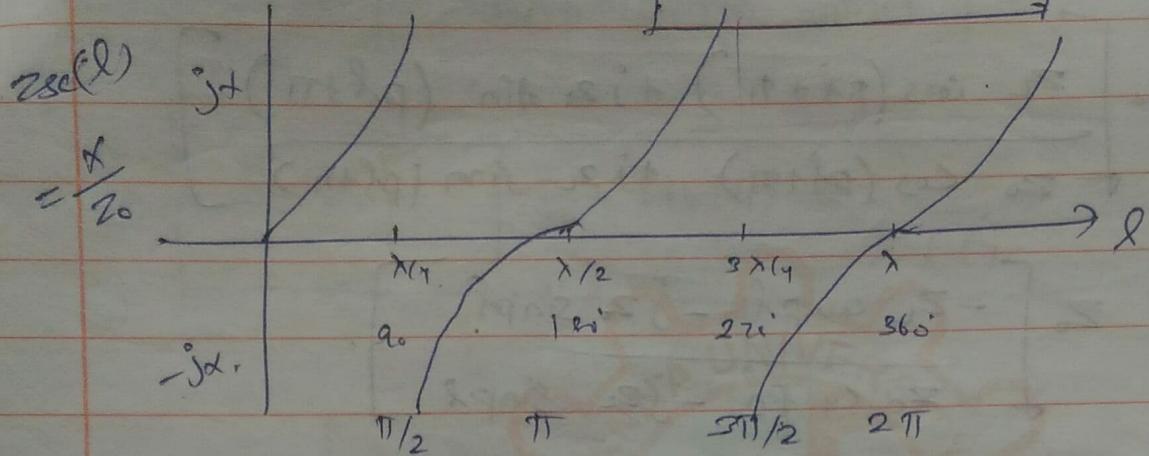

Short cut

$$\lambda = \frac{2\pi}{\beta}$$

$$\beta = \frac{2\pi}{\lambda} \times \ell$$

=

$\lambda_4$  line  $\lambda$

$\lambda_4$  line

$$0 < \ell_s < \lambda_4$$

$$\frac{L}{c}$$

$\lambda_4 < \ell_s < \lambda/2$

Q 10.

$\ell$	$\beta \ell$	$\tan \beta \ell$	$Z_{sc} \ell$
0	0	0	0
$\lambda_4$	$\pi/2$	$\infty$	$\infty$
$\lambda/2$	$\pi$	0	0

$$z(\ell + \lambda_{12}) = z_0 \begin{bmatrix} z_L \cos \beta(\ell + \lambda_{12}) + j z_L \sin (\ell + \lambda_{12}) \\ z_L \cos \beta(\ell + \lambda_{12}) + j z_L \sin \beta(\ell + \lambda_{12}) \end{bmatrix}$$

$$= z_0 \begin{bmatrix} z_L \cos (\beta\ell + \pi) + j z_L \sin (\beta\ell + \pi) \\ z_L \cos (\beta\ell + \pi) + j z_L \sin (\beta\ell + \pi) \end{bmatrix}$$

$$x_{12} = z_0 \begin{bmatrix} -z_L \cos \beta\ell - j z_L \sin \beta\ell \\ -z_L \cos \beta\ell - j z_L \sin \beta\ell \end{bmatrix}$$

$$\boxed{z(\ell + \lambda_{12}) = z(\ell)}$$

Line characteristic repeat eg.  $\lambda_2$  distance in the line.

Normalized Impedance inversely proportional to distance

$$\beta(\ell + \lambda_{12}) = \beta\ell + \frac{2\pi}{\lambda} \times \lambda_{12} = \beta\ell + \pi/2$$

$$\cos \beta\ell = \cos (\beta\ell + \pi/2) = -\sin \beta\ell$$


$$\sin (\beta\ell + \pi/2) = \cos \beta\ell$$

$$\bar{z}(\ell + \lambda_{12}) = \frac{\bar{z}_L \cos (\beta\ell + \pi/2) + j \bar{z}_L \sin (\beta\ell + \pi/2)}{\cos (\beta\ell + \pi/2) + j \bar{z}_L \sin (\beta\ell + \pi/2)}$$
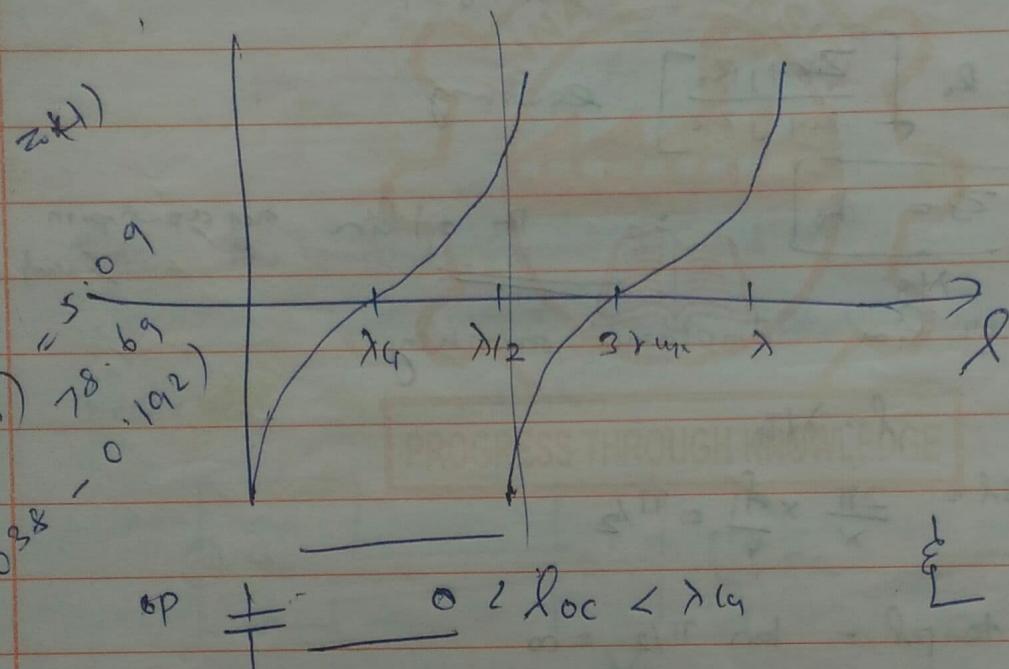
## PART - B


$$= z_0 \left[ \frac{-z_L \sin \beta l + j \omega \beta l}{-\sin \beta l + j z_L \omega \beta l} \right]$$

$$= z_0 \left[ \frac{ }{ } \right] = \frac{(l + \lambda_0)}{\lambda(l)}$$



$$\text{if } \lambda_0 < \lambda_{\text{loc}} < \lambda_0 \quad \left( \lambda_0 < \lambda < \lambda_0 \right)_2$$

poles resonant

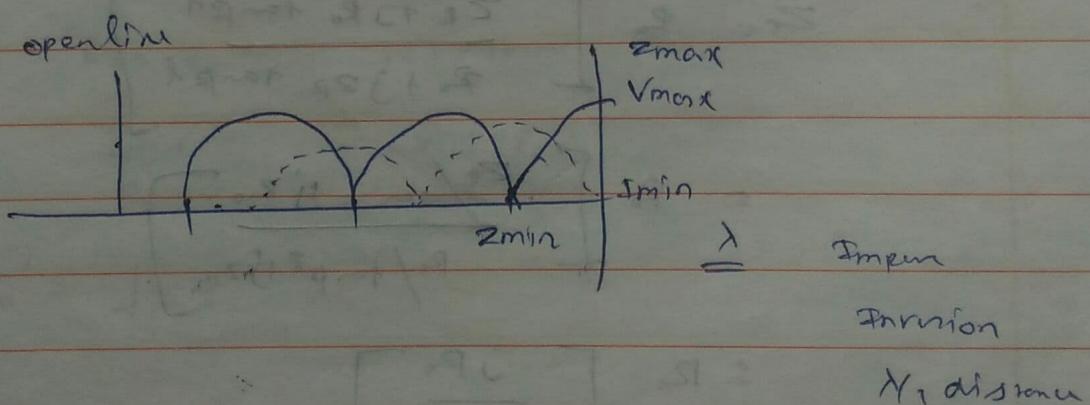

$\lambda_1$  distance

Right wave line

$$Z_B = Z_0 R \left[ \frac{Z_R + j R_0 \tan \beta l}{R_0 + j Z_R \tan \beta l} \right]$$

$$l = \lambda/8$$

$$\beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{8} = \pi/4$$

$$\tan \pi/4 = 1$$

$$Z_S = R_0 \left[ \frac{Z_R + j R_0}{R_0 + j Z_R} \right] \text{ equaling}$$

$$\boxed{Z_S = R_0}$$

$Z_S = R_0$  off line not dependent on

load

Quarter line Impedance matching

$$l = \lambda/4$$

$$\beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{4} = \pi/2$$

$$\tan \beta l = \tan \pi/2 = \infty$$

$$Z_S = R_0 \left[ \frac{Z_R + j R_0 \tan \beta l}{R_0 + j Z_R \tan \beta l} \right]$$

$$= R_0 \left[ \frac{\frac{Z_R}{\tan \beta l} + j R_0}{R_0 / \tan \beta l + j Z_R} \right]$$

$$= R_0 \left[ \frac{j R_0}{j Z_R} \right]$$

$$Z_S = \frac{R_0^2}{Z_R}$$

$$P_P^2 = \sqrt{Z_S Z_R}$$

Low Impedance  $\rightarrow$  High Impedance

Half wave line

$$l = \lambda/2$$

$$\tan \pi = 2\pi f R \times \lambda/2 \approx \pi$$

$$\tan \pi \approx$$

$$Z_S = R_0 \left( \frac{Z_R + jR_0 \tan \pi}{R_0 + jZ_R \tan \pi} \right)$$

$$= R_0 \frac{Z_R}{R_0}$$

$$\boxed{Z_S = Z_R}$$

Half wave line can be


one to one

$Z_{S1}/Z_L$  not matched. Square formed

transformer

↳ Causes power loss, preferential

breakdown, noise, radiation,

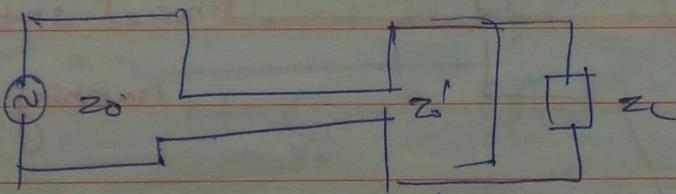

$\lambda/4$  can be transformer

$$R_L = Z_0 \quad 1:1 \text{ turn}$$

$$R_L > Z_0$$

Step up

$$R_L < Z_0$$

Step down

$$Z_0' = \sqrt{Z_0 Z_L}$$

Determine the physical length and  $Z_0$  for  $\lambda/4$  transformer that is used to match a source ( $Z_0 = 50 \Omega$ ) to  $150 \Omega$  resistive load, the frequency of operation is  $150 \text{ MHz}$  and the Velocity factor  $V_f = 1$


$$\lambda = \frac{C}{f} = \frac{3 \times 10^8 \text{ m/s}}{150 \times 10^9} = 2 \text{ m}$$

$$\lambda_{\text{eq}} = \frac{\lambda}{4} = 0.5 \text{ m.}$$

$Z_0$  of  $(0.5 \text{ m})$  transformer

$$Z_0' = \sqrt{Z_0 Z_L} = \sqrt{50 \times 150} = 86.6 \Omega$$


Stub matching  $\star$

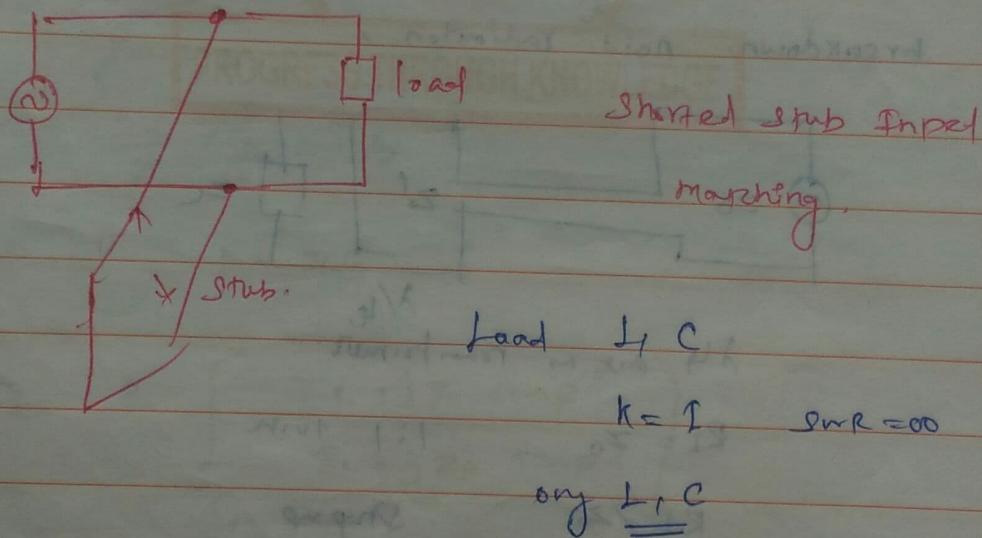

Reactive component of load is cancelled by the stub whose reactance.

Stub matching

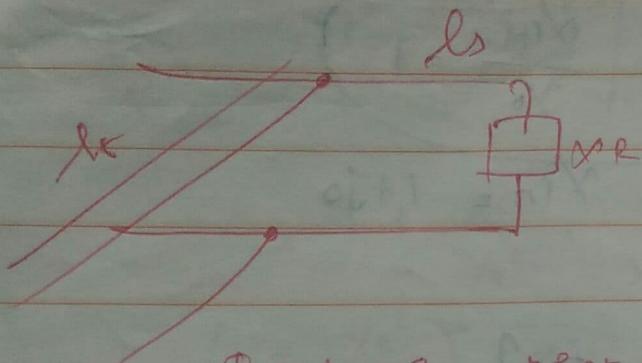Stub match by open Ckt spur  
or short Ckt stub.



shorten man  
 $\lambda/4$  fr,  $\lambda/4$  med  
as a stub.

Impedance point of tx line

$$Z_{in} = Z_0 \frac{Z_L + Z_0 \tan \beta l}{Z_0 + Z_L \tan \beta l}$$

$$Y_{in} = Y_0 \frac{Y_R + Y_0 \tan \beta l}{Y_0 + Y_R \tan \beta l}$$

$\alpha = 0$  High Q application

position, low

$$\frac{Y_{in}}{Y_0} = \frac{Y_R/Y_0 + \tanh \beta l}{1 + Y_R/Y_0 \tanh \beta l}$$

$$\tanh j\alpha = j \tanh \alpha$$

$$\left[ Y_{in} = \frac{Y_{in}}{Y_0} \right] = \text{Normalised Input Impedance}$$

$$Y_R = \frac{Y_R}{Y_0} = \text{Normalised Load admittance}$$

$$Y_{in} = \frac{Y_R + j \tan \beta l}{1 + j Y_R \tan \beta l} \times \frac{(1 - j Y_R \tan \beta l)}{1 - j Y_R \tan \beta l}$$

$$Y_{in} = \frac{Y_R - j Y_R \tan \beta l + j \tan \beta l + Y_R^2 \tan^2 \beta l}{1 + Y_R^2 \tan^2 \beta l}$$

For No reflection +/

$$X_{in} = Y_0$$

$$Y_{in} = \frac{X_{in}}{Y_0} = 1$$

$$X_{in} = 1 + j0$$

$$Y_0 (1 + \tan^2 \beta ls)$$

$$\frac{1}{1 + X_R^2 \tan^2 \beta ls} = 1$$

~~$$Y_R (1 + \tan^2 \beta ls)$$~~

$$= 1 + Y_R^2 \tan^2 \beta ls$$

$$\tan^2 \beta ls (Y_R - Y_R^2) = 1 - Y_R$$

stubs located  
at  $ls$

$$Y_R \tan^2 \beta ls (1 - Y_R) = (1 - Y_R)$$

$$Y_R \tan^2 \beta ls = 1$$

$$\tan \beta ls = \frac{1}{\sqrt{X_R}} = \sqrt{\frac{Y_0}{Y_R}}$$

$$\beta ls = \tan^{-1} \sqrt{\frac{Y_0}{Y_R}}$$

$$\frac{2\pi}{\lambda} ls = \tan^{-1} \sqrt{\frac{Z_R}{Z_0}}$$

$$ls = \frac{\lambda}{2\pi} \tan^{-1} \sqrt{\frac{Z_R}{Z_0}}$$

The susceptance at the location of stub will be

$$\frac{bs}{Y_0} = \frac{(1 - Y_R^2) \tan \beta ls}{1 + Y_R^2 \tan^2 \beta ls}$$

$$\tan \beta_{BS} = \sqrt{\frac{y_0}{x_R}}$$

$$\frac{bs}{y_0} = \left( 1 - \frac{x_R^2}{x_0^2} \right) \sqrt{\frac{y_0}{x_R}} \\ 1 + \frac{x_R^2}{y_0^2}, \frac{y_0}{x_R}$$

$$= \frac{\left( 1 - \frac{x_R^2}{x_0^2} \right) \sqrt{\frac{y_0}{x_R}}}{1 + \frac{x_R}{x_0}} \cdot \frac{\frac{1}{y_0^2} (y_0 - y_R)}{\frac{1}{y_0}}$$

$$\frac{bs}{y_0} = \frac{1}{y_0} (y_0 - y_R) \sqrt{\frac{y_0}{x_R}}$$

$$bs = (y_0 - y_R) \sqrt{\frac{y_0}{x_R}} \left( \frac{1}{z_0} - \frac{1}{z_R} \right) \left( \sqrt{z_0 z_R} \right)$$

$$\cot \beta_{BL} = y_0 - y_R \sqrt{\frac{y_0}{x_R}} \frac{z_R - z_0}{z_0 z_R} \sqrt{z_0 z_R}$$

$$\cot \beta_{LR} = (y_0 - y_R) \sqrt{\frac{1}{y_0 y_R}} \frac{z_R - z_0}{\sqrt{z_0 z_R}}$$

$$\phi_{BL} = \tan^{-1} \sqrt{\frac{z_R z_0}{z_R - z_0}}$$

$$\boxed{\phi_L = \gamma_{2\pi} \tan^{-1} \frac{\sqrt{z_R z_0}}{z_R - z_0}}$$

Smith chart

$$K = \frac{Z_r - Z_0}{Z_r + Z_0}$$

$$\frac{Z_r/Z_0 - 1}{Z_r/Z_0 + 1}$$

$$K = \frac{Z_r - 1}{Z_r + 1}$$

$$K Z_r + K = Z_r - 1$$

$$1 + K = Z_r (1 - K)$$

$$Z_r = \frac{1 + K}{1 - K}$$

$Z_1, K$  are complex No's.

$$R + jX = \frac{1 + K_r + jK_x}{(1 - K_r) - jK_x}$$

$$= \frac{(1 + K_r) + jK_x}{(1 - K_r)^2 + K_x^2} \times (1 - K_r) + jK_x$$

$$= (1 + K_r)(1 - K_r) + (1 + K_r)jK_x + jK_x(1 - K_r) - K_x^2$$

~~$$1 - K_r^2 + jK_x + jK_x K_x + jK_x - jK_x K_x - K_x^2$$~~

$$jX = \frac{1 - K_r^2 + 2jK_x - K_x^2}{(1 - K_r)^2 + K_x^2}$$

$$R_z = \frac{1 - K_r^2 - K_x^2}{(1 - K_r)^2 + K_x^2}$$

$$X = \frac{2K_x}{(1 - K_r)^2 + K_x^2}$$

The Comt R-circle

$$R \{ 1 + Kr^2 - 2Kr + Kx^2 \} = 1 + Kr^2 - Kx^2$$

$$R + RKr^2 - 2RKr + RKx^2 = 1 - Kr^2 - Kx^2$$

$$Kr^2 (1+R) + Kx^2 (1+R) - 2RKr = 1 - R$$

$$Kr^2 + Kx^2 - \frac{2R}{1+R} Kr = \frac{1-R}{1+R}$$

Add  $\frac{R^2}{(1+R)^2}$  both sides,

$$Kr^2 + Kx^2 - \frac{2R}{1+R} Kr + \frac{R^2}{(1+R)^2} = \frac{(1-R)}{(1+R)} + \frac{R^2}{(1+R)^2}$$

$$Kx^2 + \left( Kr - \frac{R}{1+R} \right)^2 = \frac{(1-R)(1+R) + R^2}{(1+R)^2}$$

$$Kx^2 + \left( Kr - \frac{R}{1+R} \right)^2 = \frac{1 - R^2 + R^2}{(1+R)^2}$$

$$Kx^2 + \left( Kr - \frac{R}{1+R} \right)^2 = \left( \frac{1}{1+R} \right)^2$$

Constant R circles.


Radius  $\left( \frac{R}{1+R} \right)$

centre  $\left[ \frac{R}{1+R}, 10 \right]$

Centre  $(0, 10)$

$Kr, Kx$

$Kr, Kx = 0$

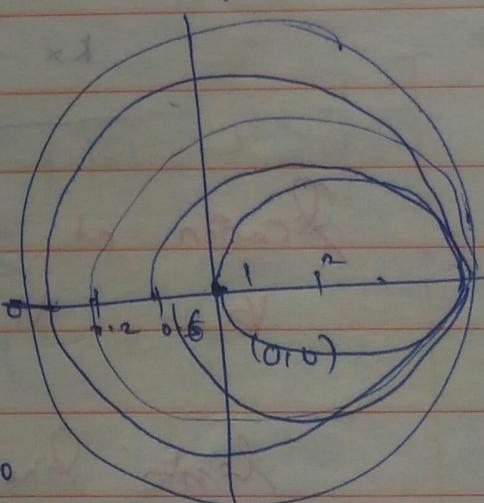

$B^2 L - S^2 + B^2 L \quad R = r$

## Constant Resistance Curve

$$(1 - k_r)^2 + k_x^2 = \frac{2k_x}{x}$$

$$(1 - k_r)^2 + k_x^2 = \frac{2k_x}{x} = 0$$

$$(1 - k_r)^2 + k_x^2 - \frac{2k_x}{x} + \left(\frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2$$

$$(1 - k_r)^2 + (k_x - 1/x)^2 = (1/x)^2$$

$$(k_r - 1) + (k_x - 1/x)^2 = (1/x)^2$$

$$(1, 1/x)$$

$x$  position

above H2 axis

$x - ny$


below H2 axis.

$$k_x, k_r = 0$$

$$x = 0$$

$k_x \quad k_r$  Vary

$x$  Vary

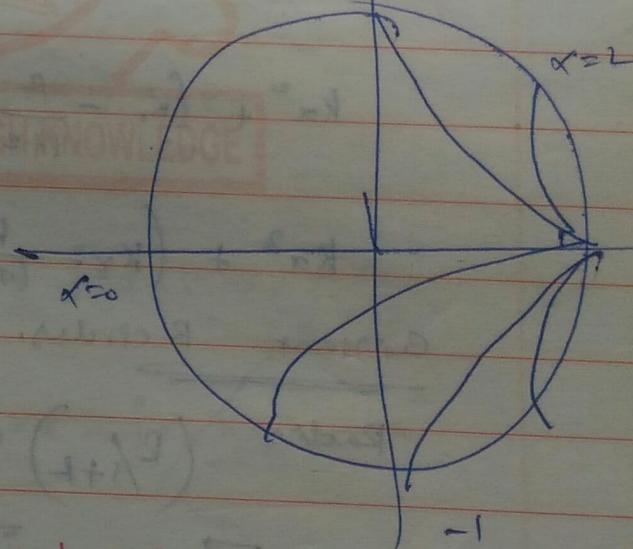

Location of voltage max and minima

$$V_x \quad V_r + V_x$$

Inphase  $V_{max}$

$V_{min}$

lumped line  $\alpha \gg \beta$

$$V_x = b e^{j\beta y} + a e^{-j\beta y}$$