


CONTROL SYSTEMS

①

Assignment - I - Solutions


- I) Write the differential equations governing the mechanical system shown in the fig. Draw the Force-voltage and Force-current electrical analogue circuits and verify by writing mesh and node equations.

(i)

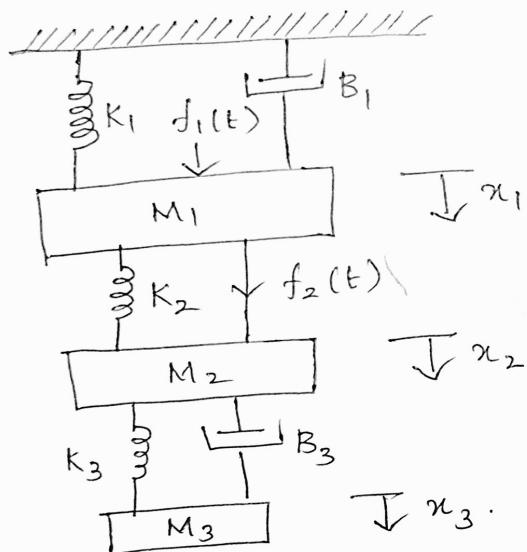

Solution:

M₁ - free body diagram

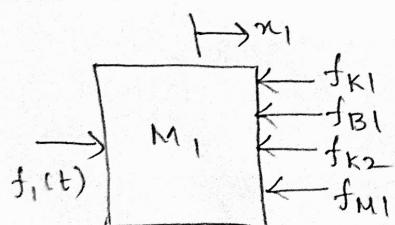

$$f_{M1} = M_1 \frac{d^2x_1}{dt^2}$$

$$f_{K1} = K_1 x_1$$

$$f_{B1} = B_1 \frac{dx_1}{dt}$$


$$f_{K2} = K_2 (x_1 - x_2)$$

By Newton's II - law,

$$f_1(t) = f_{M1} + f_{K1} + f_{B1} + f_{K2}$$

$$\boxed{f_1(t) = M_1 \frac{d^2x_1}{dt^2} + K_1 x_1 + B_1 \frac{dx_1}{dt} + K_2 (x_1 - x_2)} \quad \textcircled{1}$$

$M_2 \rightarrow$ free body diagram

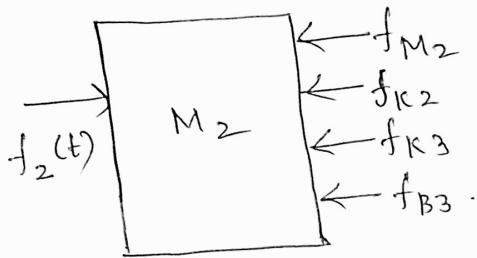

$$f_{M2} = M_2 \frac{d^2x_2}{dt^2}$$

$$f_{K2} = K_2 (x_2 - x_1)$$

$$f_{K3} = K_3 (x_2 - x_3)$$


$$f_{B3} = B_3 \frac{d(x_2 - x_3)}{dt}$$

By Newton's II law,

$$f_2(t) = f_{M2} + f_{K2} + f_{K3} + f_{B3}.$$

$$\boxed{f_2(t) = M_2 \frac{d^2x_2}{dt^2} + K_2 (x_2 - x_1) + K_3 (x_2 - x_3) + B_3 \frac{d(x_2 - x_3)}{dt}} \quad \textcircled{2}$$

$M_3 \rightarrow$ free body diagram:

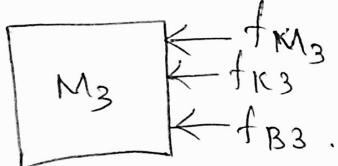

$$f_{M3} = M_3 \frac{d^2x_3}{dt^2}$$

$$f_{K3} = K_3 (x_3 - x_2)$$

$$f_{B3} = B_3 \frac{d(x_3 - x_2)}{dt}$$

By Newton's II - law

$$f_{M3} + f_{K3} + f_{B3} = 0$$

$$\boxed{M_3 \frac{d^2x_3}{dt^2} + K_3 (x_3 - x_2) + B_3 \frac{d(x_3 - x_2)}{dt} = 0} \quad \textcircled{3}$$


We know that, $\frac{d^2x}{dt^2} = \frac{dv}{dt}$, $\frac{dx}{dt} = v$ and $x = \int v dt$. (1)

on Replacing the displacements by velocities in differential equations (1), (2) & (3),

$$f_1(t) = M_1 \frac{dv_1}{dt} + B_1 v_1 + K_2 \int (v_1 - v_2) dt + K_1 \int v_1 dt \quad (4)$$

$$f_2(t) = M_2 \frac{dv_2}{dt} + B_3 [v_2 - v_3] + K_2 \int (v_2 - v_1) dt + K_3 \int (v_2 - v_3) dt \quad (5)$$
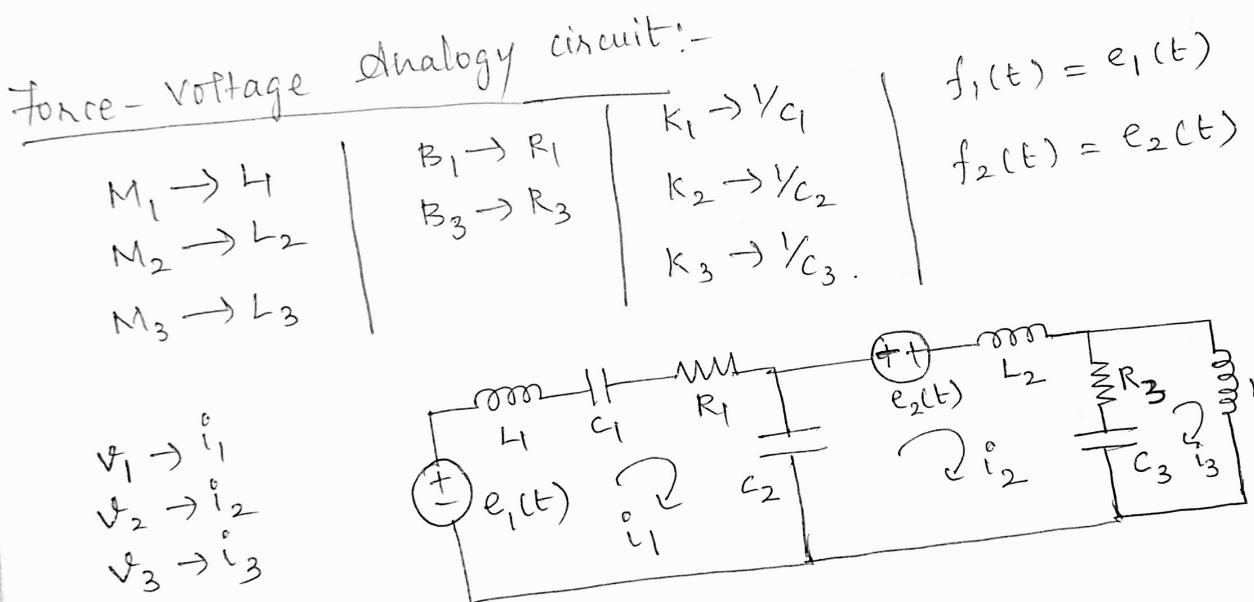
$$0 = M_3 \frac{dv_3}{dt} + B_3 [v_3 - v_2] + K_3 \int (v_3 - v_2) dt \quad (6)$$



Mesh Equations:-

loop 1: $e_1(t) = L_1 \frac{d\dot{i}_1}{dt} + \frac{1}{C_1} \int \ddot{i}_1 dt + R_1 \dot{i}_1 + \frac{1}{C_2} \int (\dot{i}_1 - \dot{i}_2) dt$

loop 2: $e_2(t) = L_2 \frac{d\dot{i}_2}{dt} + R_3 (\dot{i}_2 - \dot{i}_3) + \frac{1}{C_3} \int (\dot{i}_2 - \dot{i}_3) dt + \frac{1}{C_2} \int (\dot{i}_2 - \dot{i}_1) dt$

loop 3: $R_3 (\dot{i}_3 - \dot{i}_2) + \frac{1}{C_3} \int (\dot{i}_3 - \dot{i}_2) dt + L_3 \frac{d\dot{i}_3}{dt} = 0$

Force-current Analogy circuit:-


$$\begin{array}{l} M_1 \rightarrow C_1 \\ M_2 \rightarrow C_2 \\ M_3 \rightarrow C_3 \end{array}$$

$$\begin{array}{l} B_1 \rightarrow Y_{R_1} \\ B_3 \rightarrow Y_{R_3} \end{array}$$

$$\begin{array}{l} K_1 \rightarrow Y_{L_1} \\ K_2 \rightarrow Y_{L_2} \\ K_3 \rightarrow Y_{L_3} \end{array}$$

$$\begin{array}{l} f_1(t) \rightarrow i_1(t) \\ f_2(t) \rightarrow i_2(t) \end{array}$$
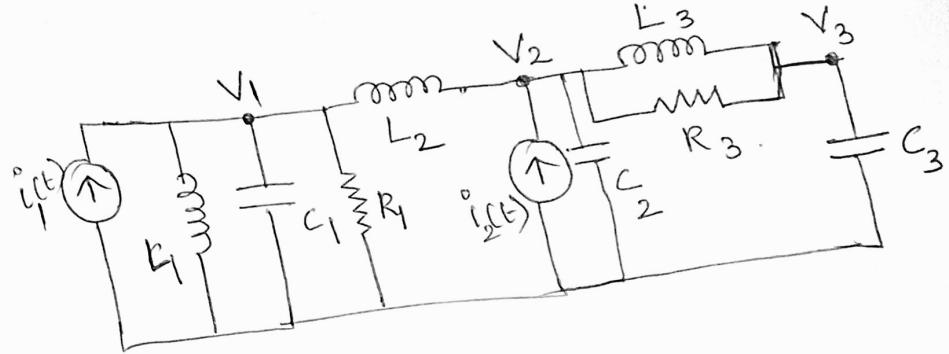
$$\begin{array}{l} V_1 \rightarrow V_1 \\ V_2 \rightarrow V_2 \\ V_3 \rightarrow V_3 \end{array}$$



Node equations.


$$\text{Node 1: } \frac{1}{L_1} \int v_1 dt + C_1 \frac{dv_1}{dt} + \frac{v_1}{R_1} + \frac{1}{L_2} \int (v_1 - v_2) dt = i_1(t)$$

$$\text{Node 2: } \frac{1}{L_2} \int (v_2 - v_1) dt + C_2 \frac{dv_2}{dt} + \frac{1}{L_3} \int (v_2 - v_3) dt + \frac{(v_2 - v_3)}{R_3} = i_2(t)$$


$$\text{Node 3: } \frac{1}{L_3} \int (v_3 - v_1) dt + \frac{1}{R_3} (v_3 - v_2) + C_3 \frac{dv_3}{dt} = 0$$

It is inferred that the node equations and mesh equations are similar to ~~that~~ of the differential equations, (4), (5) & (6).

(ii)

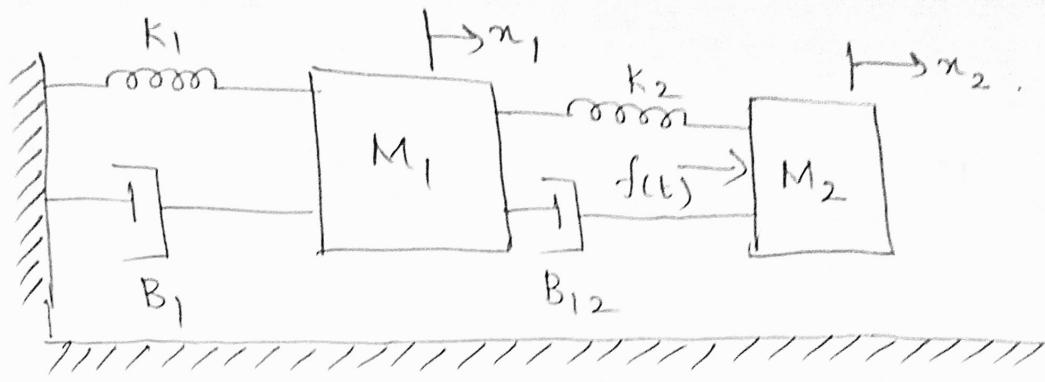

③

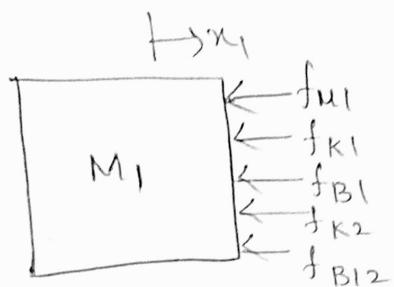Solu

$$f_{M1} = M_1 \frac{d^2 x_1}{dt^2}$$

$$f_{K1} = k_1 x_1$$


$$f_{B1} = B_1 \frac{dx_1}{dt}$$

$$f_{K2} = k_2 (x_1 - x_2)$$

$$f_{B12} = B_{12} \frac{d(x_1 - x_2)}{dt}$$

By Newton's II law,
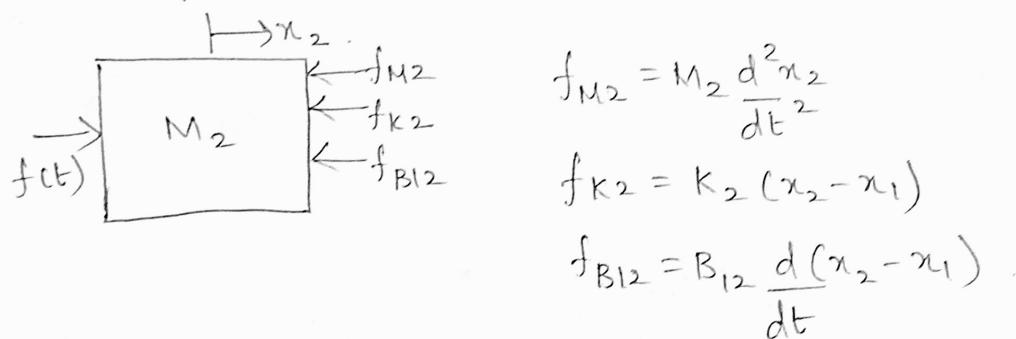
$$\boxed{M_1 \frac{d^2 x_1}{dt^2} + B_1 \frac{dx_1}{dt} + B_{12} \frac{d(x_1 - x_2)}{dt} + k_1 x_1 + k_2 (x_1 - x_2) = 0} \quad ①$$



$$f_{M2} = M_2 \frac{d^2 x_2}{dt^2}$$

$$f_{K2} = k_2 (x_2 - x_1)$$

$$f_{B12} = B_{12} \frac{d(x_2 - x_1)}{dt}$$

By Newton's II law,

$$\boxed{M_2 \frac{d^2 x_2}{dt^2} + B_{12} \frac{d(x_2 - x_1)}{dt} + k_2 (x_2 - x_1) = f(t)} \quad ②$$

→ Replace, the displacements by Velocities,

$$M_1 \frac{dv_1}{dt} + B_1 v_1 + B_{12} (v_1 - v_2) + k_1 \int v_1 dt + k_2 \int (v_1 - v_2) dt = 0 \quad (3)$$

$$M_2 \frac{dv_2}{dt} + B_{12} (v_2 - v_1) + k_2 \int (v_2 - v_1) dt = f(t) \quad (4)$$


→ Force-voltage analogy circuit

$$\begin{array}{lll} M_1 \rightarrow L_1 & B_1 \rightarrow R_1 & K_1 \rightarrow \frac{1}{C_1} \\ M_2 \rightarrow L_2 & B_{12} \rightarrow R_{12} & K_2 \rightarrow \frac{1}{C_2} \end{array}$$

$$f(t) = e(t)$$

$$V_1 = \overset{\circ}{i}_1$$

$$V_2 = \overset{\circ}{i}_2$$

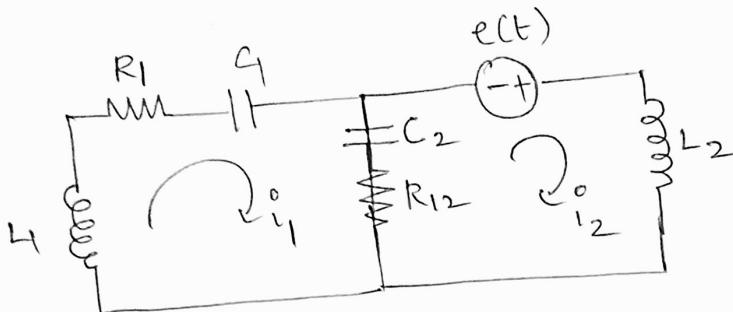

Mesh equations:-

$$\text{loop 1: } L_1 \frac{d\overset{\circ}{i}_1}{dt} + R_1 \overset{\circ}{i}_1 + \frac{1}{C_1} \int \overset{\circ}{i}_1 dt + \frac{1}{C_2} \int (\overset{\circ}{i}_1 - \overset{\circ}{i}_2) dt + R_{12} (\overset{\circ}{i}_1 - \overset{\circ}{i}_2) = 0$$

$$\text{loop 2: } L_2 \frac{d\overset{\circ}{i}_2}{dt} + R_{12} (\overset{\circ}{i}_2 - \overset{\circ}{i}_1) + \frac{1}{C_2} \int (\overset{\circ}{i}_2 - \overset{\circ}{i}_1) dt = e(t).$$


→ Force-current analogy circuit

$$\begin{array}{lll} M_1 \rightarrow C_1 & B_1 \rightarrow \frac{1}{R_1} & K_1 \rightarrow \frac{1}{L_1} \\ M_2 \rightarrow C_2 & B_{12} \rightarrow \frac{1}{R_{12}} & K_2 \rightarrow \frac{1}{L_2} \end{array}$$

$$f(t) = \overset{\circ}{i}(t)$$

$$V_1 = \overset{\circ}{V}_1$$

$$V_2 = \overset{\circ}{V}_2$$

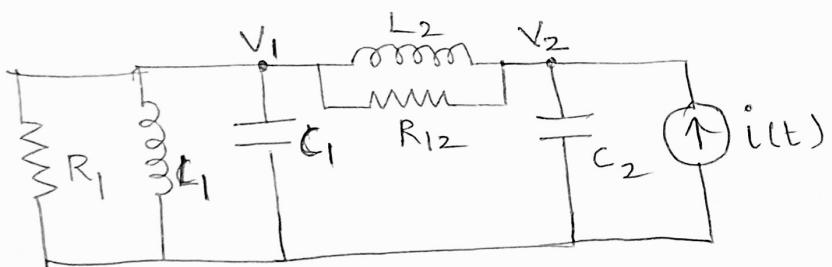


Node Equations:

$$\text{node 1: } \frac{V_1}{R_1} + \frac{1}{L_1} \int V_1 dt + C_1 \frac{dV_1}{dt} + \frac{1}{L_2} \int (V_1 - V_2) dt + \frac{(V_1 - V_2)}{R_{12}} = 0$$

$$\text{node 2: } C_2 \frac{dV_2}{dt} + \frac{1}{L_2} \int (V_2 - V_1) dt + \frac{V_2 - V_1}{R_{12}} = \overset{\circ}{i}(t)$$


The node equations & Mesh equations are similar to the differential equations (3) + (4).

(iii)

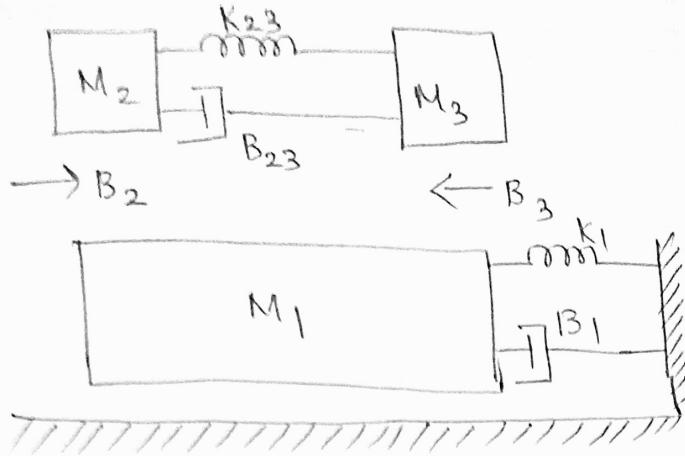

Q

soln

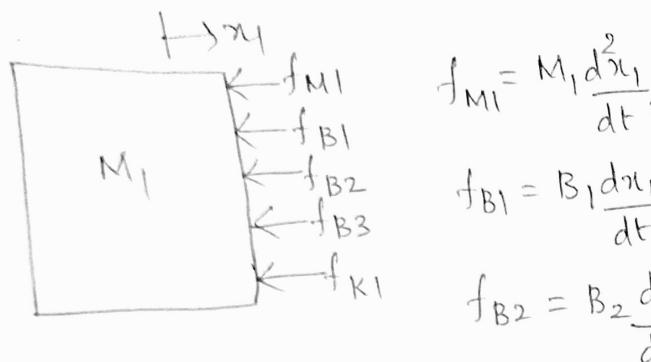

$$f_{M1} = M_1 \frac{d^2 x_1}{dt^2}$$

$$f_{B1} = B_1 \frac{dx_1}{dt}$$


$$f_{B2} = B_2 \frac{d(x_1 - x_2)}{dt}$$

$$f_{B3} = B_3 \frac{d(x_1 - x_3)}{dt}$$

$$f_{K1} = K_1 x_1$$

By Newton's II-law,
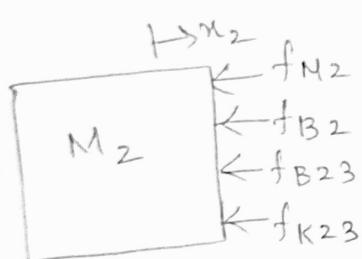
$$M_1 \frac{d^2 x_1}{dt^2} + B_1 \frac{dx_1}{dt} + B_2 \frac{d(x_1 - x_2)}{dt} + B_3 \frac{d(x_1 - x_3)}{dt} + K_1 x_1 = 0 \quad (1)$$



$$f_{M2} = M_2 \frac{d^2 x_2}{dt^2}$$


$$f_{K23} = K_{23} (x_2 - x_3)$$

$$f_{B2} = B_2 \frac{d(x_2 - x_1)}{dt}$$

$$f_{B23} = B_{23} \frac{d(x_2 - x_3)}{dt}$$

By Newton's II law
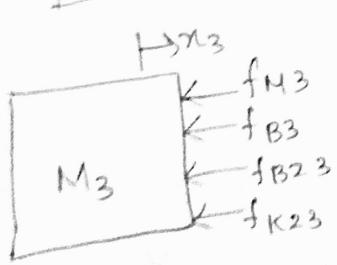
$$M_2 \frac{d^2 x_2}{dt^2} + B_{23} \frac{d(x_2 - x_3)}{dt} + B_2 \frac{d(x_2 - x_1)}{dt} + K_{23} (x_2 - x_3) = 0 \quad (2)$$



$$f_{M3} = M_3 \frac{d^2 x_3}{dt^2}$$

$$f_{K23} = K_{23} (x_3 - x_2)$$

$$f_{B3} = B_3 \frac{d(x_3 - x_1)}{dt}$$

$$f_{B23} = B_{23} \frac{d(x_3 - x_2)}{dt}$$

By Newton's II law,

$$M_3 \frac{d^2 x_3}{dt^2} + B_3 \frac{dx_3 - x_1}{dt} + B_{23} \frac{d(x_3 - x_2)}{dt} + K_{23}(x_3 - x_2) = 0. \quad (3)$$

Replace displacements by velocities,

$$M_1 \frac{dv_1}{dt} + B_1 v_1 + B_2(v_1 - v_2) + B_3(v_1 - v_3) + K_1 \int v_1 dt = 0 \quad (4)$$


$$M_2 \frac{dv_2}{dt} + B_{23}(v_2 - v_3) + B_2(v_2 - v_1) + K_{23} \int (v_2 - v_3) dt = 0 \quad (5)$$

$$M_3 \frac{dv_3}{dt} + B_3(v_3 - v_1) + B_{23}(v_3 - v_2) + K_{23} \int (v_3 - v_2) dt = 0. \quad (6)$$

→ Force-voltage analogy circuit

$$\begin{array}{lll} M_1 \rightarrow L & B_1 \rightarrow R_1 & K_1 \rightarrow V_{C_1} \\ M_2 \rightarrow L_2 & B_2 \rightarrow R_2 & K_{23} \rightarrow V_{C_{23}} \\ M_3 \rightarrow L_3 & B_3 \rightarrow R_3 & \\ & B_{23} \rightarrow R_{23} & \end{array}$$
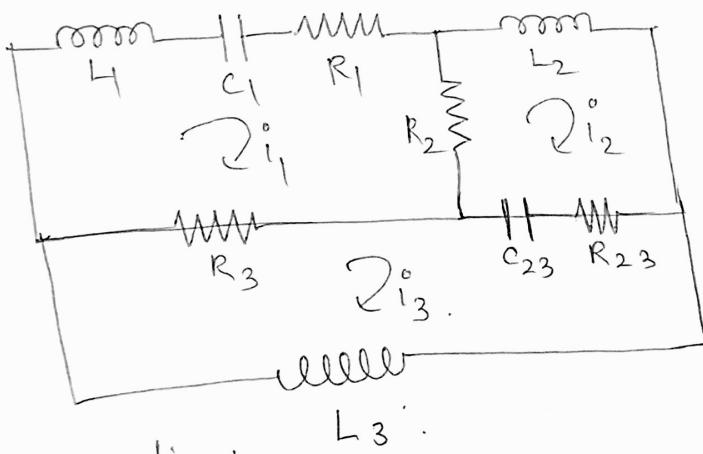
$$\begin{array}{l} v_1 \rightarrow i_1 \\ v_2 \rightarrow i_2 \\ v_3 \rightarrow i_3 \end{array}$$



Mesh equations:-

$$\text{loop 1: } L_1 \frac{di_1}{dt} + \frac{1}{C_1} \int i_1 dt + R_1 i_1 + R_2(i_1 - i_2) + R_3(i_1 - i_3) = 0.$$


$$\text{loop 2: } L_2 \frac{di_2}{dt} + R_{23}(i_2 - i_3) + \frac{1}{C_{23}} \int (i_2 - i_3) dt + R_2(i_2 - i_1) = 0$$

$$\text{loop 3: } L_3 \frac{di_3}{dt} + R_{23}(i_3 - i_1) + \frac{1}{C_{23}} \int (i_3 - i_2) dt + R_{23}(i_3 - i_2) = 0.$$

Force-current Analogy circuit

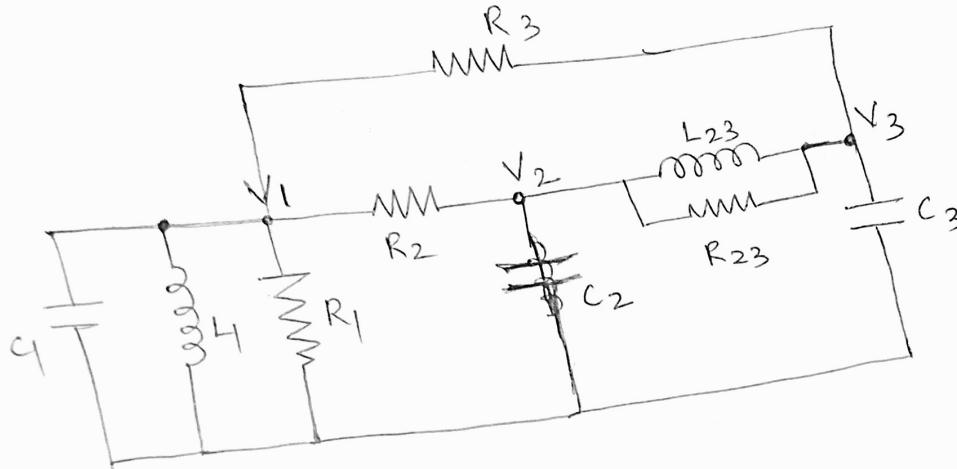(5)

$$\begin{array}{lll}
 M_1 \rightarrow C_1 & B_1 \rightarrow V/R_1 & K_1 \rightarrow 1/L \\
 M_2 \rightarrow C_2 & B_2 \rightarrow V/R_2 & K_{23} \rightarrow 1/R_{23} \\
 M_3 \rightarrow C_3 & B_3 \rightarrow 1/R_3 & V_1 \rightarrow V_1 \\
 & B_{23} \rightarrow V/R_{23} & V_2 \rightarrow V_2 \\
 & & V_3 \rightarrow V_3
 \end{array}$$



Node Equations:-


$$\text{node 1: } C_1 \frac{dv_1}{dt} + \frac{1}{L_1} \int v_1 dt + \frac{v_1}{R_1} + \frac{(v_1 - v_2)}{R_2} + \frac{(v_1 - v_3)}{R_3} = 0.$$

$$\text{node 2: } C_2 \frac{dv_2}{dt} + \frac{(v_2 - v_1)}{R_2} + \frac{1}{L_{23}} \int (v_2 - v_3) dt + \frac{v_2 - v_3}{R_{23}} = 0.$$


$$\text{node 3: } C_3 \frac{dv_3}{dt} + \frac{1}{L_{23}} \int (v_3 - v_2) dt + \frac{(v_3 - v_2)}{R_{23}} + \frac{(v_3 - v_1)}{R_3} = 0.$$

The Mesh & node equations are similar to the differential equations (4), (5) & (6) of mechanical S/m's.

iv)

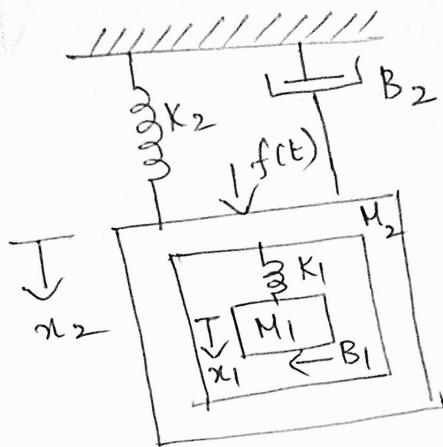

solve

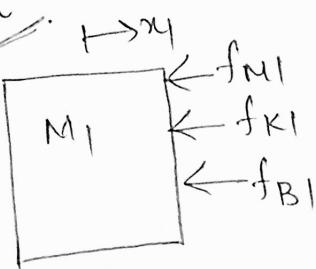


$$f_{M1} = M_1 \frac{d^2x_1}{dt^2}$$

$$f_{B1} = B_1 \frac{d(x_1 - x_2)}{dt}$$

$$f_{K1} = K_1(x_1 - x_2)$$

By Newton's II-law
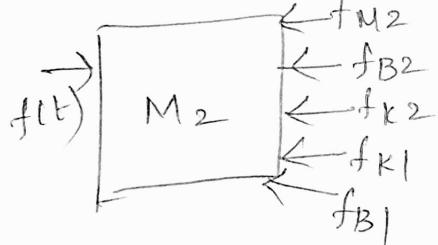
$$M_1 \frac{d^2x_1}{dt^2} + B_1 \frac{d(x_1 - x_2)}{dt} + K_1(x_1 - x_2) = 0 \quad \boxed{1}$$



$$f_{M2} = M_2 \frac{d^2x_2}{dt^2}$$

$$f_{B2} = B_2 \frac{d x_2}{dt}$$

$$f_{K2} = K_2 x_2$$

$$f_{K1} = K_1(x_2 - x_1)$$

$$f_{B1} = B_1 \frac{d(x_2 - x_1)}{dt}$$

By Newton's II-law.

$$M_2 \frac{d^2x_2}{dt^2} + B_2 \frac{dx_2}{dt} + B_1 \frac{d(x_2 - x_1)}{dt} + K_1(x_2 - x_1) + K_2 x_2 = f(t) \quad \boxed{2}$$

Replacing displacements by velocities, (6)


$$M_1 \frac{dv_1}{dt} + B_1(v_1 - v_2) + K_1 \int (v_1 - v_2) dt = 0 \quad (3)$$

$$M_2 \frac{dv_2}{dt} + B_2 v_2 + B_1(v_2 - v_1) + K_1 \int (v_2 - v_1) dt + K_2 \int v_2 dt = f(t) \quad (4)$$

Force-Voltage Analogous circuit:

$$\begin{array}{lll} M_1 \rightarrow L & B_1 \rightarrow R_1 & K_1 \rightarrow 1/C_1 \\ M_2 \rightarrow L_2 & B_2 \rightarrow R_2 & K_2 \rightarrow 1/C_2 \end{array}$$
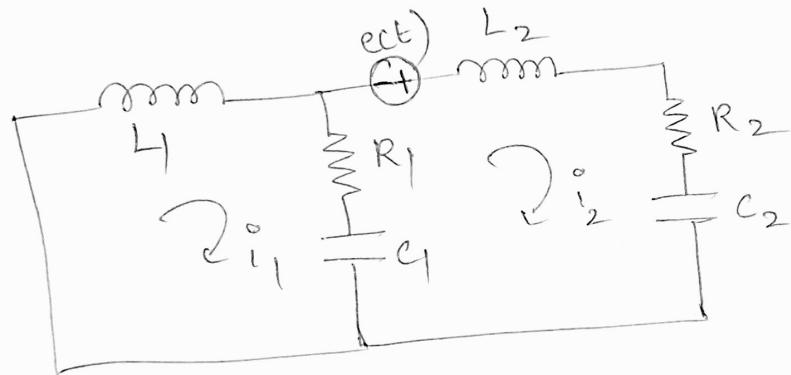
$$\begin{array}{l} f(t) \rightarrow e(t) \\ v_1 \rightarrow i_1 \\ v_2 \rightarrow i_2 \end{array}$$




Mesh Equations:

$$\text{loop 1: } L_1 \frac{di_1}{dt} + R_1(i_1 - i_2) + \frac{1}{C_1} \int (i_1 - i_2) dt = 0$$

$$\text{loop 2: } L_2 \frac{di_2}{dt} + R_2 i_2 + \frac{1}{C_2} \int i_2 dt + \frac{1}{C_1} \int (i_2 - i_1) dt + R_1(i_2 - i_1) = e(t)$$

→ Force-current analogy circuit (B)
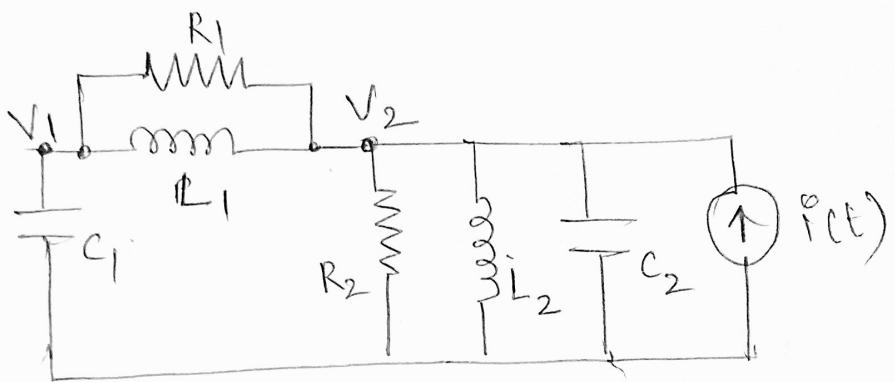
$$\begin{array}{lll}
 M_1 \rightarrow C_1 & B_1 \rightarrow V_{R_1} & K_1 \rightarrow V_L \\
 M_2 \rightarrow C_2 & B_2 \rightarrow V_{R_2} & K_2 \rightarrow V_{L_2} \\
 & & f(t) = P(t) \\
 & & v_1 \rightarrow V_1 \\
 & & v_2 \rightarrow V_2
 \end{array}$$



Node equations:

$$\text{node 1: } C_1 \frac{dV_1}{dt} + \frac{1}{L_1} \int (V_1 - V_2) dt + \frac{V_1 - V_2}{R_1} = 0.$$


$$\text{node 2: } C_2 \frac{dV_2}{dt} + \frac{1}{L_2} \int V_2 dt + \frac{V_2}{R_2} + \frac{(V_2 - V_1)}{R_1} + \frac{1}{L_1} \int (V_2 - V_1) dt = i(t)$$

→ Thus the node & mesh equations are verified
w/ the differential equations (3) & (4) of
mechanical s/m.

①


Write the differential equations governing the mechanical rotational systems. Draw the Torque-voltage and Torque-current electrical analogous circuits and verify by writing mesh and node equations.

(i)

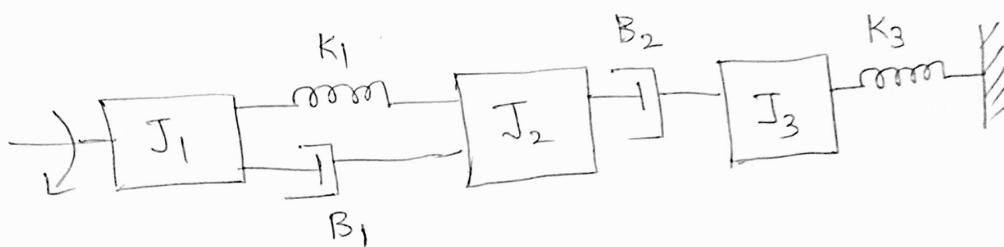


Solu:-

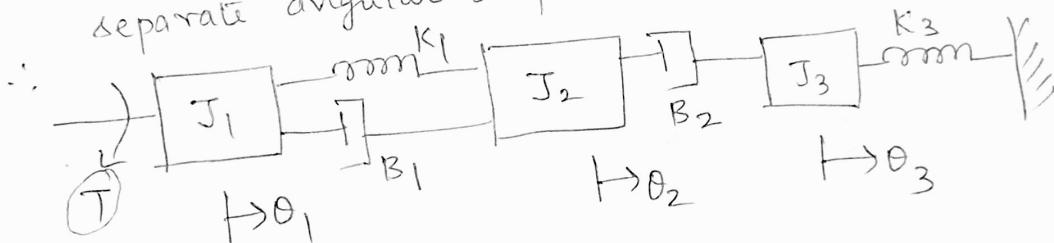→ In the above diagram, there is one arrow mark indication is given. We have to assume that one i/p torque is given to J_1 . Also assume separate angular displacements (θ) for each (J).



J_1 - free body diagram.

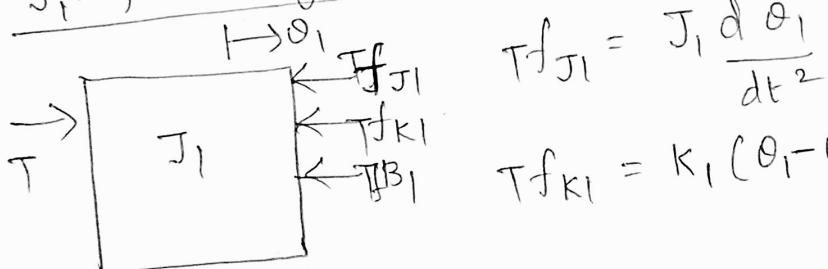

$$T_f_{J1} = J_1 \frac{d^2\theta_1}{dt^2}$$


$$T_f_{B1} = B_1 \frac{d(\theta_1 - \theta_2)}{dt}$$

$$T_f_{K1} = K_1 (\theta_1 - \theta_2)$$

By newton's II-law

$$J_1 \frac{d^2\theta_1}{dt^2} + B_1 \frac{d(\theta_1 - \theta_2)}{dt} + K_1 (\theta_1 - \theta_2) = T \quad \boxed{1}$$

$J_2 \rightarrow$ free body diagram.

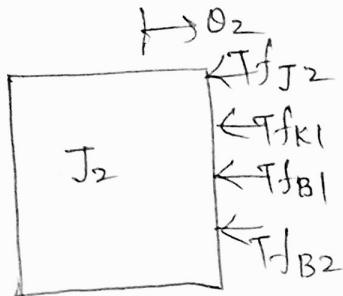

$$T_f_{J2} = J_2 \frac{d^2(\theta_2)}{dt^2}$$

$$T_f_{K1} = K_1(\theta_2 - \theta_1)$$

$$T_f_{B1} = B_1 \frac{d(\theta_2 - \theta_1)}{dt}$$


$$T_f_{B2} = B_2 \frac{d(\theta_2 - \theta_3)}{dt}$$

By newton's II law,

$$J_2 \frac{d^2\theta_2}{dt^2} + B_1 \frac{d(\theta_2 - \theta_1)}{dt} + B_2 \frac{d(\theta_2 - \theta_3)}{dt} + K_1(\theta_2 - \theta_1) = 0$$

(2)

$J_3 \rightarrow$ free body diagram.

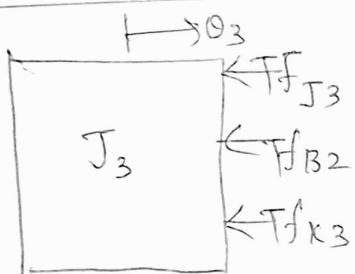

$$T_f_{J3} = J_3 \frac{d^2\theta_3}{dt^2}$$

$$T_f_{B2} = B_2 \frac{d(\theta_3 - \theta_2)}{dt}$$

$$T_f_{K3} = K_3 \theta_3 .$$

$$\therefore J_3 \frac{d^2\theta_3}{dt^2} + B_2 \frac{d(\theta_3 - \theta_2)}{dt} + K_3 \theta_3 = 0 \quad (3)$$

→ Replace angular displacement with angular velocities (ω)

$$\frac{d^2\theta}{dt^2} = \frac{d\omega}{dt}, \quad \frac{d\theta}{dt} = \omega, \quad \theta = \int \omega dt .$$


$$\rightarrow J_1 \frac{d\omega_1}{dt} + B_1(\omega_1 - \omega_2) + K_1 \int (\omega_1 - \omega_2) dt = T \quad (4)$$

$$J_2 \frac{d\omega_2}{dt} + B_1(\omega_2 - \omega_1) + B_2(\omega_2 - \omega_3) + K_1 \int (\omega_2 - \omega_1) dt = 0 \quad (5)$$

$$J_3 \frac{d\omega_3}{dt} + B_2 (\omega_3 - \omega_2) + K_3 \int \omega_3 dt = 0 \quad (6)$$

\rightarrow Torque - voltage analogous circuit

$J_1 \rightarrow L_1$	$B_1 \rightarrow R_1$	$K_1 \rightarrow 1/C_1$	$T \rightarrow e(t)$
$J_2 \rightarrow L_2$	$B_2 \rightarrow R_2$	$K_2 \rightarrow 1/C_2$	$\omega_1 \rightarrow i_1$
$J_3 \rightarrow L_3$			$\omega_2 \rightarrow i_2$
			$\omega_3 \rightarrow i_3$

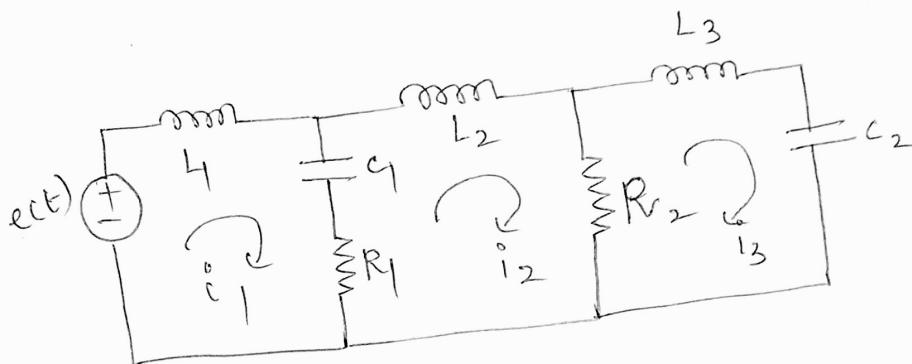

Mech equations:-


$$L_1 \frac{di_1}{dt} + \frac{1}{C_1} \int (i_1 - i_2) dt + R_1 (i_1 - i_2) = e(t)$$

$$L_2 \frac{di_2}{dt} + R_2 (i_2 - i_3) + R_1 (i_2 - i_1) + \frac{1}{C_1} \int (i_2 - i_1) dt = 0$$

$$L_3 \frac{di_3}{dt} + \frac{1}{C_2} \int i_3 dt + R_2 (i_3 - i_2) = 0$$

\rightarrow Torque - current analogous circuit

$J_1 \rightarrow C_1$	$B_1 \rightarrow V_{R1}$	$K_1 \rightarrow V_{L1}$	$T = i(t)$
$J_2 \rightarrow C_2$	$B_2 \rightarrow V_{R1}$	$K_2 \rightarrow V_{L2}$	$\omega_1 \rightarrow V_1$
$J_3 \rightarrow C_3$			$\omega_2 \rightarrow V_2$
			$\omega_3 \rightarrow V_3$

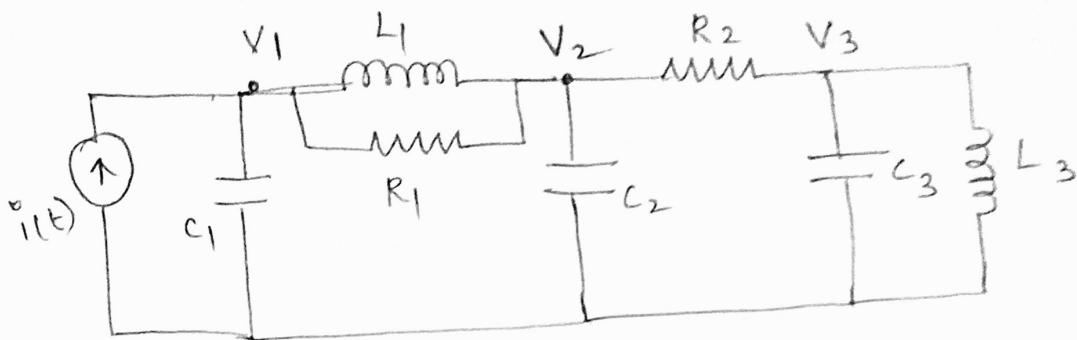


node equations:-

$$\text{node 1: } C_1 \frac{dv_1}{dt} + \frac{1}{L_1} \int (v_1 - v_2) dt + \left(\frac{v_1 - v_2}{R_1} \right) = i(t)$$

$$\text{node 2: } C_2 \frac{dv_2}{dt} + \frac{1}{L_1} \int (v_2 - v_1) dt + \frac{v_2 - v_1}{R_1} + \frac{v_2 - v_3}{R_2} = 0$$

$$\text{node 3: } C_3 \frac{dv_3}{dt} + \frac{v_3 - v_2}{R_2} + \frac{1}{L_3} \int v_3 dt = 0$$

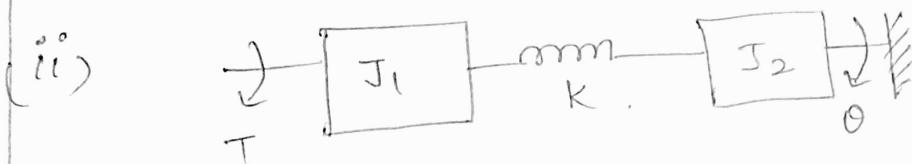→ Thus the node & mesh equations are verified with eqn (6)/eqn (6)



solve. → θ_1 (assume)

$$T_f J_1 = J_1 \frac{d^2 \theta_1}{dt^2}$$

$$T_f K = K (\theta_1 - \theta)$$

$$\therefore \boxed{J_1 \frac{d^2 \theta_1}{dt^2} + K (\theta_1 - \theta) = T} \quad \text{①}$$

$$\begin{aligned} \text{For } \theta_2: & T_f J_2 = J_2 \frac{d^2 \theta_2}{dt^2} & T_f K_1 = K_b (\theta - \theta_1) \\ & J_2 \leftarrow T_f K_2 \end{aligned}$$

$$\therefore \boxed{J_2 \frac{d^2 \theta_2}{dt^2} + K_b (\theta - \theta_1) = 0} \quad \text{②}$$


→ Replace the angular displacements by angular velocities.

$$J_1 \frac{d\omega_1}{dt} + K \int (\omega_1 - \omega) dt = T \quad (3)$$

$$J_2 \frac{d\omega_2}{dt} + K \int (\omega - \omega_1) dt = 0 \quad (4)$$

→ Torque-voltage analogy:

$$\begin{array}{c|c|c} J_1 \rightarrow L & K \rightarrow 1/C_1 & T \rightarrow R(t) \\ \hline J_2 \rightarrow L_2 & & \omega \rightarrow i \\ & & \omega_1 \rightarrow i_1 \end{array}$$

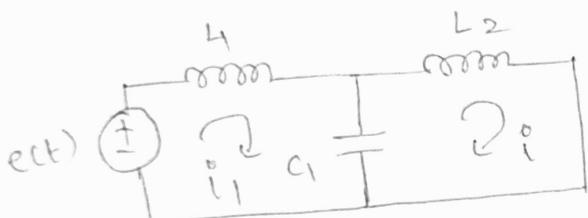


node equations:-

$$\text{loop 1: } L_1 \frac{di_1}{dt} + \frac{1}{C_1} \int (i_1 - i) dt = e(t) .$$

$$\text{loop 2: } L_2 \frac{di_2}{dt} + \frac{1}{C_1} \int (i - i_1) dt = 0 .$$

→ Torque-current analogy

$$\begin{array}{c|c|c} J_1 \rightarrow q & K \rightarrow 1/L_1 & T \rightarrow i(t) \\ \hline J_2 \rightarrow C_2 & & \omega \rightarrow v \\ & & \omega_1 \rightarrow v_1 \end{array}$$

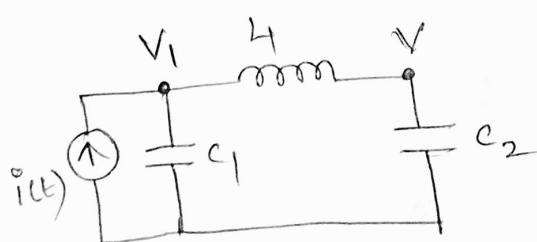

node equations:-

$$\text{node 1: } C_1 \frac{dv_1}{dt} + \frac{1}{L_1} \int (v_1 - v) dt = i(t) .$$

$$\text{node 2: } C_2 \frac{dv_2}{dt} + \frac{1}{L_1} \int (v - v_1) dt = 0 .$$

Node & Mesh equ. thus Verified.