

Unit-II

Transmission lines & wave guides

Impedance matching and transformation

Reflection phenomena - standing waves,

$\lambda/8$, $\lambda/4$ and $\lambda/2$ lines \rightarrow $1/4$ Impedance

transformers, stub matching - Single and Double stub - Smith chart and

Applications - Numerical Examples.

From $\lambda = \frac{c}{f}$ $\lambda = \frac{300}{10^9} = 30 \mu m$

at $10^9 Hz$ $\lambda = 30 \mu m$

$$\textcircled{2} \rightarrow \frac{1}{30} = \alpha = \frac{1}{\lambda}$$

Constants for the line of zero dissipation

for transmission of energy at high frequencies, where the power efficiency is high, it is possible to assume negligible losses or zero dissipation in the analysis of performance of transmission lines.

The line parameters for the line of zero dissipation are, ($R + G = 0$)

$$Z = j\omega L; \quad Y = j\omega C$$

\therefore The charac. imp Z_0 may be written as

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{j\omega L}{j\omega C}} = \sqrt{\frac{L}{C}} \text{ ohms.} \quad \text{--- (1)}$$

This value is wholly resistive & may be given by the symbol R_0 ,

$$Z_0 = R_0 = \sqrt{\frac{L}{C}} \quad \text{--- (2)}$$

Voltages & currents on the dissipationless line

The voltage at any point distant s units from the receiving end to a transmission line is,

$$E_s = \frac{E_R (Z_R + Z_0)}{2Z_R} (e^{jBs} + k e^{-js})$$

for the line of zero dissipation, when $k = 0$
 $Z_0 = R_0$. So that,


$$E_s = \frac{E_R (Z_R + R_0)}{2Z_R} (e^{jBs} + k e^{-js}) \quad \text{--- (2)}$$

e^{jBs} \rightarrow wave propagating from source to load

e^{-js} \rightarrow reflected wave moving from load back towards the source.

- * The magnitude of the reflected wave is dependent on the value of k , the reflection co-efficient.

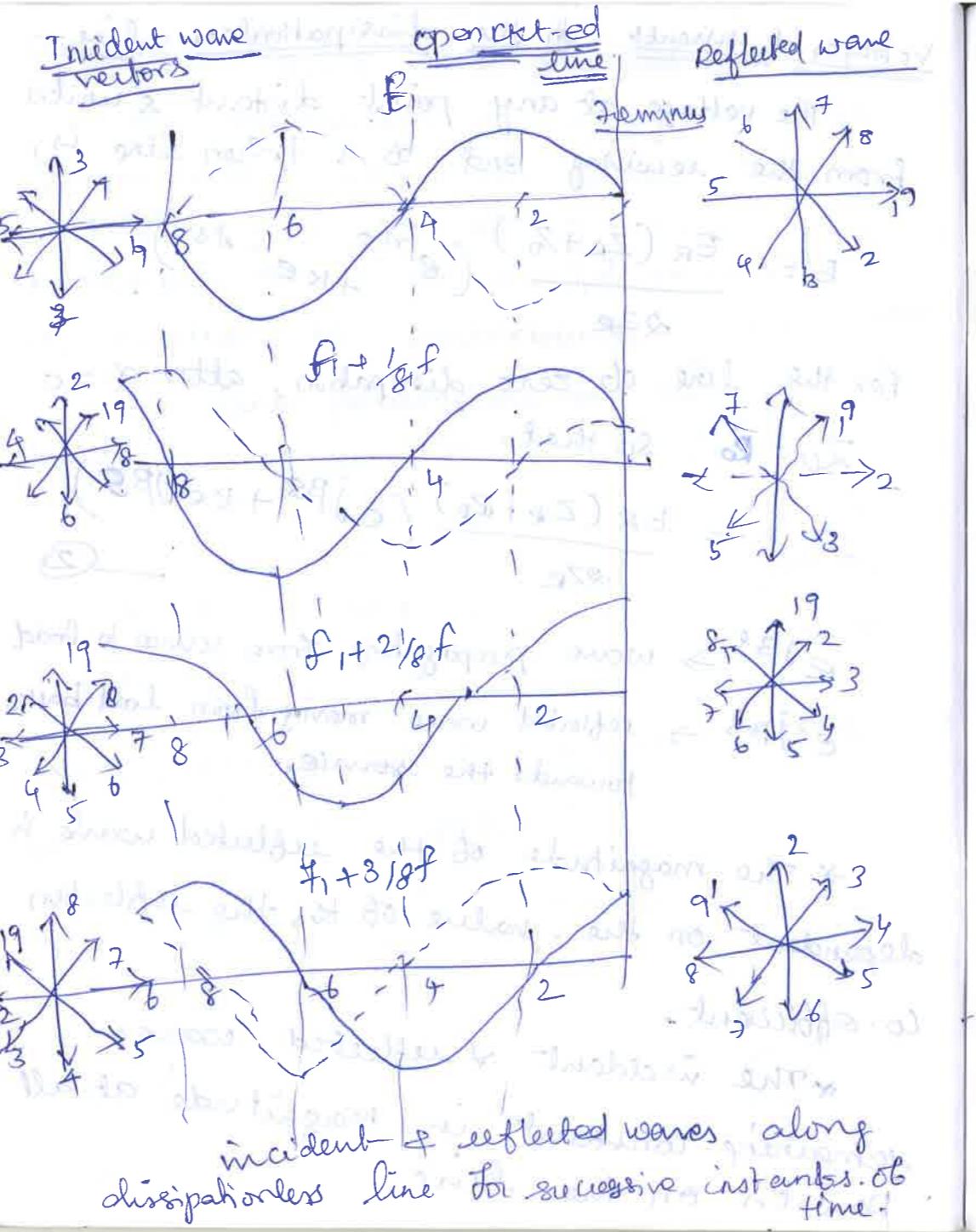- * The incident & reflected waves remaining constant in magnitude at all points on the line.



* The actual voltage at any point on the transmission line is the sum of the incident and reflected wave voltages at that point.


The sum voltage

is plotted in fig
(open circuited line)

* It can be seen that the resultant total voltage wave appears to stand still on the line, oscillating in magnitude with time but having fixed positions of maxima and minima.

* Such a wave is known as standing wave.

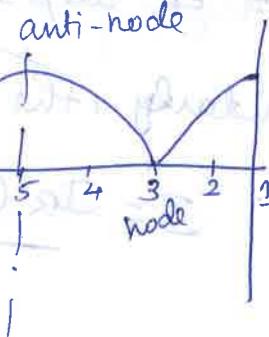* If line voltages are measured with an effective voltmeter, the magnitude will appear like as in fig 7



* Since the voltmeter does not distinguish b/w positive and negative values.

Equation ② may be reduced to,

$$E = \frac{E_R}{Z_R} \left[Z_R \frac{e^{j\beta z} + e^{-j\beta z}}{2} + jR_o \frac{e^{j\beta z} - e^{-j\beta z}}{2j} \right]$$

$$\begin{aligned} &= \frac{E_R (Z_R + R_o)}{2Z_R} \left[e^{j\beta s} + \left(\frac{Z_R - R_o}{Z_R + R_o} \right) e^{-j\beta s} \right] \\ &= \frac{E_R}{Z_R} \frac{1}{2} \left[Z_R e^{j\beta s} + R_o e^{j\beta s} + Z_R e^{-j\beta s} - R_o e^{-j\beta s} \right] \\ &= \frac{E_R}{Z_R} \left[Z_R \left(\frac{e^{j\beta s} + e^{-j\beta s}}{2} \right) + jR_o \left(\frac{e^{j\beta s} - e^{-j\beta s}}{2j} \right) \right] \end{aligned}$$

$$E = E_R \cos \beta s + j I_R R_o \sin \beta s \quad \text{--- (3)}$$

Similarly, the current on the line is,

$$I = \frac{I_R (Z_R + Z_o)}{2Z_o} \left(e^{j\beta s} - k e^{-j\beta s} \right) \quad \text{--- (4)}$$

The current at any point on the distortionless line is,

$$I = I_R \cos \beta s + j \frac{E_R}{R_o} \sin \beta s \quad \text{--- (5)}$$

$$I = \frac{I_R (Z_R + R_o)}{2Z_R} \left[e^{j\beta s} - \left(\frac{Z_R - R_o}{Z_R + R_o} \right) e^{-j\beta s} \right]$$

$$= \frac{I_R}{2Z_R} \left[Z_R e^{j\beta s} + R_o e^{j\beta s} - Z_R e^{-j\beta s} + R_o e^{-j\beta s} \right]$$

$$= \frac{I_R}{2Z_R} \left[Z_R \left(\frac{e^{j\beta s} - e^{-j\beta s}}{2} \right) + R_o \left(\frac{e^{j\beta s} + e^{-j\beta s}}{2} \right) \right]$$

$$= I_R \cos \beta s + j \frac{E_R}{R_o} \sin \beta s$$

$$\begin{aligned} &\frac{j I_R}{Z_R} \cdot R_o \\ &= j E_R \cdot R_o \cdot \frac{1}{Z_R R_o} \\ &= j E_R \cdot R_o \cdot \frac{1}{Z_R R_o} \end{aligned}$$

From the defn. of velocity of propagation,

$$\beta = \frac{2\pi f}{v} = \frac{2\pi}{\lambda}$$

The ch. & voltage may be written as,

$$E = E_R \cos \frac{2\pi s}{\lambda} + j I_R R_0 \sin \frac{2\pi s}{\lambda} \quad (6)$$

$$I = I_R \cos \frac{2\pi s}{\lambda} + j \frac{E_R}{R_0} \sin \frac{2\pi s}{\lambda} \quad (7)$$

The current & voltage distribution is seen as the sum of cosine & quadrature sine distributions.



* If the line is OC-ed. $I_R = 0$.

$$E_{OC} = E_R \cos \frac{2\pi s}{\lambda} \quad (8)$$

$$I_{OC} = j \frac{E_R}{R_0} \sin \frac{2\pi s}{\lambda} \quad (9)$$

If the line is short circuited, then $E_R = 0$
eqn (6) becomes, $E_{SC} = j I_R R_0 \sin \frac{2\pi s}{\lambda} \quad (10)$
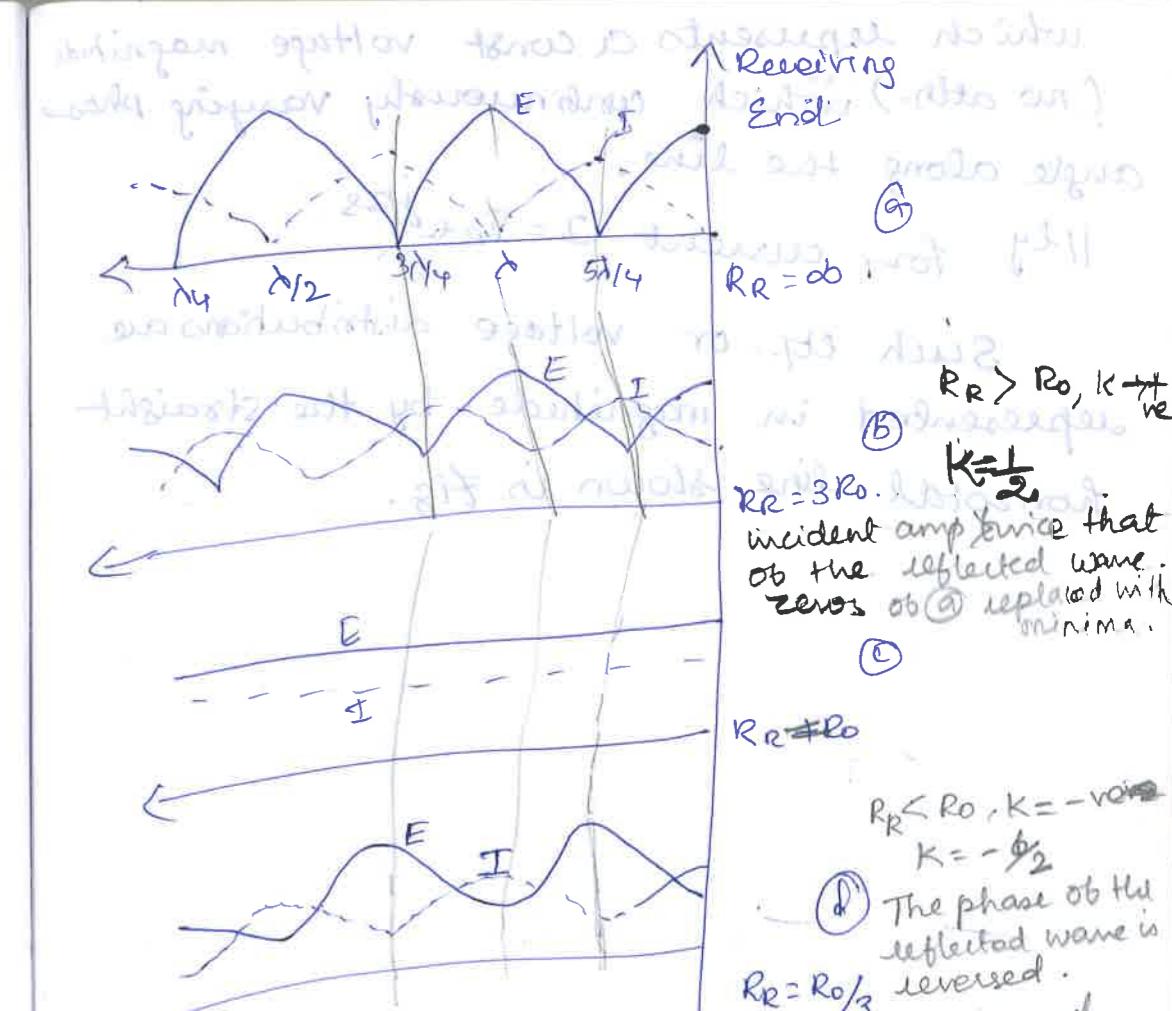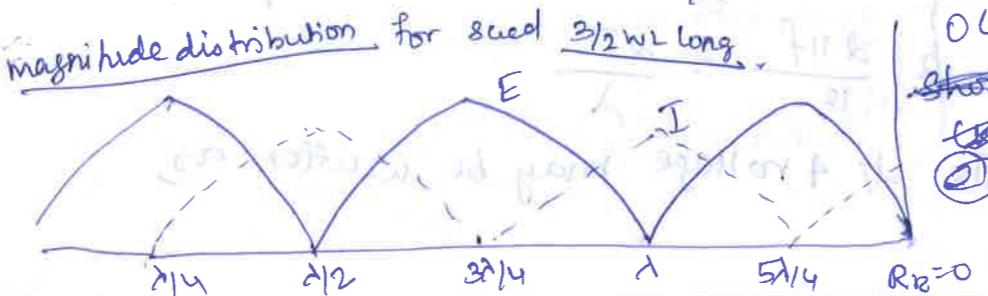
$$(7) \Rightarrow I_{SC} = I_R \cos \frac{2\pi s}{\lambda} \quad (11)$$



If the line is terminated in $Z_R = Z_0 = R_0$, the reflection coefficient and reflected wave become zero, & the voltage on the line is found $\Rightarrow E = E_R e^{j\beta s} \quad (12)$

which represents a const voltage magnitude
(no att.) which continuously varying phase
angle along the line. -

$$\text{Hence for current } I = I_0 e^{j\phi}.$$

Such ph.- or voltage distributions are
represented in magnitude by the straight
horizontal line shown in fig.



Ans. in question is such that
voltage has to be constant with
extreme option 2 & 3 are correct answer
 $\Rightarrow \text{const phi} = \theta_0$ will

which shows suitable about, const phi

between two end points all




is between and a dipole ext pole

at both ends back to

between
extremes and
at next value


constant

extreme

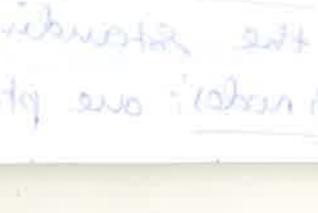 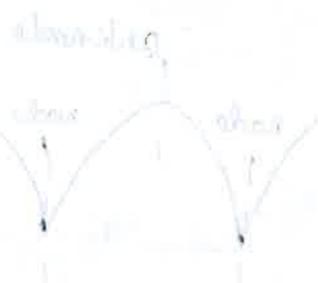

Standing Waves, nodes, Standing wave Ratio

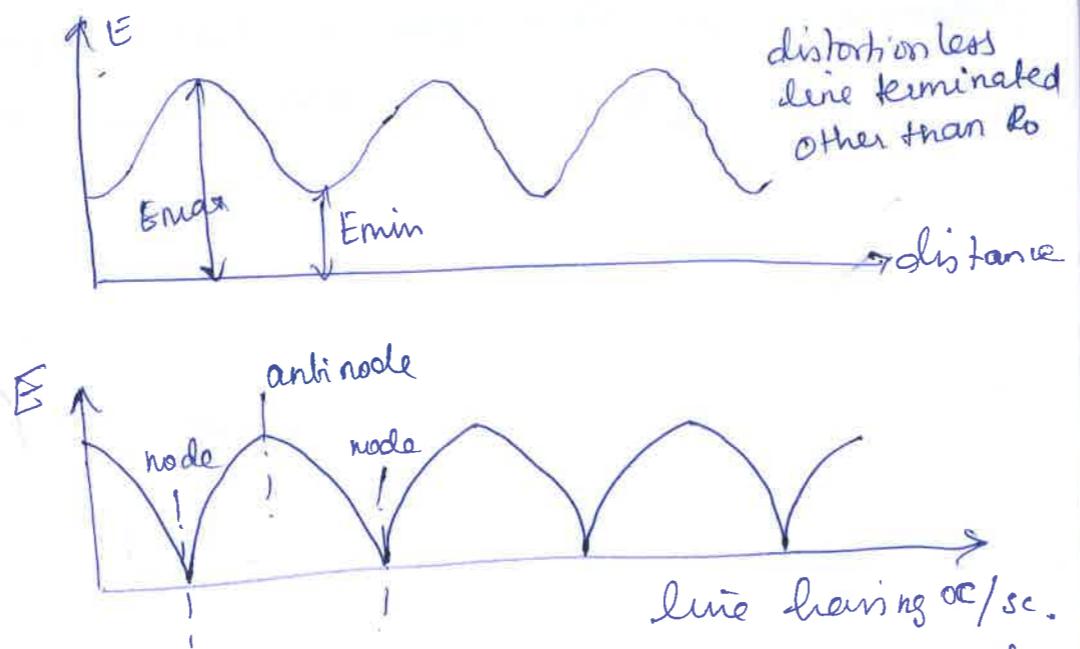The voltage magnitudes are measured along the length of a line terminated in a load other than R_0 .



* The maxima and minima values on a line are labeled as,

1) Nodes:- are pts of zero voltage or current in the standing wave system.

2) Antinodes:- are pts of max. voltage or current.

converging line terminated in R_0 has no standing waves, & called smooth line.

for open circ.

Voltage nodes occurs at :- $0, \frac{\lambda}{4}, \frac{3\lambda}{4}, \frac{5\lambda}{4}, \dots$

ct. nodes occurs at :- $0, \frac{\lambda}{2}, \lambda, \frac{3\lambda}{2}, \dots$

for short circ.

Voltage nodes $\rightarrow 0, \frac{\lambda}{2}, \lambda, \dots$

current nodes $\rightarrow \frac{\lambda}{4}, \frac{3\lambda}{4}, \frac{5\lambda}{4}, \dots$

Standing Wave Ratio $= S = \left| \frac{E_{max}}{E_{min}} \right| = \left| \frac{I_{max}}{I_{min}} \right|$

from the voltage eqn

$$E = \frac{E_R (Z_R + Z_0)}{2Z_R} (e^{jBs} + k e^{-jBs}) \quad (1)$$

At the pts where the incident & reflected waves are in phase,

$$E_{max} = \frac{E_R (Z_R + Z_0)}{2Z_R} (1 + k) \quad (2)$$

only, the Voltage minima occurs at pts


at which the incident & reflected waves are out of phase

$$E_{min} = \frac{E_R (Z_R + Z_0)}{\alpha Z_R} (1 - |\alpha|) \quad (3)$$

∴ SWR in terms of ref. Co-efficient

$$S = \frac{1 + |\alpha|}{1 - |\alpha|} \quad (4)$$

$$|\alpha| = \frac{S-1}{S+1} = \frac{(E_{max}) - E_{min}}{(E_{max}) + |E_{min}|} \quad (5)$$

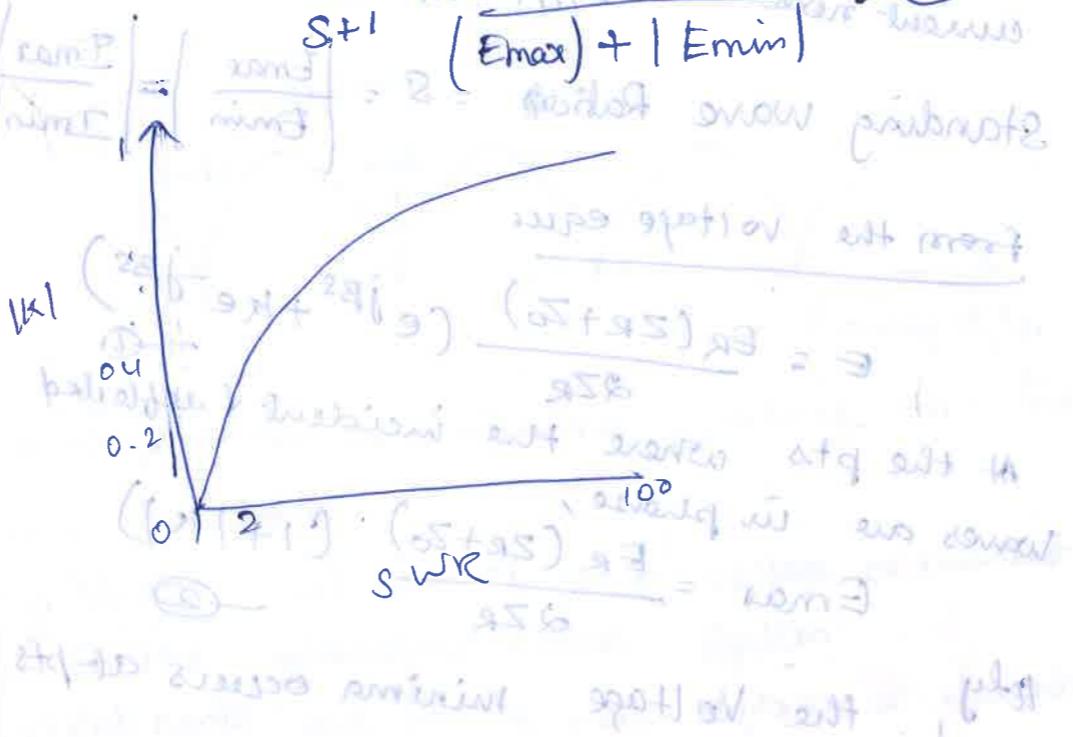

I/P Impedance of the dissipationless line

The I/P imp of a dissipationless line is,

$$E_R = E_R \cos \beta s + j I_R R_0 \sin \beta s$$

$$I = I_R \cos \beta s + j \frac{E_R}{R_0} \sin \beta s$$

$$Z_g = \frac{E_S}{I_S} = \frac{E_R \cos \beta s + j I_R R_0 \sin \beta s}{I_R \cos \beta s + j \frac{E_R}{R_0} \sin \beta s}$$

$E_R = I_R Z_R$, Therefore; \therefore by $I_R \cos \beta s$

$$Z_g = \frac{Z_R + j R_0 \tan \beta s}{1 + j \frac{Z_R}{R_0} \tan \beta s}$$

$$Z_g = R_0 \left[\frac{Z_R + j R_0 \tan \beta s}{R_0 + j Z_R \tan \beta s} \right] \quad (1)$$

- From this equ, imp is
- Imp. is complex in general
 - periodic with variation of βs , the period being π or $s = \lambda/2$.

Another form of I/P imp is

$$E_S = \frac{E_R (Z_R + R_0)}{\alpha Z_R} (e^{j \beta s} + K e^{-j \beta s})$$

$$I = \frac{IR(z_0 + Z_0)}{2Z_0} (e^{j\beta s} - k e^{-j\beta s})$$

$$Z_s = \frac{E_s}{I_s} = \frac{IR \left(\frac{(Z_0 + R_0)}{2} \right) (e^{j\beta s} + k e^{-j\beta s})}{IR \left(\frac{(Z_0 + R_0)}{2} \right) (e^{j\beta s} - k e^{-j\beta s})}$$

$$Z_s = R_0 \left[\frac{e^{j\beta s} + k e^{-j\beta s}}{e^{j\beta s} - k e^{-j\beta s}} \right]$$

$$= R_0 \left(\frac{1/k + 1/k |1/\phi - \beta s|}{1/k - 1/k |1/\phi - \beta s|} \right) \quad \text{--- (2)}$$

$\phi \rightarrow$ angle of reflection co-efficient k .


÷ by $1/\beta s$,

$$\therefore Z_s = R_0 \left(\frac{1 + 1/k |1/\phi - \beta s|}{1 - 1/k |1/\phi - \beta s|} \right) \quad \text{--- (3)}$$

* The numerator & denominator show by separate phasors.

* Adding unity to $+/-k$

$$\text{for } |k| = 0.5 \text{ or } s = 3 \angle 10^\circ$$

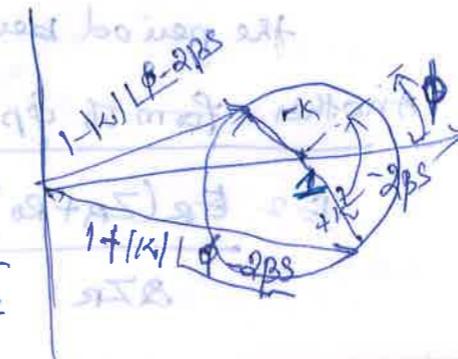

* At $s = \phi/2\beta + n\pi/4$ the numerator & denominator terms are in-phase ($n = 0, 1, 2, \dots$). At these p.t.s. - the i.p. of the line is purely resistive.
* The angle ϕ vector in terms of ϕ_{BS} , has a revolution represents ϕ terms of wavelength λ i.p. (resistive), occurring at the value ϕ_{BS} max i.p. (resistive).

$$\text{at } s = \phi/2\beta + n\pi/4, \quad R_{max} = R_0 \left(\frac{1+k}{1-k} \right) = \frac{2R_0}{s} \quad \text{--- (4)}$$

The min. i.p. resistive, occurring

$$\text{at } s = \phi/2\beta + (2n-1)\pi/4, \quad R_{min} = R_0 \left(\frac{1-k}{1+k} \right) = \frac{R_0}{s}. \quad \text{--- (5)}$$

I.p. imp. of open & short circuited line

The i.p. imp. of a dissipationless line is:


$$Z_s = R_0 \left(\frac{Z_R + j R_0 \tan \beta s}{R_0 + j Z_R \tan \beta s} \right) \quad \text{--- (6)}$$

For SC-ed line $Z_R = 0$,

$$Z_{sc} = j R_0 \tan \beta s$$

$$\text{Since } \beta = \frac{2\pi}{\lambda}, \quad Z_{sc} = j R_0 \tan \frac{2\pi s}{\lambda}. \quad \text{--- (7)}$$

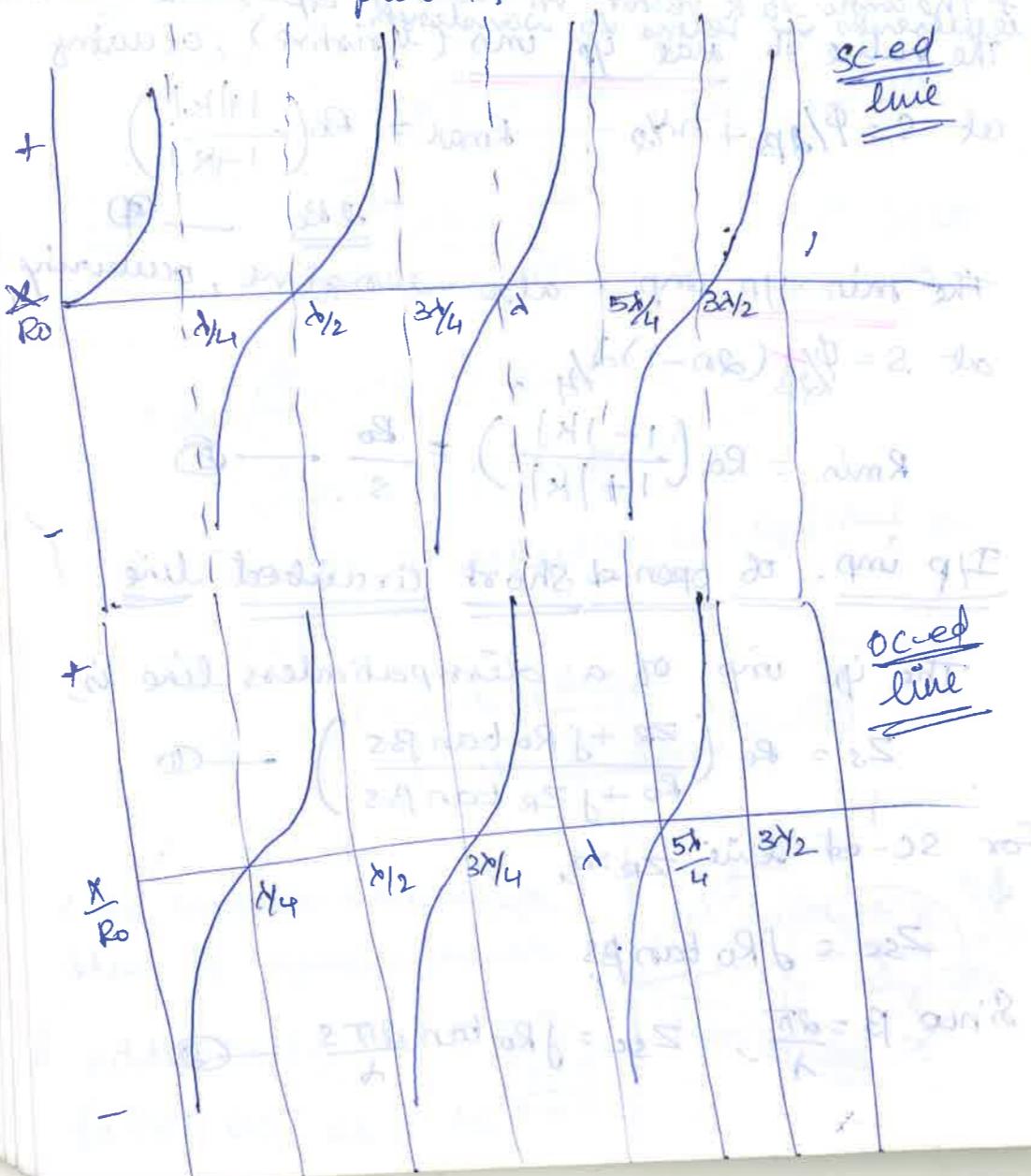The variation $\frac{Z_{oc}}{R_0} = \frac{x}{R_0}$ with length of line where x is plotted.



I_P imp for OC-ed line

From eqn ①,
 $Z_S = R_0 \left(\frac{1 + j \frac{R_0}{Z_R} \tan \beta s}{\frac{R_0}{Z_R} + j \tan \beta s} \right)$

$$Z_S = R_0 \left(\frac{1 + j \frac{R_0}{Z_R} \tan \beta s}{\frac{R_0}{Z_R} + j \tan \beta s} \right) = \frac{R_0}{j \tan \beta s}$$

For OC-ed line $Z_R = \infty$, so that, $\frac{R_0}{j \tan \beta s}$

$$Z_S = \frac{-j R_0}{\tan \beta s} = -j R_0 \cot \frac{2\pi s}{\lambda} \quad \text{--- (3)}$$

plot of $\frac{Z_{oc}}{R_0} = \frac{x}{R_0}$ as a fn. of length of line is shown in fig.

* for both cases I_P imp is pure reactance

* for 1st $\lambda/4$ wl,

* SC line act as an Inductance

* OC line act as a capacitance.

- These reactances reverse each $\lambda/4$ wl.

* I_P imp of $\lambda/4$ SC-ed \rightarrow appears as infinite reactance

* " " " " OCed \Rightarrow " " " zero "

In practical cases,

- always be a small resistance component of the $\text{V.P. imp.} \rightarrow$ indicates power loss.
- zero or ∞ infinite imp.s are never achieved.

The Quarter wave line - Imp. Matching

The expression for the V.P. imp. of a dissipationless line may be rearranged as,

$$Z_s = R_0 \left[\frac{Z_R + jR_0 \tan \beta s}{R_0 + jZ_R \tan \beta s} \right]$$
$$= R_0 \left[\frac{\frac{Z_R}{\tan(\frac{2\pi s}{\lambda})} + jR_0}{\frac{R_0}{\tan(\frac{2\pi s}{\lambda})} + jZ_R} \right]$$

if the line is made a quarter wave long

$$S = \frac{\lambda}{4}$$

$Z_s = \frac{R_0^2}{Z_R}$
ie the V.P. imp. of the line is equal to the square of R_0 of the line divided by the load impedance.

A quarter wave section of line may be thought of as a topo. to match the load imp Z_R to a source of $Z_{s'}$'s.

To obtain this, the charac. imp R_0' of the Quarter wave section of line is properly chosen according to,

$$R_0' = \sqrt{|Z_s Z_R|}$$

R_0' is matching section. ie equal to geometric mean of free source & load imp's.

① $\lambda/4$ line - Impedance Inverter

It can transform low imp. into a high imp & vice versa.


* $\lambda/4$ sc-ed line tofr-ing the zero-imp SC termination to an apparent OC, & if the OC-ed $\lambda/4$ line is tofr-ing the ~~OC~~ termination to a low value or an apparent SC.

Appln: ① $\lambda/4$ matching section is to couple a trans. line to a resistive load such as an antenna.

The $\lambda/4$ line ~~line~~ matching section then must be designed to a charac. imp R_0' , chosen that the ant. resistance R_A is tofr-ed to a value equal to the charac. imp R_0 of the trans. line.

$$R_0' = \sqrt{R_A R_0} \quad \text{--- eqn ①}$$

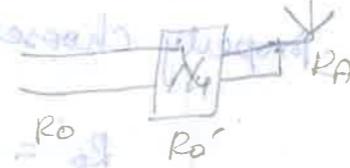R_0' → just the value required to achieve



critical coupling and max. power trfr from the trans. line to the load.

trfr. is is a single freq or NB device

The Band width may be broad by using 2 or more $\lambda/4$ sections in series.

* Also used if the load is not pure resistance.

* It should be connected b/w pt's.

corresponding to I_{max} or E_{max} .

* At which places the trans. line has resistive imp. given by $\frac{R_0}{s}$ or sR_0


∴ Matching tofr. charac. imp is,

$$R_0' = \sqrt{R_0 \cdot \frac{R_0}{s}} = R_0 \sqrt{\frac{1}{s}}$$

② Appln: 2: sc-ed $\lambda/4$ line → Insulator

* To support open wire line or the center conductor of a co-axial line.

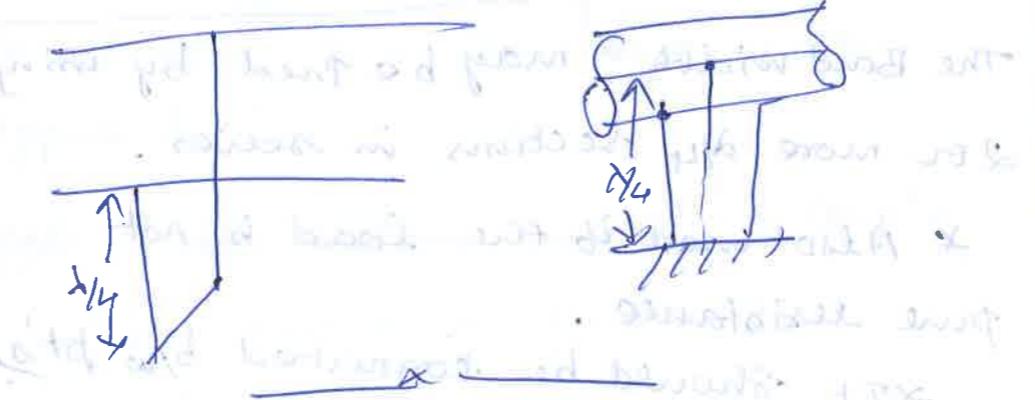* The imp. of a $\lambda/4$ shorted line
is very high → called copper insulator



$\lambda/8$ wave line

imp. of a line, when $s = \lambda/8$

$$Z_s = R_o \left[\frac{Z_R + jR_o \tan(\frac{\pi}{4})}{R_o + jZ_R \tan(\frac{\pi}{4})} \right] \quad (1)$$

line is terminated in a pure resist R_R

$$Z_s = R_o \left(\frac{R_R + jR_o}{R_o + jR_R} \right) \quad (2)$$

Numerator & deno. have identical magnitudes

$|Z_s| = R_o$
 $\lambda/8$ line used to transform any resistance to an imp.

with mag. = to R_o of the line.

The $\lambda/2$ line - Half wave line

when the length of the line having $s = \lambda/2$ is, the imp. is,

$$Z_s = R_o \left(\frac{Z_R + jR_o \tan \pi}{R_o + jZ_R \tan \pi} \right)$$

$$Z_s = Z_{R_o}$$

* $\lambda/2$ line → considered as 1 to 1 transformation.

* used to connect a load to source, where the load & source can't be made adjacent.

* A group of capacitors may be placed in $\lambda/2$ by connecting them with sections of line $n = \text{half waves in length}$.

∴ Insulators on a HF line should not be spaced at $\lambda/2$ intervals, since their effect would be cumulative, lowering the insulation resistance of the line.


Single stub impedance Matching

For greatest efficiency & delivered max. power, a HF trans. line should be operated as a smooth line or with Z_0 termination (charac imp).

- Theory - L, T, H, matching & MTS.

One way is, the use of an open or closed stub line of suitable length as a reactance shunted across the trans. line at a designated distance from the load.

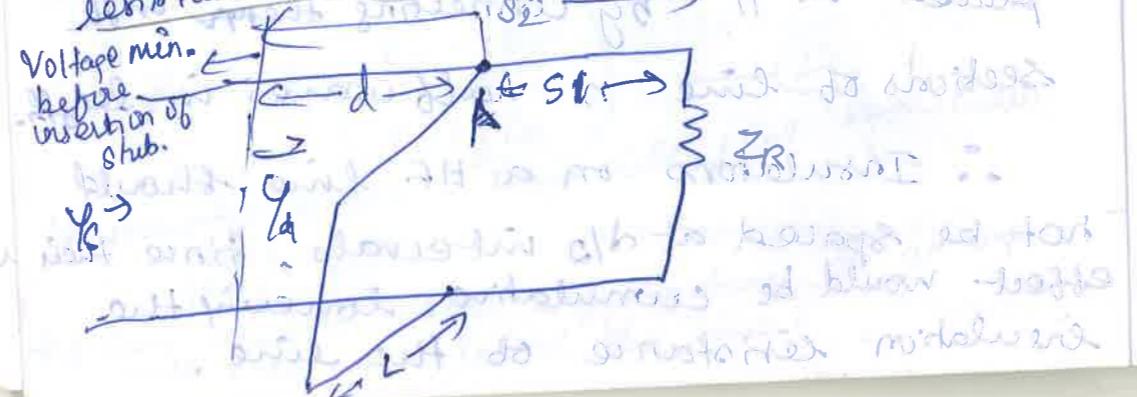* The length of line + the load to resonance with an anti-resonant resistance equal to R_0 .



* The ip conductance of a line is $\frac{1}{R_0}$ at voltage max.

* " " " at a voltage min.

→ S-SWR

. At some intermediate pt. A, the real part of the ip admittance may have an intermediate value Y_{R0} .

The ip admittance $Y_S = \frac{1}{R_0} + jB$.

$\frac{1}{R_0} \rightarrow$ conductance $B \rightarrow$ susceptance.

* After placing the conductance Y_{R0} , a short stubs line having ip susceptance B may be connected across the trans. line.

$$Y_S = \frac{1}{R_0} + jB + jB = \frac{1}{R_0}$$

The ip imp of the trans. line at pt. A. is $Z_S = R_0$

- * The line from the source to A is then terminated in R_0 , & is a smooth line
- * From A to load, reflection & standing waves occur.

* But the distance is always $<$ than a wavelength, the losses are not severe.

- * The min. nearest to the load
- * Free min. is chosen rather than V_{max} .

* The location of the stub is fixed, w.r.t. to an V_{min} , no knowledge of the load imp. is needed.

From (2) from imp. of a fr-con line

$$Z_s = R_0 \frac{1+|k|(φ-2βs)}{1-|k|(φ-2βs)} \quad (1)$$

$$Y_s = \frac{1}{R_0} \left(\frac{1-|k|(φ-2βs)}{1+|k|(φ-2βs)} \right) \quad (2)$$

$G_0 = \frac{1}{R_0}$ changing to rectangular co-ordinates gives

$$Y_s = G_0 \left[\frac{1-|k|\cos(\phi-2\beta s) + j|k|\sin(\phi-2\beta s)}{1+|k|\cos(\phi-2\beta s) + j|k|\sin(\phi-2\beta s)} \right]$$

~~$\Rightarrow Y_s = G_0 \left[\frac{(1+|k|\cos\phi - j|k|\sin\phi)(1+|k|\cos\phi + j|k|\sin\phi)}{|k|^2 + 2|k|\cos(\phi-2\beta s)} \right]$~~

~~$Y_s = G_0 \left[\frac{1-|k|^2 - 2j|k|\sin(\phi-2\beta s)}{|k|^2 + 2|k|\cos(\phi-2\beta s)} \right]$~~


Expressing the shunt conductance as a dimensionless ratio $\frac{G_s}{G_0}$ or per unit basis

$$Y_s = G_s \pm jB_s$$

$$\frac{G_s}{G_0} = \frac{1-|k|^2}{1+|k|^2 + 2|k|\cos(\phi-2\beta s)} \quad (3)$$

~~$\Rightarrow Y_s = \frac{-2j|k|\sin(\phi-2\beta s)}{1+|k|^2 + 2|k|\cos(\phi-2\beta s)} \quad (4)$~~

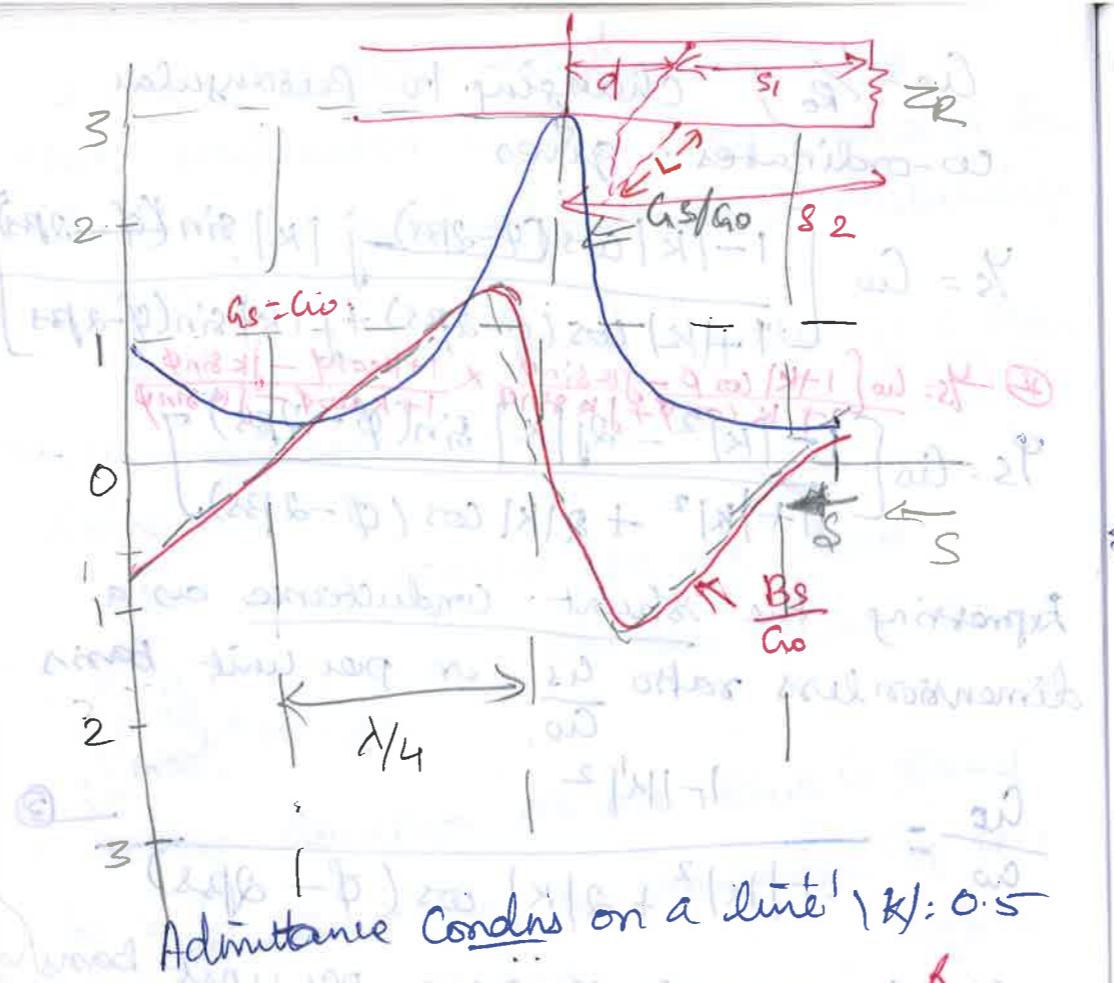~~$\Rightarrow G_0 \left[\frac{1+k\cos\phi - jk\sin\phi - k\cos^2\phi - jk^2\cos^2\phi + jk^2\sin^2\phi}{1+k\cos\phi - jk\sin\phi + k^2\cos^2\phi + k\cos\phi - jk^2\sin^2\phi - jk^2\sin\phi} \right]$~~



Admittance Condns on a line $|k|: 0.5$

$$\text{From } ④, \phi - 2Bs_2 = -\pi$$

$$s_2 = \frac{\phi + \pi}{2B} \quad ⑤$$

$$\text{At this distance from the load,}$$

$$G(s) = \frac{G_0}{1 - |k|^2} = \frac{1 + k}{1 - k} + S \quad ⑥$$

$$G_0 = \frac{1 - |k|^2}{1 + |k|^2 - 2k} = \frac{1 + k}{1 - k} \quad ⑦$$

$R_s = \frac{R_0}{s}$, The pt ob. Max. $\frac{G_s}{G_0}$ is recognized as a pt ob min. voltage at a distance s_2 from the load. at $G_s = G_0$, at which the stub is to be connected, the value of $\frac{G_s}{G_0} = 1$,

$$1 = \frac{1 - |k|^2}{1 + |k|^2 + 2k \cos(\phi - 2Bs_1)}.$$

$$\text{from } ⑥, \cos(\phi - 2Bs_1) = -k, \cos^{-1}(-k) = -\pi + \cos^{-1}|k|$$

$$s_1 = \frac{\phi + \pi - \cos^{-1}|k|}{2B} \quad ⑧$$

Hence the distance d from the V_{min} to pt ob is,

$$d = s_2 - s_1, \text{ from } ⑤ \& ⑧, d = \frac{\cos^{-1}|k|}{2B}.$$

$$d = \cos^{-1}\left(\frac{s-1}{s+1}\right)\lambda/4 \quad ⑨$$

$$2B = \frac{2 \times 2\pi}{\lambda} = \frac{4\pi}{\lambda}$$

$$\text{from } ⑥ \& ⑨, B_s = G_0 \left[\frac{-2|k| \sin(\pi + \cos^{-1}|k|)}{1 + |k|^2 + 2|k| \cos(\pi + \cos^{-1}|k|)} \right]$$

for an angle whose cosine is $|k|$, sine is $\sqrt{1 - k^2}$

$$\therefore B_s = G_0 \left(\frac{2|k| \sqrt{1 - |k|^2}}{1 - |k|^2} \right) \quad ⑩$$

The susceptance of the stub required to cancel the line susceptance of B_s must be -ve

The circle diagram for the dissipationless

- Solves the imp. equis line

The GP expr. of a dissipationless line may be written on per unit basis, is,

$$\frac{Z_s}{R_0} = \frac{14|k| \sqrt{\varphi - 2\beta^2}}{|-|k|| \sqrt{\varphi - 2\beta^2}} \quad \text{--- (1)}$$

\hookrightarrow normalized source impedance - applicable
 \hookrightarrow normalized source impedance may be write,
 to all lines, Z/Z_0 is complex.

$$\frac{Z_s}{R_0} = \frac{r_a + jx_a}{1+2} \quad \begin{matrix} \text{reactance} \\ \downarrow \text{resistance} \end{matrix}$$

$$x_a + jx_b = \frac{1 + |k|}{|1 + |k||} e^{-j\phi_B} \quad \text{--- (3)}$$

1) Viscosity measured live quality
2) Viscosity measured live quality
3) Viscosity measured live quality

SWR S. $\frac{Z_o}{Z_L} = \frac{V_o}{V_L}$ \Rightarrow $Z_L = Z_o \cdot \frac{V_L}{V_o}$

Z_L in terms of V_o \Rightarrow $V_o = Z_o \cdot \frac{V_L}{Z_o}$

$\boxed{K = \frac{V_o}{V_L}}$

$$(r_a + 1 + jx_a) \cdot \left(\frac{S-1}{S+1} \right) \cancel{\phi - \alpha \beta s} = r_a - 1 + jx_a \quad \text{--- ④}$$

$$z_a = z_a |k| \left(\underline{q - 2\beta s} + j \underline{x_a} - j \underline{x_a} |k| \right) \underline{\left(q - 2\beta s - i - |k| \right)} \underline{\left(q - 2\beta s \right)} =$$

$$n_a - 1 + jx_a = n_a |k| \left(\phi - 2\beta s + jx_a/k \right) \phi - 2\beta s +$$

$$r_a - 1 + jx_a = (r_a + 1 + jx_a) | k \rangle \langle \phi - \alpha | B_S$$

Equating the squares of the magnitudes after clearing of fractions,

$$ra^2 - ra \left(\frac{s^2 + 1}{s - 2} \right) + 2a^2 = 1$$

$$\frac{C_{S_1}}{C_{10}} = 1, \quad I = \frac{1 - |K|^2}{1 + |K|^2 + 2|K|\cos(\phi - 2\beta S_1)}$$

$$\cos(\phi - 2\beta s_1) = -|k| \rightarrow (1-|k|^2)$$

$$\cos^{-1}(-1/k) = -\pi + \cos^{-1}(1/k)$$

By adding ~~the~~ term to complete the square,

$$\frac{x^2 - 2x + 1}{2s} + \left(\frac{s^2+1}{2s}\right)^2 + x_0^2 = \left(\frac{s^2+1}{2s}\right)^2$$

$$\left[\frac{x^2 - 2x + 1}{2s} + \left(\frac{s^2+1}{2s}\right)^2\right]^2 + x_0^2 = \left(\frac{s^2-1}{2s}\right)^2 \quad \text{--- (5)}$$

i.e. (5) is in the form of

$$(x - c)^2 + y^2 = r^2$$

r - radius c - center


An actual circle will have a radius, so

$$r = \frac{s^2-1}{25} = \frac{s-1/s}{2} \quad \text{--- (6)}$$

a shift of the center of the circle on the x -axis is s (abscissa)

$$c = \frac{s^2+1}{25} = \frac{s+1/s}{2} \quad \text{--- (7)}$$

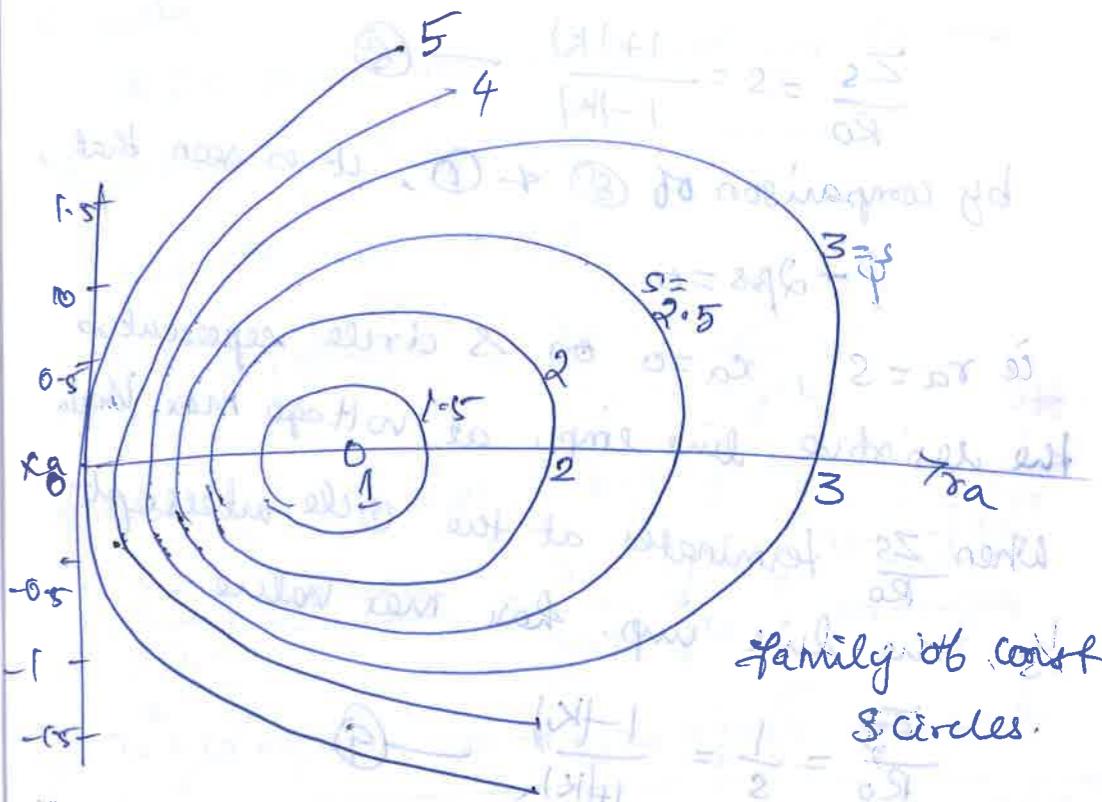The family of circles may be drawn for successive values of s .



The minimum value for s is unity.
max. value for s is infinity.

$s \rightarrow$ radius is $1/s$
 \rightarrow centers move to the right given limit
 $s \rightarrow \infty$ the circle becomes the x -axis

When $\frac{Z_s}{R_0}$ lies on the abscissa, with magnitude S , the line impedance has max value.

$$\frac{Z_s}{R_0} = S = \frac{1+jk}{1-jk} \quad \text{--- (8)}$$

by comparison of (8) + (1), it is seen that,

$$\phi - 2\beta s = 0$$

i.e. $r_a = S$, $x_a = 0$ on S circle represents the resistive line imp. at voltage max. When

When $\frac{Z_s}{R_0}$ terminates at the O cle intercept, βs , the line imp. has max value.

$$\frac{Z_s}{R_0} = \frac{1}{S} = \frac{1+jk}{1+jk} \quad \text{--- (9)}$$

i.e. for resistive load $\phi = 0$.

$$\beta s = \frac{\pi}{2}$$

Thus moving through $\beta s = \frac{\pi}{2}$ radians back along the line has caused the tip of the imp vector to travel over a distance on the

O cle π radians. Hence it is seen advisable to place a βs scale on the S circle.

* βs scale goes clockwise, or in the direction of π in negative angles.

describe the eqn (1),

$$\left(\frac{S-1}{S+1} \right) \underbrace{\phi - 2\beta s} = \frac{r_a - 1 + jx_a}{r_a + 1 + jx_a}$$

rationalizing the right side gives,

$$\left(\frac{S-1}{S+1} \right) \underbrace{\phi - 2\beta s} = \frac{r_a - 1 + jx_a}{r_a + 1 + jx_a} \times \frac{r_a + 1 - jx_a}{r_a + 1 - jx_a}$$

$$= \frac{r_a^2 + r_a - jx_a r_a - r_a - 1 + jx_a + jx_a r_a + jx_a + x_a^2}{r_a^2 + r_a - jx_a r_a + r_a + 1 - jx_a + jx_a r_a + jx_a + x_a^2}$$

$$= \frac{x_a^2 - 1 + 2jx_a + x_a^2}{2x_a^2 + 2r_a + 1 + x_a^2} = \frac{r_a^2 - 1 + x_a^2 + jx_a}{(r_a + 1)^2 + x_a^2}$$

The angle ϕ may be made zero in order that the βs scale may start at 0° on the abscissa. (10)

* Equating the tangents of the angles in equ ⑩,

$$\tan(-2\beta s) = \frac{2x_a}{x_a^2 - 1 + x_a^2} \quad \text{--- ⑪}$$

sign? $(x_a^2 - 1 + x_a^2)(\tan 2\beta s) = 2x_a$

$$(x_a^2 - 1 + x_a^2) + \frac{2x_a}{\tan 2\beta s} = 0 \Rightarrow x_a^2 + x_a^2 + 2x_a = \frac{\tan 2\beta s}{\tan 2\beta s}$$

After the square, this may be written as,

$$x_a^2 + \left(x_a + \frac{1}{\tan 2\beta s}\right)^2 = 1 + \frac{1}{\tan^2 2\beta s} = \frac{1}{\sin^2 2\beta s}$$

$$\left(x_a^2 + \frac{2x_a}{\tan 2\beta s} + \frac{1}{\tan^2 2\beta s}\right) \quad \text{--- ⑫}$$


Lines of equal βs value are then seen to be circles of radius, $= \frac{1}{\sin 2\beta s}$ --- ⑬

with a shift of center downward on the x_a axis (ordinate) $= \frac{x_a}{\tan 2\beta s}$ --- ⑭

$$1 + \frac{\cos^2 2\beta s}{\sin^2 2\beta s} = 1 + \frac{1 - \sin^2 2\beta s}{\sin^2 2\beta s} = 1 + \frac{1}{\sin^2 2\beta s} - \frac{\sin^2 2\beta s}{\sin^2 2\beta s} = \frac{1}{\sin^2 2\beta s}$$

A family of such circles is shown in fig.

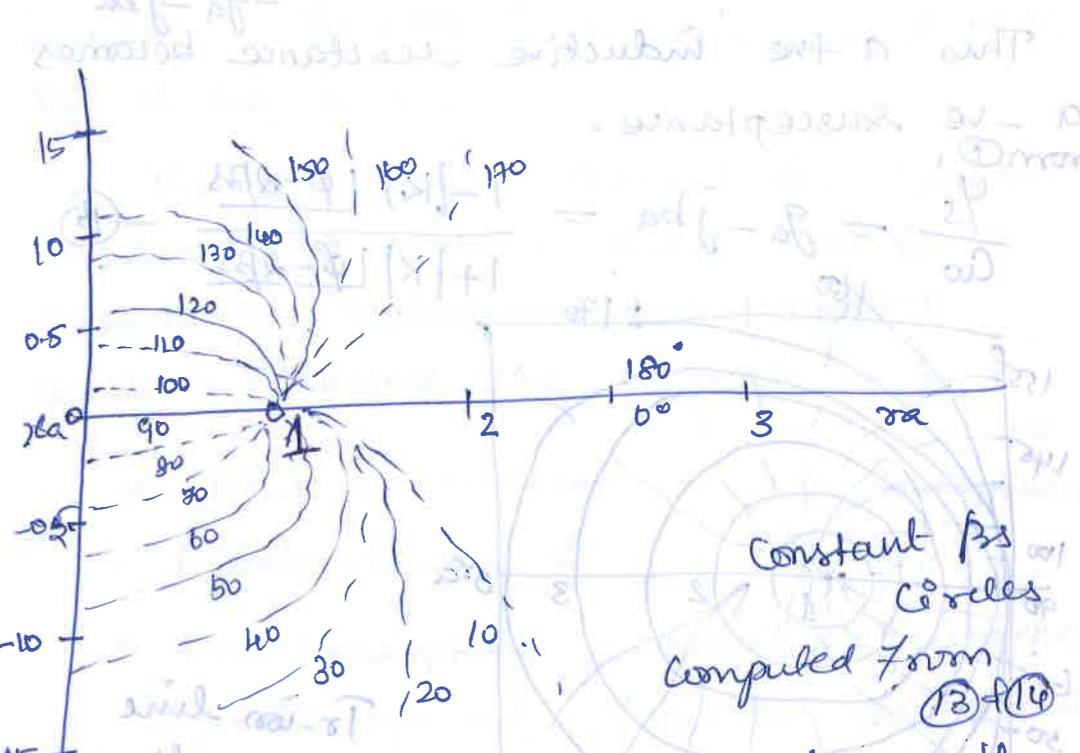All the ps circle pass through the point $x_a = 1, z_a = 0$



Superposition of the βs circles on the s circles provides a scale of βs angles & results in the below circle diagram.

* computed from ⑬ & ⑭ in terms of $2\beta s$.


Per Unit admittance may be written as,

$$\frac{Y_s}{C_0} = \frac{1}{x_a + jx_a} = \frac{r_a - jx_a}{(r_a + jx_a)(r_a - jx_a)}$$

$$= \frac{r_a}{r_a^2 + x_a^2} - j \frac{x_a}{r_a^2 + x_a^2} = g_a - j b_a \quad (15)$$

Thus at the inductive reactance becomes
a -ve susceptance.
from (1),

$$\frac{Y_s}{C_0} = g_a - j b_a = \frac{1 - |K| L \phi - 2 Ps}{1 + |K| L \phi - 2 Ps} \quad (16)$$

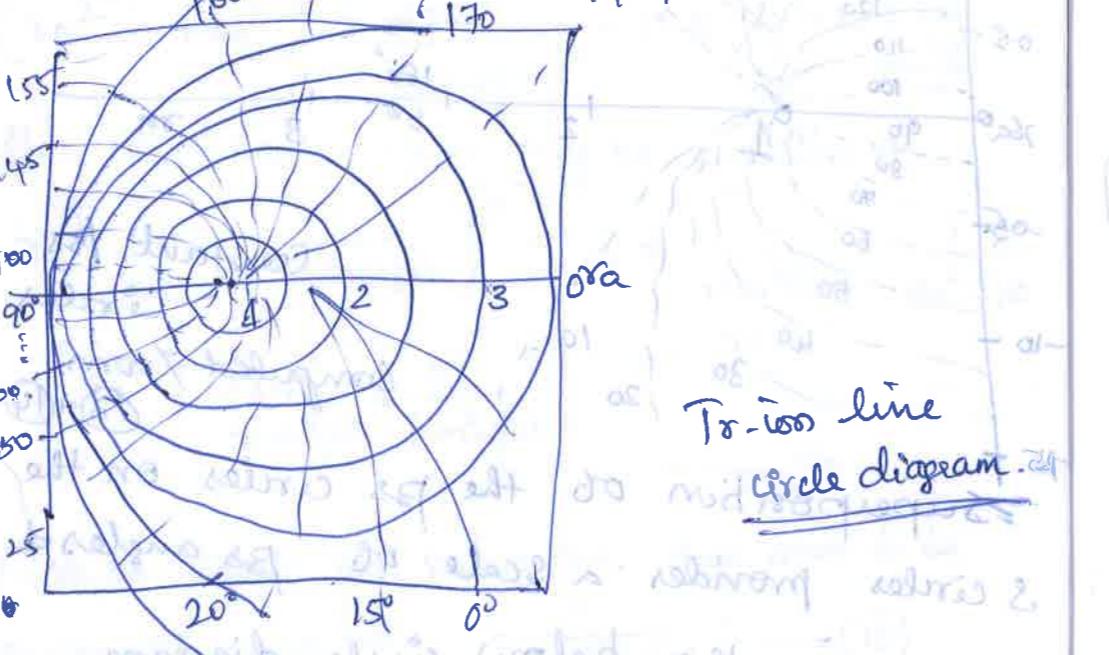

Replacing r_a by g_a

$$r_a \rightarrow -b_a \quad |K| \rightarrow -|K| \quad \text{sub. in (5) we have,}$$

$$\left[g_a - \left(\frac{s^2 - 1}{2s} \right) \right]^2 + b_a^2 = \left(\frac{s^2 - 1}{2s} \right)^2 \quad (17)$$

which is exactly similar to eqn (5).
The substitution of $-b_a$ for r_a need not be made, since eqn (5) is independent of the sign of the b_a term.

The circle diagram obtained for impedance, resistance and reactance can be used for admittance, conductance & susceptance merely by changing the ray scale to g_a .

* Inductive reactance is $-b_a$ -ve susceptance
* plots downward.

* the susceptance - capacitive reactance
- plots upward from the axis of reactance

From the above data, we can see that the resistance and inductance are positive and

the susceptance is negative, therefore

$$(1) \rightarrow \frac{2V}{1 - 2} \quad R = \frac{1}{2} \Omega$$

and the current is directed out of the coil

and the voltage across the coil is directed across the coil in the clockwise direction

and the voltage across the coil is directed across the coil in the clockwise direction

⇒ The susceptance of a sc-ed stub is,

$$B_{sc} = -G_0 \cot \beta L$$

where, $L \rightarrow$ length of the sc-ed stub.

If stub & line have equal G_0 , then,

$$\frac{G_0}{\tan \beta L} = G_0 \left(\frac{2|k| \sqrt{1-|k|^2}}{2|k|\sqrt{1-|k|^2}} \right)$$

$$\tan \beta L = \frac{1-|k|^2}{2|k|\sqrt{1-|k|^2}} \quad (\text{eqn 10})$$

$$L = \frac{\lambda}{2\pi} \tan^{-1} \left(\frac{1-|k|^2}{2|k|\sqrt{1-|k|^2}} \right) \quad (\text{eqn 10})$$

By the use of SWR existing before connection of the stub, this eqn. may be conveniently expressed as,

$$L = \frac{\lambda}{2\pi} \tan^{-1} \frac{\sqrt{s}}{s-1} \quad (\text{eqn 11})$$

This is the length of sc-ed stub to be placed d meters toward the load from a point at which a Vmin existed before the

attachment of the stub.

Also possible to place the stub d meters toward the source from the voltage min.

The sign of the reactance is reversed on that side w.r.t. the sign of the location nearer the load.

The stub length L' should be,

$$L' = d\gamma_Q - L \quad \text{for sc-ed stub}$$

(12)

The Smith Circle diagram

The Smith diagram is obtained from a transformation of equation (10).

$$\left(\frac{s-1}{s+1}\right) \underline{|\phi - 2\beta s|} = |K| \underline{|\phi + \alpha s|}$$

$$= \frac{r_a^2 - 1 + x_a^2 + j2x_a}{(r_a+1)^2 + x_a^2}$$

By introducing a new variable $U+jV$.

$$U+jV = \frac{r_a^2 - 1 + x_a^2}{(r_a+1)^2 + x_a^2} + j \frac{2x_a}{(r_a+1)^2 + x_a^2}$$

Equating the real and Imaginaries, we have,

$$U = \frac{r_a^2 - 1 + x_a^2}{(r_a+1)^2 + x_a^2} \quad \text{--- (1)}$$

$$V = \frac{2x_a}{(r_a+1)^2 + x_a^2} \quad \text{--- (2)}$$

$$\Rightarrow \frac{Z_s}{R_0} = r_a + jx_a = \frac{1+|K| \underline{|\phi - 2\beta s|}}{1-|K| \underline{|\phi - 2\beta s|}} \quad \text{--- (1)}$$

$$\text{say } |K| \underline{|\phi - 2\beta s|} = U+jV$$

$$\frac{Z_s}{R_0} = r_a + jx_a = \frac{1+(U+jV)}{1-(U+jV)} = \frac{(1+U)+jV}{(1-U)-jV} \quad \text{--- (2)}$$

on rationalizing the above equation,

$$r_a + jx_a = \frac{(1+U)+jV}{(1-U)-jV} \times \frac{(1-U)+jV}{(1-U)+jV}$$

$$= \frac{(1+U)(1-U) + jV + jx_a + j(UV - V^2)}{(1-U)^2 + V^2}$$

$$= \frac{(1-U^2-V^2) + j(2V)}{(1-U)^2 + V^2}$$

$$= \frac{(1-U^2-V^2)}{(1-U)^2 + V^2} + j \frac{2V}{(1-U)^2 + V^2} \quad \text{--- (3)}$$

$$r_a = \frac{1-U^2-V^2}{(1-U)^2 + V^2} \quad \text{--- (4)}$$

$$x_a = \frac{2V}{(1-U)^2 + V^2} \quad \text{--- (5)}$$

Constant resistance circle

From eqn ④,

$$x_a [(1-u)^2 + v^2] = 1 - u^2 - v^2$$

$$x_a [(1-2u+u^2) + v^2] = 1 - u^2 - v^2$$

$$\therefore x_a [1 - 2u + u^2 + v^2] = 1 - u^2 - v^2$$

$$x_a - 2u x_a + u^2 x_a + v^2 x_a \neq \sqrt{1} = 1.$$

$$u^2 [x_a + 1] - 2u x_a + v^2 (x_a + 1) = 1 - x_a$$

÷ by $1 + x_a$,

$$u^2 - 2u \left(\frac{x_a}{1+x_a} \right) + v^2 = \frac{1-x_a}{1+x_a}$$

To complete the square by adding $\left(\frac{x_a}{1+x_a} \right)^2$

on both sides, we have,

$$u^2 - 2u \left(\frac{x_a}{1+x_a} \right) + \left(\frac{x_a}{1+x_a} \right)^2 + v^2 = \left(\frac{-x_a}{1+x_a} \right)^2 + \left(\frac{x_a}{1+x_a} \right)^2$$

$$\left(u - \frac{x_a}{1+x_a} \right)^2 + v^2 = \frac{(1+x_a)(x_a)}{(1+x_a)^2} + x_a^2 = \frac{1}{(1+x_a)^2}$$


$$\left(u - \frac{x_a}{1+x_a} \right)^2 + v^2 = \frac{1}{(1+x_a)^2} \quad \text{--- ⑥}$$

i.e. in the form of $(x-c)^2 + y^2 = r^2$

∴ Circle of radius $r = \left(\frac{1}{1+x_a} \right)$

center = $\left(\frac{x_a}{1+x_a}, 0 \right)$

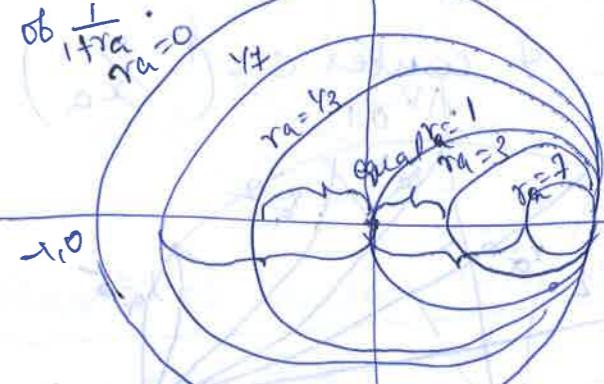const x_a circles having centers on the V axis at $\frac{x_a}{1+x_a}$ and radii of $\frac{1}{1+x_a}$.



constant x_a circles
resistance of

Constant reactance circles

From eqn ⑤,

$$x_a = \frac{2v}{(1-u)^2 + v^2} \quad \text{--- ⑤}$$

$$x_a [(1-u)^2 + v^2] = 2v$$

$$x_a [1 - 2u + u^2 + v^2] - 2v = 0.$$

$$\therefore \text{by } x_a \quad 1 - 2u + u^2 + v^2 - \frac{2v}{x_a} = 0$$

$$(u-1)^2 + v^2 - \frac{2v}{x_a} = 0 \quad \text{--- ⑦}$$


adding $\frac{1}{x_a^2}$ on both sides,

$$(u-1)^2 + v^2 - 2v + \frac{1}{x_a^2} = \frac{1}{x_a^2}$$


$$(u-1)^2 + \left(v - \frac{1}{x_a}\right)^2 = \frac{1}{x_a^2} \quad \text{--- (7)}$$

eqn (7) represents a family of circles

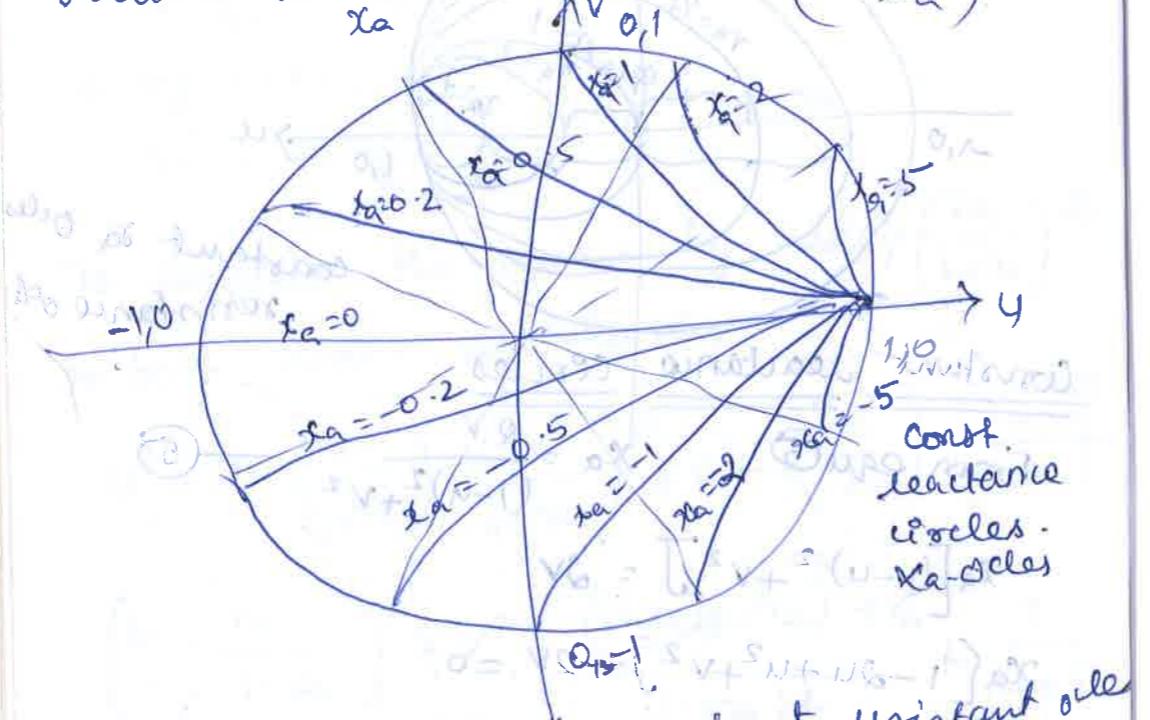radius $r = \frac{1}{x_a}$ & center $c = (1, \frac{1}{x_a})$



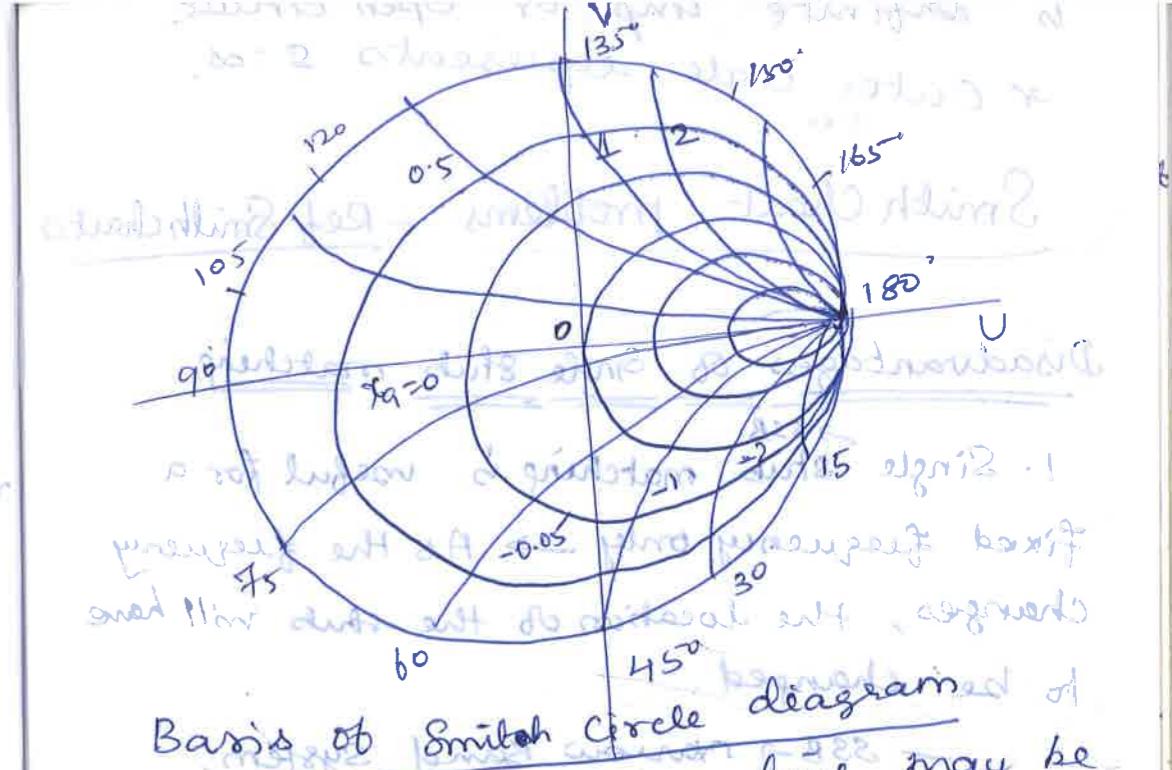* The superposition of constant resistance circles and constant reactance circles forms the Smith chart.



- * The imp. of a line may be read at any point on the appropriate SWR circle.
- * The point at the center of the SWR circle is the center of the chart represents the impedance characteristics if it is terminated in its source of signal.
- * The pt. at extreme left of Ra axis is zero imp or SC.
- * The pt. at extreme rt. of Ra axis is

is infinite imp or open circuit.
* outer circle represents $\sigma = \infty$.

Smith Chart - problems - Ref Smithcharts

Disadvantages of Single stub matching

1. Single ^{→ SSB} stub matching is useful for a fixed frequency only \rightarrow As the frequency changes, the location of the stub will have to be changed.
— SSB \rightarrow narrow band system.
2. for final adjustment, the stub has to be moved along the line slightly.
This is possible only in open wire lines and \therefore on co-axial lines, SSB may become inaccurate in practice.
though it reduces the reflection losses to a considerable extent.

Intertwined
- various attenuated contact
- regions with σ - characteristics with $\sigma \neq \infty$
- load factors have elements beyond
- objective result of design of transmission lines
- no always to minimize loss in each
section so losses, equal with load
attenuation at maximum \rightarrow attenuates
maximally outside \rightarrow load
impedance balanced

Unit-II

Network Components

Filter ~~fundamentals~~ - filter design -
 Lumped elements and distributed
 element approach to filter design -
 Design of Attenuators & equalizers -
 Lattice type, concept of inverse
 networks - Transients in transmission
 lines - Lattice diagram.
 Numerical examples.

Filters

* Resonant circuit that will select
 narrow bands of frequencies and reject
 the other frequencies.

i.e. freely pass desired bands &
 rejects & almost totally suppress
 other band of frequencies.

Such reactive N/w's called filters
Ideal filter: would pass all freq's
 in a given band without reduction
 in magnitude and totally suppress
 all other frequencies.

Nepers: The ratio of o/p voltage
 or o/p voltage & current is

$$\frac{V_1}{V_2} = \frac{I_1}{I_2} = e^{\frac{N}{2}}$$

$$\ln \frac{V_1}{V_2} = N$$

The unit of N has been given the name neper, & is defined as,

$$N \text{ nepers} = \ln \frac{V_1}{V_2} = \ln \frac{I_1}{I_2}$$

Two voltages or currents differ by one neper when one of them is e^N times as large as the other.

Also be expressed as,

$$\frac{P_1}{P_2} = e^{2N}$$

The no. of nepers represents a convenient measure of the power loss or gain of a given N/w.

log \rightarrow log with base 10.
logarithms to the base 10,
naming the unit of the bel

$$\text{no. of bels} = \log \frac{P_1}{P_2}$$

It is convenient that a unit $1/10^{\text{th}}$ called decibels abbreviated "dB"

$$dB = 10 \log \frac{P_1}{P_2}$$

for the case of equal imp in op & op circuits,

$$dB = 20 \log \frac{I_1}{I_2} = 20 \log \frac{V_1}{V_2}$$

Equation with power ratios,

$$e^{2N} = 10^{dB/10}$$

Taking log on both sides,


$$8.686 N = dB$$

$$1 \text{ neper} = 8.686 \text{ dB}$$

i.e. the relationship b/w nepers & decibels

Characteristics impedance of symmetrical N/w


Symmetrical N/w

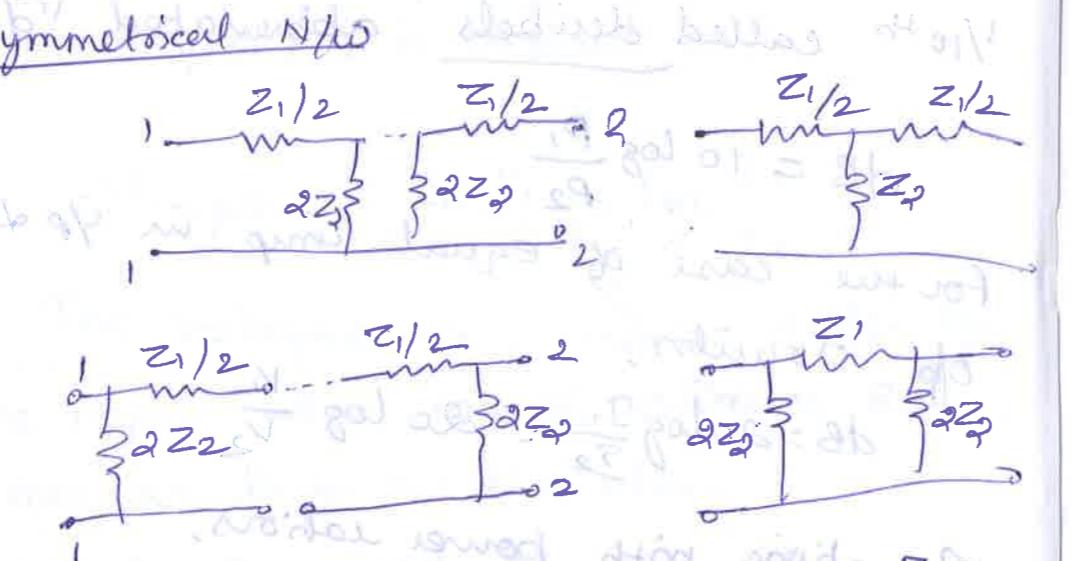

- * when $z_1 = z_2$ or 2 series arms of a T N/w are equal or the shunt arms of a π N/w are equal the N/w is symmetrical.
- * A series connection of several T or π N/w's are called "ladder N/w's"

* A symmetrical N/w is terminated in z_0 , if z_p imp. is also z_0 , the impedance transformation ratio is unity. The value of z_0 for a symmetrical N/w can be easily determined.

For T N/w: Terminated in an imp z_0 ,

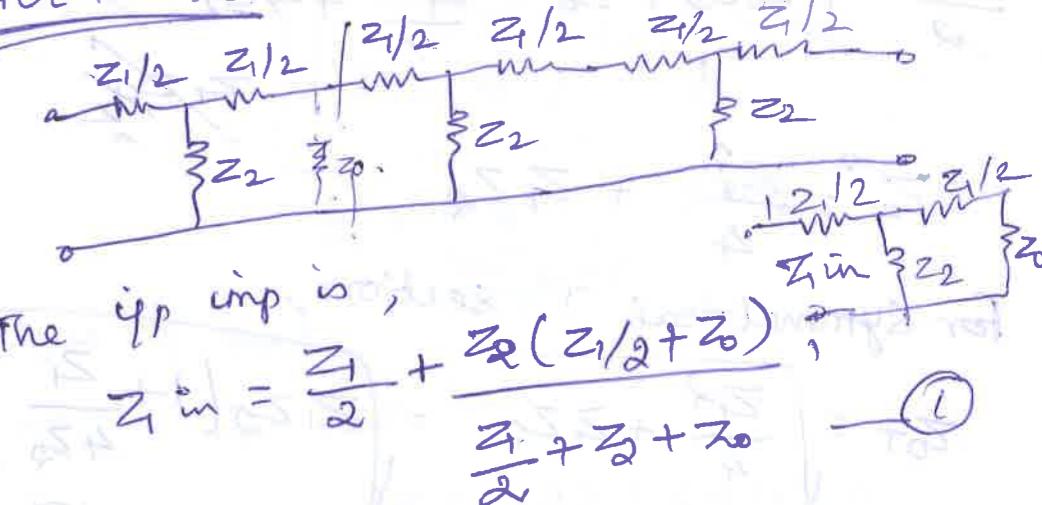

The z_p imp is,

$$z_{1m} = \frac{z_1}{2} + \frac{z_2(z_1/2 + z_0)}{z_1/2 + z_2 + z_0} \quad (1)$$

z_p is equal to z_0 ,

$$z_0 = \frac{(z_2 z_1) + z_0 z_2}{z_1 + z_2 + z_0} + \frac{z_1}{z_2}$$

$$= \frac{z_1^2 + z_1 z_2 + z_0 z_1 + z_1 z_2 + z_0 z_2}{z_1/2 + z_2 + z_0}$$

$$= \frac{z_1^2 + z_1 z_2 + z_0 z_2 + (z_1 z_2)}{z_1/2 + z_2 + z_0}$$

$$= \frac{z_1^2/4 + z_1 z_2 + z_0 z_2 + (z_1 z_2)}{z_1/2 + z_2 + z_0}$$

$$= \frac{z_1^2/4 + z_1 z_2 + z_0 z_2 + (z_1 z_2)}{z_1/2 + z_2 + z_0}$$

$$\frac{z_0 z_1}{2} + z_0 z_2 + z_0^2 = \frac{z_1^2}{4} + z_1 z_2 + z_2 z_0 + z_1 z_2$$


$$z_0^2 = \frac{z_1^2}{4} + z_1 z_2.$$

for symmetrical 'T' section,


$$z_{OT} = \sqrt{\frac{z_1^2}{4} + z_1 z_2} = \sqrt{z_1 z_2 \left(1 + \frac{1}{4z_2}\right)} \quad \textcircled{2}$$

z_{OT} \rightarrow charac. imp for 'T' N/W.

try for 'II' matching N/W

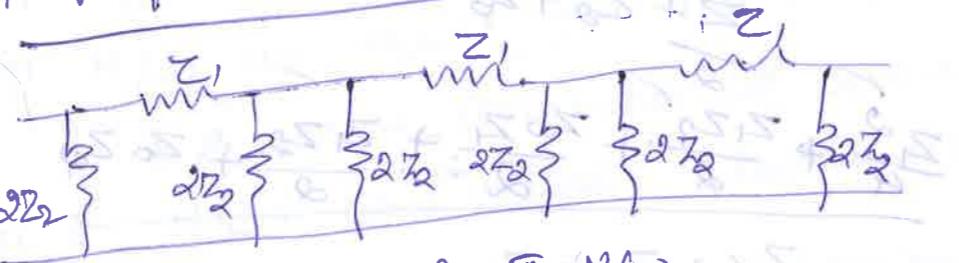

Consider a single II N/W

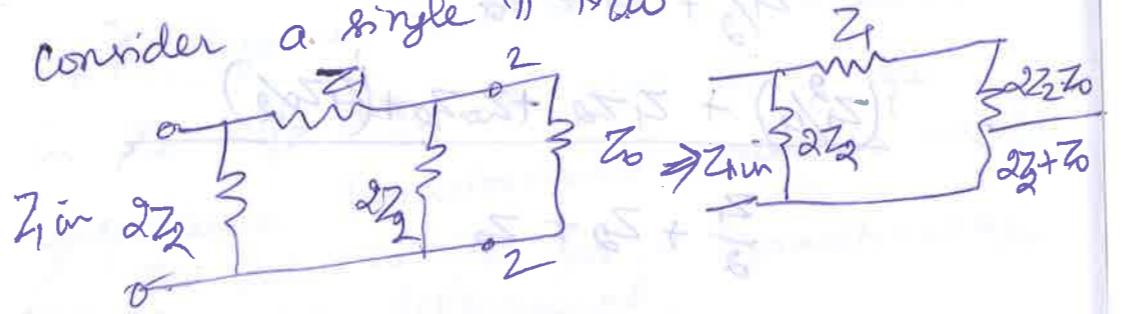

$$Z_{in} = \left[\left(\frac{2z_2 z_0}{2z_2 + z_0} \right) + z_1 \right] 2z_2$$

$$z_1 + \frac{2z_2 z_0}{2z_2 + z_0} + 2z_2$$

Requiring that,

$$Z_{in} = z_0 \text{ leads to}$$

$$Z_{OT} = z_0 = \frac{4z_1 z_2^2 + 2z_1 z_2 z_0 + 4z_0^2 z_0}{2z_1 z_2 + z_1 z_0 + 2z_2 z_0 + 4z_2^2 + 2z_0 z_2}$$

$$4z_1 z_2^2 + 2z_1 z_2 z_0 + 4z_0^2 z_0 = 2z_0 z_1 z_2 + z_1 z_0^2 + 2z_2 z_0^2 \\ + 4z_0 z_2^2 + 2z_0^2 z_2$$


$$4z_1 z_2^2 = z_0^2 + 4z_0^2 z_2$$

$$z_0^2 [z_1 + 4z_2] = 4z_1 z_2^2$$

$$\frac{z_0^2}{z_0^2} = \frac{4z_1 z_2^2}{z_1 + 4z_2} = \left(\frac{z_1 z_2}{\frac{z_1}{4z_2} + 1} \right)$$

$$Z_{0\pi} = \sqrt{\frac{Z_1 Z_2}{1 + Z_1/4Z_2}} \quad \text{with } \quad ③$$

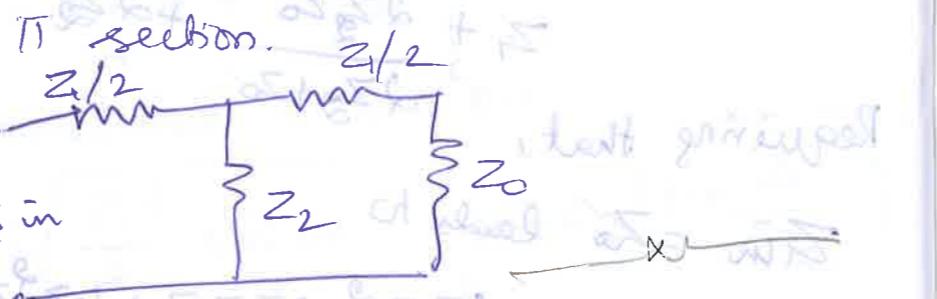$Z_{0\pi}$ → char. imp. of the symmetric π section.



$$Z_{1,OC} = Z_{OC} = \frac{Z_1}{2} + Z_2$$

$$Z_{SC} = Z_{SC} = \frac{Z_1}{2} + \frac{Z_1 Z_2 / 2}{Z_1 + Z_2}$$

$$Z_{OC} \cdot Z_{SC} = \frac{Z_1^2}{4} + \frac{Z_1^2 Z_2}{4}$$

$$\frac{Z_1^2}{4} + \frac{Z_1^2 Z_2}{4} = \frac{Z_1^2}{4} \cdot 1.5$$

$$\frac{Z_1^2}{4} \cdot 1.5 = [0.25 + 0.75] Z_1$$

$$\frac{Z_1^2}{4} \cdot 1.5 = Z_1$$

$$\left(\frac{Z_1}{2} \right)^2 \cdot 1.5 = Z_1$$

disadvantages of cascade operation
to other test to easier shadowing effect
downstream having a lot to do with it
of shadowing is not so harmful over long
distances & all depends on θ
 $\theta = \frac{\pi}{2}$
 $\theta = \frac{\pi}{4}$
 $\theta = \frac{\pi}{3}$
 $\theta = \frac{\pi}{6}$
 $\theta = \frac{\pi}{12}$
 $\theta = \frac{\pi}{24}$
 $\theta = \frac{\pi}{48}$
 $\theta = \frac{\pi}{96}$
 $\theta = \frac{\pi}{192}$
 $\theta = \frac{\pi}{384}$
 $\theta = \frac{\pi}{768}$
 $\theta = \frac{\pi}{1536}$
 $\theta = \frac{\pi}{3072}$
 $\theta = \frac{\pi}{6144}$
 $\theta = \frac{\pi}{12288}$
 $\theta = \frac{\pi}{24576}$
 $\theta = \frac{\pi}{49152}$
 $\theta = \frac{\pi}{98304}$
 $\theta = \frac{\pi}{196608}$
 $\theta = \frac{\pi}{393216}$
 $\theta = \frac{\pi}{786432}$
 $\theta = \frac{\pi}{1572864}$
 $\theta = \frac{\pi}{3145728}$
 $\theta = \frac{\pi}{6291456}$
 $\theta = \frac{\pi}{12582912}$
 $\theta = \frac{\pi}{25165824}$
 $\theta = \frac{\pi}{50331648}$
 $\theta = \frac{\pi}{100663296}$
 $\theta = \frac{\pi}{201326592}$
 $\theta = \frac{\pi}{402653184}$
 $\theta = \frac{\pi}{805306368}$
 $\theta = \frac{\pi}{1610612736}$
 $\theta = \frac{\pi}{3221225472}$
 $\theta = \frac{\pi}{6442450944}$
 $\theta = \frac{\pi}{12884901888}$
 $\theta = \frac{\pi}{25769803776}$
 $\theta = \frac{\pi}{51539607552}$
 $\theta = \frac{\pi}{103079215104}$
 $\theta = \frac{\pi}{206158430208}$
 $\theta = \frac{\pi}{412316860416}$
 $\theta = \frac{\pi}{824633720832}$
 $\theta = \frac{\pi}{1649267441664}$
 $\theta = \frac{\pi}{3298534883328}$
 $\theta = \frac{\pi}{6597069766656}$
 $\theta = \frac{\pi}{13194139533216}$
 $\theta = \frac{\pi}{26388279066432}$
 $\theta = \frac{\pi}{52776558132864}$
 $\theta = \frac{\pi}{105553116265728}$
 $\theta = \frac{\pi}{211106232531456}$
 $\theta = \frac{\pi}{422212465062912}$
 $\theta = \frac{\pi}{844424930125824}$
 $\theta = \frac{\pi}{1688849860251648}$
 $\theta = \frac{\pi}{3377699720503296}$
 $\theta = \frac{\pi}{6755399441006592}$
 $\theta = \frac{\pi}{13510798882013184}$
 $\theta = \frac{\pi}{27021597764026368}$
 $\theta = \frac{\pi}{54043195528052736}$
 $\theta = \frac{\pi}{108086391056105472}$
 $\theta = \frac{\pi}{216172782112210944}$
 $\theta = \frac{\pi}{432345564224421888}$
 $\theta = \frac{\pi}{864691128448843776}$
 $\theta = \frac{\pi}{1729382256897687552}$
 $\theta = \frac{\pi}{3458764513795375104}$
 $\theta = \frac{\pi}{6917529027590750208}$
 $\theta = \frac{\pi}{13835058055181500416}$
 $\theta = \frac{\pi}{27670116110363000832}$
 $\theta = \frac{\pi}{55340232220726001664}$
 $\theta = \frac{\pi}{110680464441520033328}$
 $\theta = \frac{\pi}{221360928883040066656}$
 $\theta = \frac{\pi}{442721857766080133312}$
 $\theta = \frac{\pi}{885443715532160266624}$
 $\theta = \frac{\pi}{1770887431064320533248}$
 $\theta = \frac{\pi}{3541774862128641066496}$
 $\theta = \frac{\pi}{7083549724257282132992}$
 $\theta = \frac{\pi}{14167099448514564265984}$
 $\theta = \frac{\pi}{28334198897029128531968}$
 $\theta = \frac{\pi}{56668397794058257063936}$
 $\theta = \frac{\pi}{113336795588116514127872}$
 $\theta = \frac{\pi}{226673591176232028255744}$
 $\theta = \frac{\pi}{453347182352464056511488}$
 $\theta = \frac{\pi}{906694364704928113022976}$
 $\theta = \frac{\pi}{1813388729409856226045952}$
 $\theta = \frac{\pi}{3626777458819712452091904}$
 $\theta = \frac{\pi}{7253554917639424904183808}$
 $\theta = \frac{\pi}{14507109835278849808367616}$
 $\theta = \frac{\pi}{29014219670557699616735232}$
 $\theta = \frac{\pi}{58028439341115399233470464}$
 $\theta = \frac{\pi}{116056878682230798466940928}$
 $\theta = \frac{\pi}{232113757364461596933881856}$
 $\theta = \frac{\pi}{464227514728923193867763712}$
 $\theta = \frac{\pi}{928454029457846387735527424}$
 $\theta = \frac{\pi}{1856908058915692775471054848}$
 $\theta = \frac{\pi}{3713816117831385550942109696}$
 $\theta = \frac{\pi}{7427632235662771101884219392}$
 $\theta = \frac{\pi}{14855264471325542203768438784}$
 $\theta = \frac{\pi}{29710528942651084407536877568}$
 $\theta = \frac{\pi}{59421057885302168815073755136}$
 $\theta = \frac{\pi}{118842115770604337630147510272}$
 $\theta = \frac{\pi}{237684221541208675260295020544}$
 $\theta = \frac{\pi}{475368443082417350520590041088}$
 $\theta = \frac{\pi}{950736886164834701041180082176}$
 $\theta = \frac{\pi}{1901473772329669402082360164352}$
 $\theta = \frac{\pi}{3802947544659338804164720328704}$
 $\theta = \frac{\pi}{7605895089318677608329440657408}$
 $\theta = \frac{\pi}{15211790178637355216658881314816}$
 $\theta = \frac{\pi}{30423580357274710433317762629632}$
 $\theta = \frac{\pi}{60847160714549420866635525259264}$
 $\theta = \frac{\pi}{121694321429098841733271050518528}$
 $\theta = \frac{\pi}{243388642858197683466542101037056}$
 $\theta = \frac{\pi}{486777285716395366933084202074112}$
 $\theta = \frac{\pi}{973554571432790733866168404148224}$
 $\theta = \frac{\pi}{1947109142865581467732336808296448}$
 $\theta = \frac{\pi}{3894218285731162935464673616592896}$
 $\theta = \frac{\pi}{7788436571462325870929347232185792}$
 $\theta = \frac{\pi}{1557687314292465174185868446437584}$
 $\theta = \frac{\pi}{3115374628584930348371736892875168}$
 $\theta = \frac{\pi}{6230749257169860696743473785750336}$
 $\theta = \frac{\pi}{12461498514339721393486947571500672}$
 $\theta = \frac{\pi}{24922997028679442786973895143001344}$
 $\theta = \frac{\pi}{49845994057358885573947790286002688}$
 $\theta = \frac{\pi}{99691988114717771147895580572005376}$
 $\theta = \frac{\pi}{199383976229435542295791161144010752}$
 $\theta = \frac{\pi}{398767952458871084591582322288021504}$
 $\theta = \frac{\pi}{797535904917742169183164644576043008}$
 $\theta = \frac{\pi}{1595071809835484338366329289152086016}$
 $\theta = \frac{\pi}{3190143619670968676732658578304172032}$
 $\theta = \frac{\pi}{6380287239341937353465317156608344064}$
 $\theta = \frac{\pi}{12760574478683874706930634313216688128}$
 $\theta = \frac{\pi}{25521148957367749413861268626433376256}$
 $\theta = \frac{\pi}{51042297914735498827722537252866752512}$
 $\theta = \frac{\pi}{102084595829470997655445074505733505024}$
 $\theta = \frac{\pi}{204169191658941995310890149011467010048}$
 $\theta = \frac{\pi}{408338383317883990621780298022934020096}$
 $\theta = \frac{\pi}{816676766635767981243560596045868040192}$
 $\theta = \frac{\pi}{1633353533271535962467121192091736080384}$
 $\theta = \frac{\pi}{3266707066543071924934242384183472160768}$
 $\theta = \frac{\pi}{6533414133086143849868484768366944321536}$
 $\theta = \frac{\pi}{13066828266172287699736969536733888643072}$
 $\theta = \frac{\pi}{26133656532344575399473939073467777286144}$
 $\theta = \frac{\pi}{52267313064689150798947878146935554572288}$
 $\theta = \frac{\pi}{104534626129378301597895756293871109445776}$
 $\theta = \frac{\pi}{209069252258756603195791512587742218891552}$
 $\theta = \frac{\pi}{418138504517513206391583025175484437783104}$
 $\theta = \frac{\pi}{836277009035026412783166050350968875566208}$
 $\theta = \frac{\pi}{167255401807005282556633210070193775113216}$
 $\theta = \frac{\pi}{334510803614010565113266420140387550226432}$
 $\theta = \frac{\pi}{669021607228021130226532840280775100452864}$
 $\theta = \frac{\pi}{1338043214456042260453065680561552200905728}$
 $\theta = \frac{\pi}{2676086428912084520906131361123104401811456}$
 $\theta = \frac{\pi}{5352172857824169041812262722246208803622912}$
 $\theta = \frac{\pi}{1070434571564833808362452544449217760725584}$
 $\theta = \frac{\pi}{2140869143129667616724905088898435521451168}$
 $\theta = \frac{\pi}{4281738286259335233449810177796871042902336}$
 $\theta = \frac{\pi}{8563476572518670466899620355593742085804672}$
 $\theta = \frac{\pi}{1712695314503734093379840711118758417160944}$
 $\theta = \frac{\pi}{3425390629007468186759681422237516834321888}$
 $\theta = \frac{\pi}{6850781258014936373519362844475033668643776}$
 $\theta = \frac{\pi}{1370156251602987274703872568895066733728752}$
 $\theta = \frac{\pi}{2740312503205974549407745137790133467457504}$
 $\theta = \frac{\pi}{5480625006411949098815490275580266934915008}$
 $\theta = \frac{\pi}{10961250012823898197630980551160533868290016}$
 $\theta = \frac{\pi}{21922500025647796395261961102321067725580032}$
 $\theta = \frac{\pi}{43845000051295592790523922204642134451160064}$
 $\theta = \frac{\pi}{87690000102591185581047844409284268802320128}$
 $\theta = \frac{\pi}{17538000020518237116209568881856853604640256}$
 $\theta = \frac{\pi}{35076000041036474232419137763713707209280512}$
 $\theta = \frac{\pi}{70152000082072948464838275527427414418560224}$
 $\theta = \frac{\pi}{14030400016414589692967655105485482883712048}$
 $\theta = \frac{\pi}{28060800032829179385935310210970965767424096}$
 $\theta = \frac{\pi}{56121600065658358771870620421941931534848192}$
 $\theta = \frac{\pi}{11224320013131671754374124084388386306896384}$
 $\theta = \frac{\pi}{22448640026263343508748248168776773133792768}$
 $\theta = \frac{\pi}{44897280052526687017496496337553546667985536}$
 $\theta = \frac{\pi}{8979456001050537403499299267510709333597112}$
 $\theta = \frac{\pi}{1795891200210107480699859853502141866794224}$
 $\theta =$

obj. & voltage ratios as exponentials:

The absolute value of the ratio of op ct. to op ct. of a given symmetrical N/W was defined as an exponential f_n .

$$\frac{I_1}{I_2} = e^{\alpha} ; \alpha \rightarrow \text{complex no.} \Rightarrow \alpha + j\beta.$$

$$\frac{I_1}{I_2} = e^{\alpha} = e^{\alpha + j\beta}$$

$$\frac{I_1}{I_2} = A e^{j\beta}$$

$$A = \left| \frac{I_1}{I_2} \right| = e^\alpha ; \angle \beta = e^{j\beta}$$

$$\text{It is also true for } \frac{V_1}{V_2} = e^\alpha$$

$\alpha \rightarrow$ propagation const.

$\alpha \rightarrow$ attenuation const. \rightarrow Attn - produced in passing thro' the N/W.

$\alpha \rightarrow$ revers.

$\beta \rightarrow$ phase const \rightarrow phase angle b/w S/P and Q/P Quantities.

or the shift in phase introduced by the N/W.

B Unit - radians.

for cascaded N/W

$$\frac{I_1}{I_2} \times \frac{I_2}{I_3} \times \dots \times \frac{I_{n-1}}{I_n} = \frac{I_1}{I_n}$$

$$\text{for which } e^{\alpha_1} \times e^{\alpha_2} \times e^{\alpha_3} \times \dots = e^{\alpha_n}$$

& taking natural log, we get successive

$$\alpha_1 + \alpha_2 + \alpha_3 + \dots = \alpha_n$$

so the overall prop. const. is equal to the sum of the individual propagation constants.

$$\frac{d}{dx} \log \alpha = \alpha \frac{d\alpha}{dx}$$

$$\frac{d}{dx} \log \alpha = \frac{d\alpha}{\alpha}$$

$$1 = \alpha^2 d\alpha - \alpha d\alpha$$

Hyperbolic trigonometry

The hyperbola is the locus for the radius r .

$$\sinh u = \frac{a}{r}$$

$$\cosh u = \frac{b}{r}$$

$$\tanh u = \frac{a}{b}$$

hyperbola ~~for~~ simplifying the uniting of certain exponential relations.


A few properties are summarized & extended to the case of complex angles.

$$\sinh u = \frac{e^u - e^{-u}}{2}$$

$$\cosh u = \frac{e^u + e^{-u}}{2}$$

$$\tanh u = \frac{\sinh u}{\cosh u} = \frac{1}{\coth u}$$

$$\cosh^2 u - \sinh^2 u = 1$$

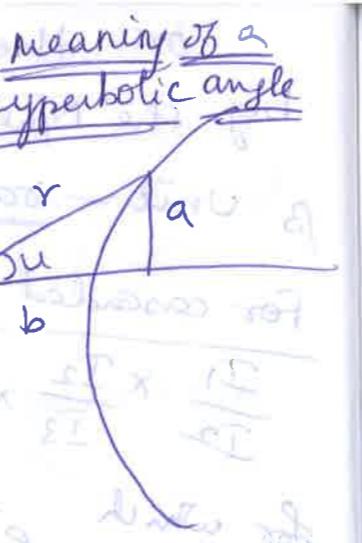

for u is larger, $\sinh u = \cosh u$.
 u is imaginary or $u = jw$.

$$\sinh jw = \frac{e^{jw} - e^{-jw}}{2} = j \sin w$$

$$\cosh jw = \frac{e^{jw} + e^{-jw}}{2} = \cos w.$$

For complex angles, $u = a + jb$

$$\sinh(a+jb) = \sinh a \cosh jb + \cosh a \sinh jb$$
$$= \sinh a \cos b + j \cosh a \sin b$$

$$\cos(a+jb) = \cosh a + \cosh jb + j \sinh a \sin b$$
$$= \cosh a \cos b + j \sinh a \sin b$$

Few useful half angles are

$$\sinh \frac{u}{2} = \sqrt{\frac{1}{2} (\cosh u - 1)}$$

$$\cosh \frac{u}{2} = \sqrt{\frac{1}{2} (\cosh u + 1)}$$

$$\sinh u = 2 \sinh \frac{u}{2} \cosh \frac{u}{2}.$$

$$\text{Ans} \quad \sinh^2 u = \cosh^2 u - 1 = \cosh 2u$$

Properties of symmetrical N/W's

Consider a symmetrical
N/W with given load.

The mesh eqns are:

$$E = I_1 \left(\frac{Z_1}{2} + Z_2 \right) - Z_2 I_2 \quad \text{--- (1)}$$

$$0 = -I_1 Z_2 + I_2 \left(\frac{Z_1}{2} + Z_0 + Z_2 \right) \quad \text{--- (2)}$$

$$I_1 Z_2 = I_2 \left(\frac{Z_1}{2} + Z_0 + Z_2 \right)$$

$$\frac{I_1}{I_2} = \frac{1}{2} \left(\frac{Z_1}{2} + Z_0 + Z_2 \right)$$

$$\frac{I_1}{I_2} = \frac{\frac{Z_1}{2} + Z_0 + Z_2}{2} = e^{j\delta} \quad \text{--- (3)}$$


notation not written

$$\frac{Z_1}{2} + Z_0 + Z_2 = Z_2 e^{j\delta}$$

$$Z_0 = Z_2 (e^{j\delta} - 1) - \frac{Z_1}{2} \quad \text{--- (4)}$$

$$\text{from } Z_{OT} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2} = Z_{ho}$$
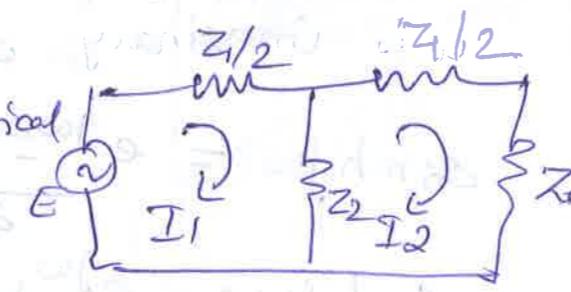
$$Z_{OT}^2 = Z_0^2 = \frac{Z_1^2}{4} + Z_1 Z_2 \quad \text{--- (5)}$$



$$Z_2 (e^{j\delta} - 1)^2 - Z_1 e^{j\delta} = 0$$

$$e^{2j\delta} - 2e^{j\delta} + 1 = \frac{Z_1}{Z_2} e^{j\delta}$$

$$\frac{e^{2j\delta} - 2e^{j\delta} + 1}{e^{j\delta}} = \frac{Z_1}{Z_2}$$

$$\frac{e^{2j\delta}}{e^{j\delta}} - 2 + \frac{1}{e^{j\delta}} = \frac{Z_1}{Z_2}$$

$$e^{j\delta} + e^{-j\delta} = 2 + \frac{Z_1}{Z_2}$$

$$\frac{e^{j\delta} + e^{-j\delta}}{2} = 1 + \frac{Z_1}{2Z_2}$$

$$\cosh j\delta = 1 + \frac{Z_1}{2Z_2} \quad \text{--- (6)}$$

$$\cosh^2 j\delta - \sinh^2 j\delta = 1$$

$$\cosh^2 j\delta - 1 = 2 \sinh^2 j\delta$$

absturzpunkt 104/2

• GFA 101/2 B

bald auf beschl. - wird zu dominant *

- 12% beschl. - dominante 10 ggf *

- 12 = 12 + 5 = 17 91% 17 ③

• 12% sozial plus 1. ritton wir in
bald sozial wir in markt mit
12% abhängig ob es geht p. k. markt ④
d. nachfrage & bewerbs und mfa

• 12% abhängig k. j. k. markt aus in
markt abhängig von 12% abhängig *

$$\left[\frac{1}{12} \right] = \left(1 - \frac{1}{12} + 1 \right)^{-\frac{1}{12}} = 1.074 \text{ Absatz}$$

• 12% abhängig und gleich verteilt mit 12% abhängig
12% abhängig & gleich 12% abhängig ⑤

• 12% abhängig do nicht wie vor gleichverteilt
markt und plus abhängig mit 12% abhängig

• 12% abhängig - 12% abhängig

$$12 = 12 + 12 = 24$$

$$12 = 12 + 12 = 24$$

$$12 = 12 + 12 = 24$$

$$12 = 12 + 12 = 24$$

$$12 = 12 + 12 = 24$$

$$12 = 12 + 12 = 24$$

12% abhängig - 12% abhängig

$$12% abhängig = 1 - 12/100$$

①

Filter Fundamentals

A Filter H/W,

- * Transmit or pass - desired freq band
- * Stop or attenuate - undesired freq.

$$\textcircled{1} \quad \frac{I_1}{I_2} = e^{\alpha} \cdot e^{j\beta} \quad \alpha = 0 \quad I_1 = I_2$$

i.e. no atten., only phase shift,
the operation is in pass band.

\textcircled{2} when $\alpha \rightarrow +ve$ I_2 is smaller than I_1
Attn. has occurred & operation is

in an stop band freq \xrightarrow{is}
* The prop. const. may be conveniently studied

$$\sinh \frac{\alpha}{2} = \sqrt{\frac{1}{2} \left(1 + \frac{Z_1}{4Z_2} - 1 \right)} = \sqrt{\frac{Z_1}{4Z_2}}$$


* Assume the H/W contains only pure reactances.
i.e. $\frac{Z_1}{4Z_2}$ will be real & either +ve or -ve
depending on the type of reactance Z_1, Z_2
& the H/W contains only pure reactance.

$$\sinh \frac{\alpha}{2} = \sinh \frac{\alpha}{2} \left(\frac{Z_1 + jZ_2}{2} \right)$$

$$= \sinh \frac{\alpha}{2} \cos \frac{\beta}{2} + j \cosh \frac{\alpha}{2} \sin \frac{\beta}{2} \quad \textcircled{2}$$

Cases

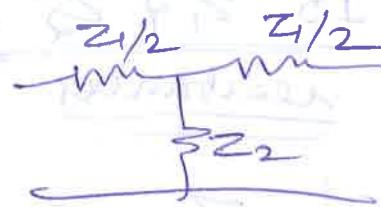If $Z_1 + jZ_2$ are same
type of reactances,



$$\frac{Z_1}{4Z_2} > 0, \rightarrow +ve \& real$$

$\therefore \sinh \frac{\alpha}{2}$ be real, imaginary term = 0

$$\textcircled{1} \quad \cosh \frac{\alpha}{2} \cdot \sin \frac{\beta}{2} = 0 \quad \textcircled{3}$$

$$\textcircled{2} \quad \sinh \frac{\alpha}{2} \cos \frac{\beta}{2} = \sqrt{\frac{Z_1}{4Z_2}} \quad \textcircled{4}$$

$$\text{From } \textcircled{2}, \quad \sin \frac{\beta}{2} = 0 \quad \beta = n\pi, \quad n = 0, 2, 4, \dots$$

$$\text{From } \textcircled{1} \quad \cosh \frac{\alpha}{2} = 1 \quad \sinh \frac{\alpha}{2} = \sqrt{\frac{Z_1}{4Z_2}}$$

$$\text{Attn. } \alpha = 2 \sinh^{-1} \sqrt{\frac{Z_1}{4Z_2}} \quad \textcircled{5}$$

$\left| \frac{z_1}{4z_2} \right| > 0$ implies a stop or attn.
band of freq's.

Case 2
If $z_1 + z_2$ are opposite types of
resonances

$\frac{z_1}{4z_2}$ is re, $\left| \frac{z_1}{4z_2} \right| < 0$,

& $\sinh \frac{\alpha}{2} = \sqrt{\frac{z_1}{4z_2}}$ is imaginary.

$$\sinh \frac{\alpha}{2} = \sinh \frac{\alpha}{2} \cdot \cos \frac{\beta}{2} + j \cosh \frac{\alpha}{2} \sin \frac{\beta}{2}$$

the real term must be zero.

$$\textcircled{3} \quad \sinh \frac{\alpha}{2} \cos \frac{\beta}{2} = 0 \quad \text{--- } \textcircled{6}$$

$$\textcircled{4} \quad \cosh \frac{\alpha}{2} \sin \frac{\beta}{2} = \sqrt{\frac{z_1}{4z_2}} \quad \text{--- } \textcircled{7}$$

must be satisfied.

two condns are possible.

$\textcircled{6} \Rightarrow \sinh \frac{\alpha}{2} = 0, \therefore \alpha = 0 \quad \beta \neq 0$

$\textcircled{7} \Rightarrow \cosh \frac{\alpha}{2} = \sqrt{\frac{z_1}{4z_2}}$

$\textcircled{6} \Rightarrow \cos \frac{\beta}{2} = 0, \therefore \sin \frac{\beta}{2} = \pm 1$

$\alpha \neq 0 \quad \beta = (2n-1)\pi$

$\cosh \frac{\alpha}{2} = \sqrt{\frac{z_1}{4z_2}}$

From condn: I leads to a PB, which is limited by the upper limit on the sine or by $\sin \frac{\beta}{2} = 1$ or

$-1 < \frac{z_1}{4z_2} < 0$

phase angle $\beta = 2 \sin^{-1} \sqrt{\frac{z_1}{4z_2}}$ --- $\textcircled{8}$


Condn-II leads to stop or attn. band

Since $\alpha \neq 0$,

The phase angle is π , & attn. is given by $\alpha = 2 \cosh^{-1} \sqrt{\frac{Z_1}{4Z_2}} \rightarrow (9)$

$\frac{Z_1}{4Z_2} < -1 \rightarrow$ The hyperbolic cosine has no value below unity.

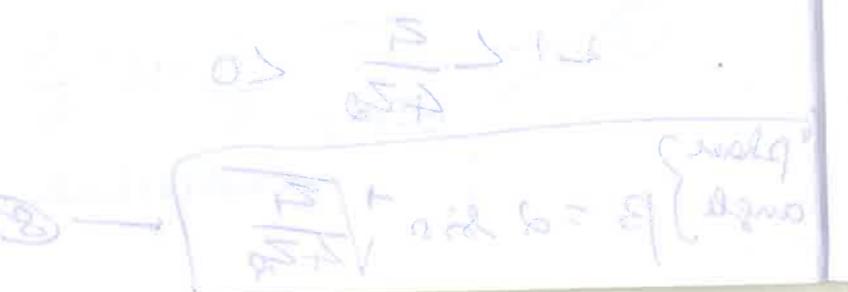Values of $\frac{Z_1}{4Z_2}$ classified into 3 regions corresponding to $\alpha + \beta$, these regions being bounded by, $\frac{Z_1}{4Z_2}$ values of $+ \infty, -1$ & $- \infty$.



$$\frac{Z_1}{4Z_2} = +\infty \text{ to } 0 \rightarrow -1 \text{ to } -\infty$$

Resistance } same opposite opposite
type

~~Band Stop pass stop~~

$$+ \infty \text{ to } 0 \rightarrow 2 \sinh^{-1} \sqrt{\frac{Z_1}{4Z_2}}$$

$$0 \rightarrow 2 \sin^{-1} \sqrt{\frac{Z_1}{4Z_2}} \rightarrow 2 \sin^{-1} \sqrt{\frac{Z_1}{4Z_2}} \rightarrow \pi$$

The frequency at which the N/W changes from pass N/W to a stop N/W, or vice versa is called cutoff freq's.

These feeds occur when

$$\frac{Z_1}{4Z_2} = 0 \text{ or } Z_1 = 0$$

$$\frac{Z_1}{4Z_2} = -1 \text{ or } Z_1 = -4Z_2$$

where Z_1 & Z_2 are opposite type reactances

Since Z_1 & Z_2 have no. of configurations, as L & C elements

or as π and series combinations
a variety of types of performances
are possible.

Behavior of the chenach impedance

for symmetrical T n/w,

$$Z_{OT} = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)}$$

if a N/W is entirely made up pure reactances, then this may be

$$Z_{OT} = \sqrt{-X_1 X_2 \left(1 + \frac{X_1}{4X_2}\right)}$$

- sign due to j^2

① X_1 & X_2 are same type reactance
stop band exist.

$$\frac{X_1}{4X_2} = \text{real & positive}$$

$Z_0 \rightarrow$ pure reactance in the
attenuation region

② X_1 & X_2 were opposite reactances

$$-1 < \frac{X_1}{4X_2} < 0 \rightarrow \text{pass band exist in moderation}$$

product $x_1 x_2 = -ve$

$Z_0 \rightarrow$ real & able to absorb power from a source.

③ $x_1 + x_2 \rightarrow$ opposite reactance.

$\frac{x_1}{x_2} < -1$ stop band exist.

$$x_1 x_2 = -ve$$

$Z_0 \rightarrow$ pure reactances

from the above,

* pass band Z_0 \rightarrow real & positive.
reactive N/w is terminated with a resistive $Z_0 = R_0$, if p. imp. = Z_0

The N/w can accept power & will transmit to the resistive load without loss or attenuation.

In stop band $Z_0 \rightarrow$ has been shown

to be reactive.
if a N/w is terminated ~~in~~ its

reactive Z_0 ,
 \rightarrow it will appear as a totally reactive circuit.

\rightarrow can't accept or transmit power.

Since there is no resistive element in which the power may be dissipated

* The N/w may transmit & or

but with 90° phase angle b/w them & with considerable attenuation.

Pg for TT N/w:

$$Z_{TT} = \frac{Z_{12}}{Z_{01}}$$

Z_{12} is always real for Z_{12} as pure reactances.

The constant k low pass filter

$Z_1 + Z_2 \rightarrow$ reactance arms

$$Z_1 Z_2 = k^2$$

where $k \rightarrow \text{const. independent of freq.}$
The N/w's or filter section \rightarrow called
const- k filters.


Let assume $Z_1 = j\omega L$ & $Z_2 = j\omega C$

$$Z_2 = -j/\omega C$$

$$\text{Then the product } Z_1 Z_2 = \frac{L}{C} = R_k^2$$

R_k is used since k must be real
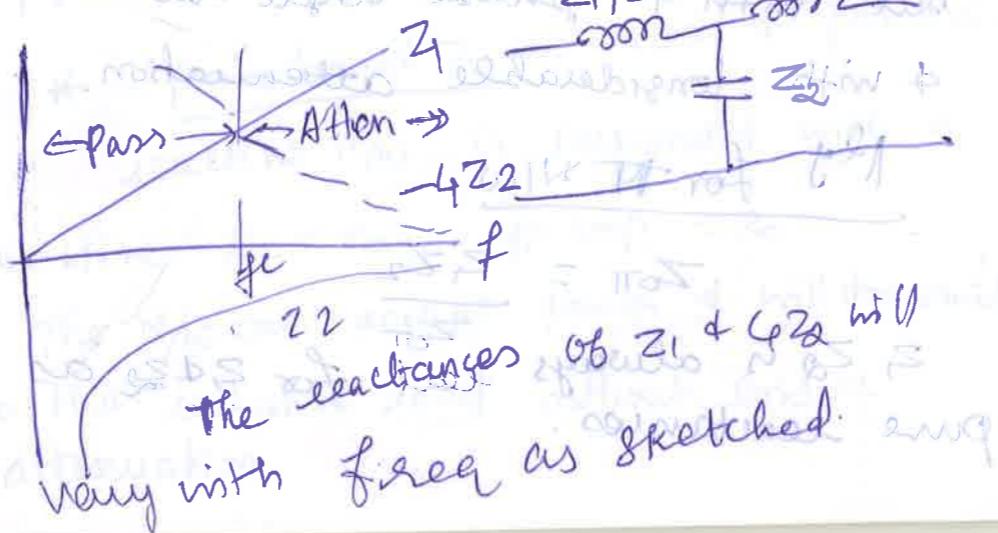
$$R_k = \sqrt{Z_1 Z_2} = \sqrt{Z_1^2 + Z_2^2}$$



The pass band starts at freq at which $Z_1 = Z_2$ & runs to the freq at which $Z_1 \rightarrow 4Z_2$.

The reactance curves show that a pass band starts at $f=0$ & continues to some higher freq f_c .

All freq's above f_c lie in stop band or attenuation band.

Thus the N/w is called LPF.
The cut off freq. may be determined,

$$Z_1 = -4Z_2 \quad j\omega L = \frac{4j}{\omega C}$$

$$j\omega C = -4Z_2$$

$$\omega_c^2 = \frac{4}{LC} \quad f_c^2 = \frac{4}{4\pi^2 LC}$$

The $\sinh \frac{\alpha}{2}$ may be evaluated as

$$\sinh \frac{\alpha}{2} \sqrt{\frac{Z_1}{4Z_2}} = \sqrt{\frac{\omega^2 LC}{4}} = \frac{j\omega}{2} \sqrt{LC}$$

$$\sinh \frac{\alpha}{2} = j \frac{2\pi f}{2} \sqrt{LC} = j \frac{f}{f_c}$$

f is passband $\frac{f}{f_c} < 1$

so that $-1 < \frac{z_1}{4z_2} < 0$


$$\frac{f}{f_c} < 1, \alpha = 0 \quad \beta = 2.8n_3^{\frac{1}{2}}(f/f_c)$$

whereas, if is in atten band or $f/f_c > 1$

so that $\frac{z_1}{4z_2} < -1$ then

$$\frac{f}{f_c} > 1, \alpha = 2 \operatorname{cosec}^{-1} \left(\frac{f}{f_c} \right); \beta = \pi$$

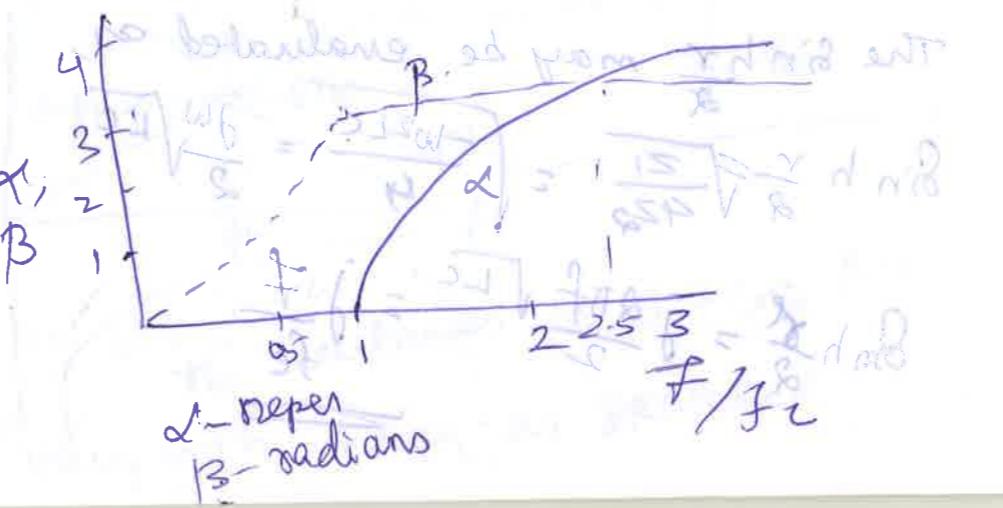The variation of $\alpha + \beta$ is plotted



α is zero throughout the passband.
* Raises gradually from fc at cut-off freq at $f/f_c = 1$ to infinite freq.

* β is zero at 0 freq.

* rises gradually through the pass band, reaching π at f_c & remaining at π for all higher freq.


The charac. imp. for T-section

$$Z_{0T} = \sqrt{z_1 z_2 \left(1 + \frac{z_1}{4z_2} \right)}$$

$$Z_{0T} = \sqrt{\frac{L}{C} \left(1 - \frac{w_0^2 LC}{4} \right)}$$

$$= \sqrt{\frac{L}{C} \left(1 - \left(\frac{f}{f_c} \right)^2 \right)} = R_k \sqrt{1 - \left(\frac{f}{f_c} \right)^2}$$

Values of Z_{OT} plotted against f/f_c

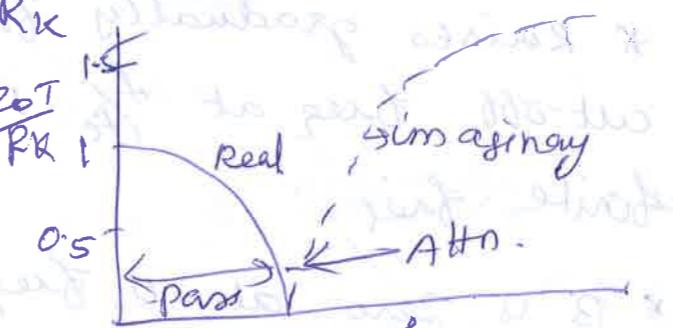

Z_{OT} varies throughout f/f_c .
 It remains real in the pass band, reaching zero at the pass band, becoming imaginary in cut-off, then becomes infinite in the atten. band, rising to infinite reactance at infinite frequency.

$$R = R_K = \sqrt{L/C}$$

$$Z_1 = -42 \quad \omega_C L = \frac{4}{\omega_C} C$$

$$f_c = \frac{1}{\pi \sqrt{LC}} \Rightarrow \pi^2 f_c^2 LC = 1$$

$$\text{sub: } L = R^2 C \Rightarrow \pi^2 f_c^2 R^2 C^2 = 1$$

$$C^2 = \frac{1}{\pi^2 f_c^2 R^2} \Rightarrow C = \frac{1}{\pi f_c R}$$

My sub $c = \frac{L}{R^2}$

$$\therefore \pi^2 f_c^2 \frac{L^2}{R^2} = 1$$

$$L = \frac{R^2}{\pi^2 f_c^2} \quad \boxed{L = \frac{R}{\pi f_c}}$$

The design is based on an imp. match at zero freq only. Matched load will drop at power trfr to a M^- will do.
 Higher pass-band freq's



Qunt K-HPF

The positions of inductance & capacitance are interchanged to make

$$Z_1 = -\frac{j}{\omega c}, \quad Z_2 = j\omega L$$

Then $Z_1 Z_2 = k^2$

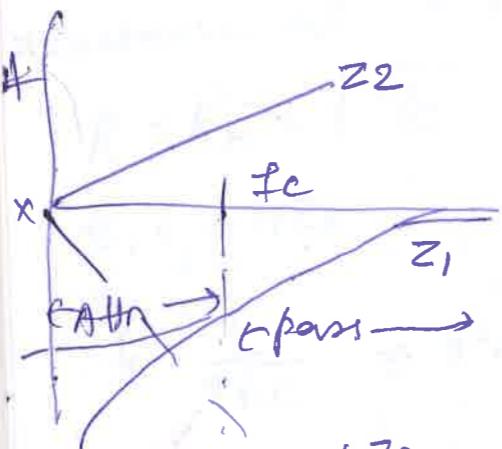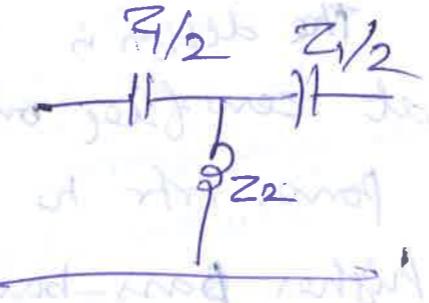Z_1, Z_2 are sketched as
a func. of freq.



- * $Z_1 \neq -4Z_2$ are compared.
- * At cut off freq Z_1 equal $-4Z_2$
- * pass band is from that freq to ∞

Cut-off freq: → determined as the freq at which, $Z_1 = -4Z_2$.

$$\frac{-j}{\omega c} = -j4\omega c L$$

$$4\omega c^2 L c = 1$$

$$f_c = \frac{1}{4\pi\sqrt{LC}}$$

using this,

$$\therefore \sinh \frac{x}{2} = \sqrt{\frac{Z_1}{4Z_2}} = \frac{1}{4\omega^2 L c}$$

$$= \frac{-j}{2\omega L c} = -j \frac{f_c}{f}$$

The region which $\frac{f_c}{f} = 1$ in pass band
 \therefore the variations of impedance &
outside the pass band will be
identical with the values of LPF

Design: $R = R_K = \sqrt{\frac{L}{C}}$ put it in

$$Z_i = -4Z_2 \quad ; \quad 4\omega_c^2 LC = 1$$

then $\frac{L}{C} = R^2$

sub $L = R^2 C$ the $4\omega_c^2 R^2 C^2 = 1$

$$C = \frac{1}{2\omega_c R}$$

$$\boxed{\frac{1}{4\pi f_c R} = C}$$

sub $C = \frac{L}{R^2}$, then $\frac{4\omega_c^2 L^2}{R^2} = 1$

$$L = \frac{R^2}{4\omega_c^2} \Rightarrow \boxed{L = \frac{R}{4\pi f_c}}$$

charac imp of HPF =

$$\boxed{Z_{OT} = R \sqrt{1 - \left(\frac{f_c}{f}\right)^2}}$$

Band Pass Filters

Pass a band of frequencies & to attenuate frequencies on both sides of the pass band.

* LP & HF filter in series

* in which the

cut-off freq's of the


LPF is above the cut-off freq. of the HPF, thus allowing only a band of freq's to pass.

* It is more economical to combine the LP & HP fn's into a single filter

section.





BPF

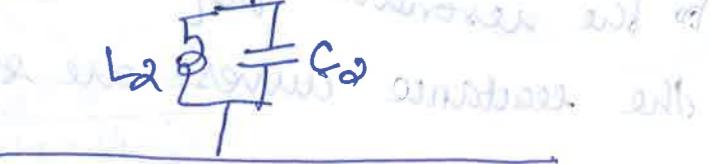

The BPF is designed with a series resonant series arm and an antiresonant shunt arm.

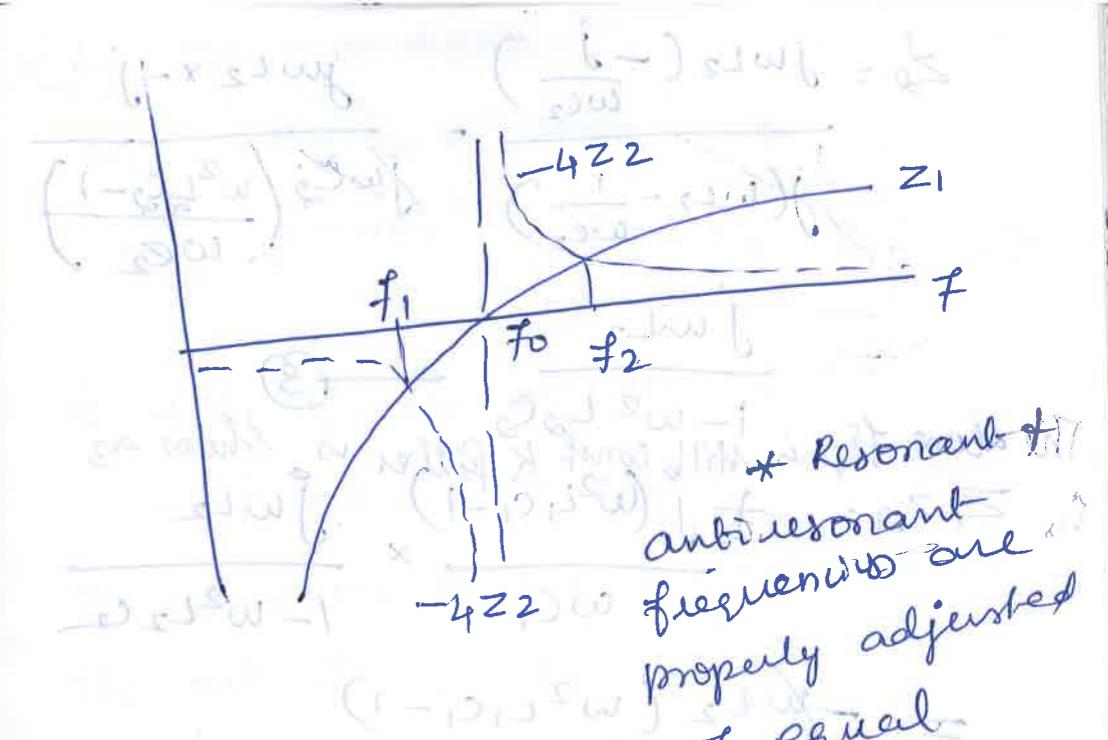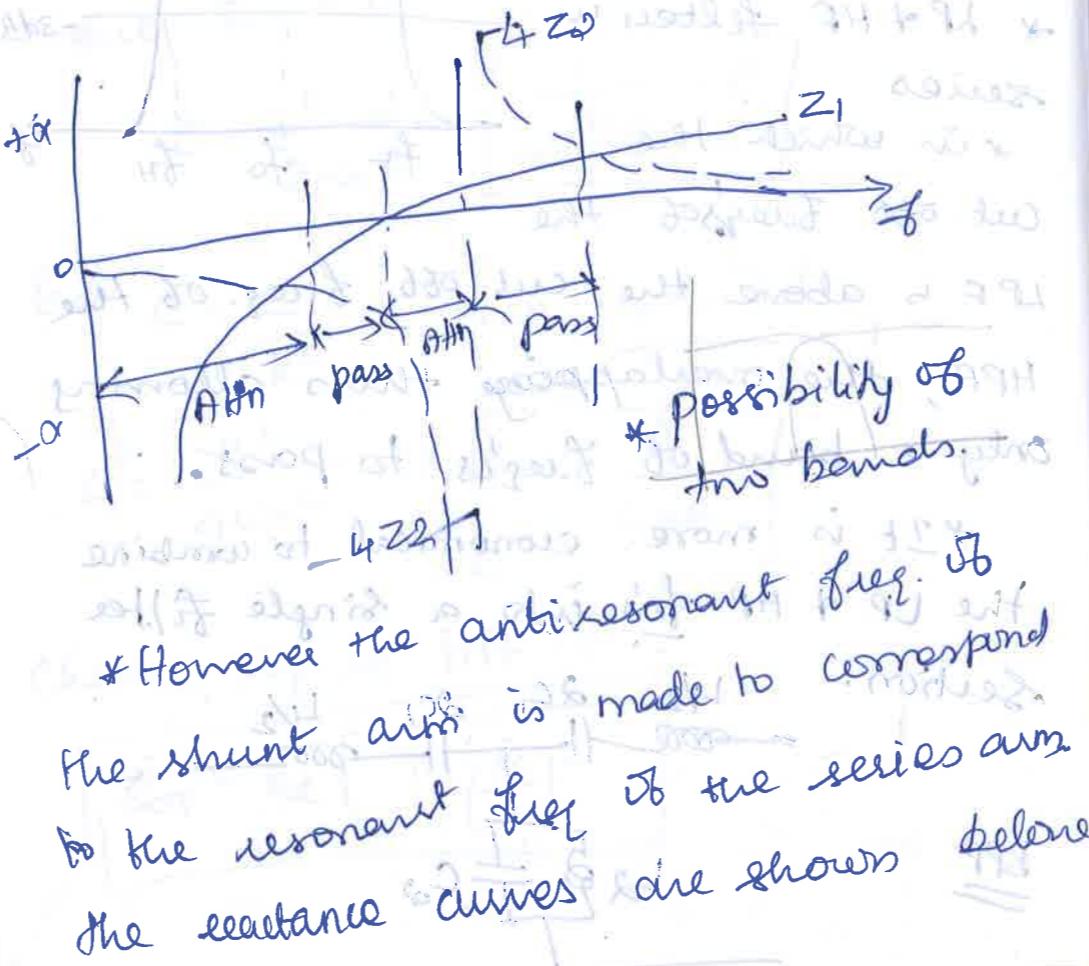* The reactance curves show that two pass bands might exist.



* For this condn, the resonant freqs

$$\omega_0^2 L_1 C_1 = 1 = \omega_0^2 L_2 C_2 \quad (1)$$

$$L_1 C_1 = L_2 C_2 \quad (2)$$

The imp. of the arms are

$$Z_1 = j\left(\omega L_1 - \frac{1}{\omega C_1}\right) = j\left(\omega^2 L_1 C_1 - 1\right) \quad (3)$$

$$Z_2 = \frac{j\omega L_2 \times j\omega C_2}{(\omega L_2 - j/\omega C_2)} \quad (4)$$

$$Z_2 = \frac{j\omega L_2 \left(-\frac{j}{\omega C_2} \right)}{j\left(\omega L_2 - \frac{1}{\omega C_2}\right)} = \frac{j\omega L_2 \times -j}{j\omega C_2 \left(\frac{\omega^2 L_2 C_2 - 1}{\omega C_2} \right)}$$

$$= \frac{j\omega L_2}{1 - \omega^2 L_2 C_2} \quad \textcircled{3}$$

The above fig b still const K filter is shown as,

$$Z_1 Z_2 = \frac{+j(\omega^2 L_1 C_1 - 1)}{\omega C_1} \times \frac{j\omega L_2}{1 - \omega^2 L_2 C_2}$$

$$= \frac{-j\omega L_2 (\omega^2 L_1 C_1 - 1)}{\omega C_1 (1 - \omega^2 L_2 C_2)}$$

$$\textcircled{4} \frac{-L_2 (\omega^2 L_1 C_1 - 1)}{(1 - \omega^2 L_2 C_2)}$$

If $L_1 C_1 = L_2 C_2$ then

$$\frac{L_1 C_1}{C_2} = \frac{L_2}{C_1} \Rightarrow Z_1 Z_2 = R_k^2 \quad \textcircled{3a}$$

At cut-off freq's, $Z_1 = -4Z_2$

From by Z_1 , we have,

$$Z_1^2 = -4Z_1 Z_2 = -4R_k^2$$

$$Z_1 = \sqrt{-4R_k^2} = \boxed{\pm j \omega R_k = Z_1} \quad \textcircled{4}$$

$\propto +Z$, at low cut-off $f_1 \approx$
 $-Z$, at upper cut-off f_2 .

The reactance of the series arm at
the cut-off freq's,

from $\textcircled{2}$

$$-j\left(\omega_1 L_1 - \frac{1}{\omega_1 C_1}\right) = j\left(\omega_2 L_2 - \frac{1}{\omega_2 C_2}\right)$$

$$\frac{1}{\omega_1 C_1} - \omega_1 L_1 = \omega_2 L_2 - \frac{1}{\omega_2 C_2}$$

$$\frac{1 - \omega_1^2 L_1 C_1}{\omega_1 C_1} = \frac{\omega_2^2 L_2 C_2 - 1}{\omega_2 C_2}$$

$$\omega_2 C_2 - \omega_1^2 \omega_2 L_1 C_1 = \omega_2^2 \omega_1 L_1 C_1 - \omega_1 C_1$$

$$\therefore \omega_2 C_2 - \omega_1^2 \omega_2 L_1 C_1 = \frac{\omega_1 \omega_2 L_1 C_1}{\omega_2} + \frac{\omega_1}{\omega_2}$$

From (6) & (7) we have

$$L_1 C_1 = \frac{1}{\omega_0^2} \rightarrow L_1 = \frac{1}{\omega_0^2 C_1} \quad \text{At } f_1 \text{ band}$$

Sub 2, from (8);
in parallel $f_{f2} = f_0$

$$L_1 = \frac{4\pi R \cdot f_1 f_2}{\pi^2 f_0^2 (f_2 - f_1)}$$

$$L_1 = \frac{R}{\pi (f_2 - f_1)} \quad \text{--- (9)}$$

Now it is possible to obtain the values
for the shunt arm,

$$\frac{L_2}{C_1} = \frac{L_1}{C_2} = R^2 \quad \text{or} \quad \frac{L_2}{C_1} = R^2$$

$$L_2 = C_1 R^2 = \frac{(f_2 - f_1) R^2}{4\pi R f_1 f_2}$$

$$C_2 = \frac{R(f_2 - f_1)}{4\pi f_1 f_2} \quad \text{--- (10)}$$

$$C_2 = \frac{L_1}{R^2} = \frac{1}{\pi (f_2 - f_1) R^2} \quad \text{--- (11)}$$


- From L_1 , C_1 , L_2 & C_2 it is possible
to design a prototype Band pass filter.

Band Elimination Filter (Band reject filter)


- This circuit does eliminate or attenuate
a given frequency band.

- This action is performed by a LPF
in parallel with HPF section.

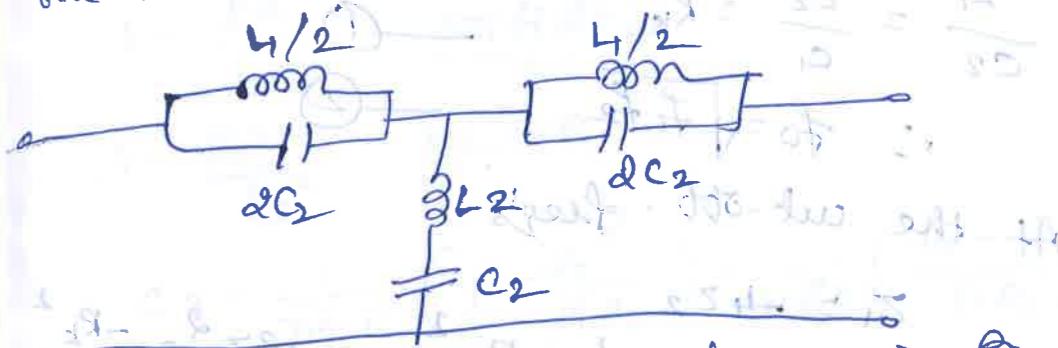- The circuit is obtained by interchange
the series & parallel arms of the BPF.



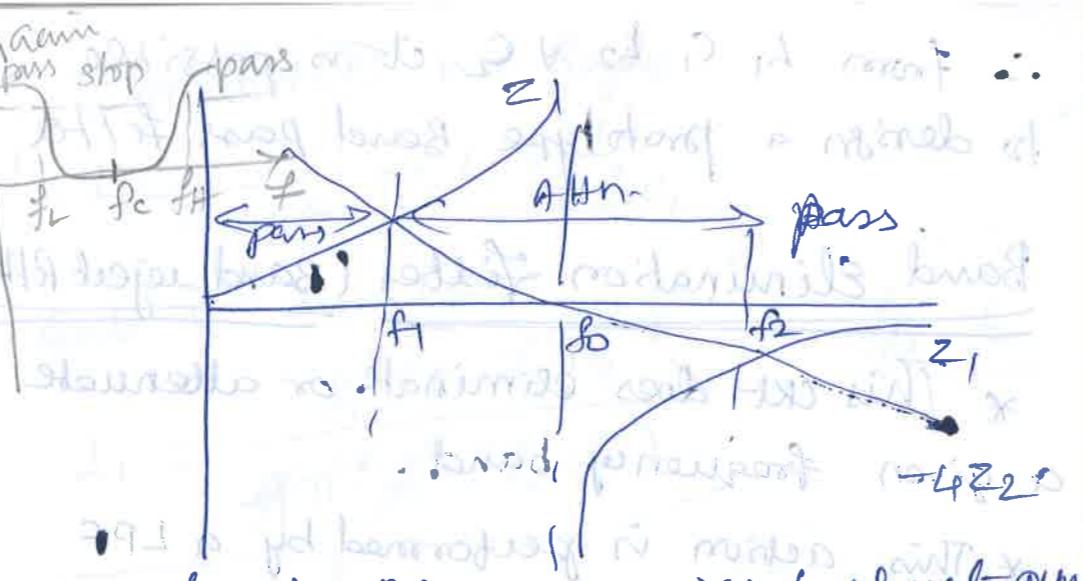- The stopband freq of LPF is
below that of HPF.



As for the BPF, the series & shunt arms are made antiresonant & resonant at the same freq f_0 .

$$\frac{L_1}{C_2} = \frac{L_2}{C_1} = k_R^2 \quad \text{--- (1)} \\ \therefore f_0 = \sqrt{f_1 f_2} \quad \text{--- (2)}$$

At the cut-off freq's:

$$Z_1 = -4Z_2 \\ Z_1 Z_2 = -4Z_2^2 = R_k^2 \Rightarrow Z_2^2 = \frac{-R_k^2}{4}$$

$$Z_2 = \pm j \frac{R_k}{2} \quad \text{--- (3)}$$

If the filter is terminated in a load $R = R_k$

then at the lower cut-off freq,

$$Z_2 = j \left(\frac{1}{\omega_0 C_2} - \omega_0 L_2 \right)$$

$$(1) \quad Z_2 = \left(j \left(\frac{1}{\omega_0 C_2} - \omega_0 L_2 \right) \right) = j \frac{R}{2} \quad \text{--- (3)}$$

$$\text{Since } L_2 C_2 = \frac{1}{\omega_0^2}$$

$$\delta \left(\frac{1 - \omega_1^2 L_2 C_2}{\omega_1 C_2} \right) = \frac{j R}{2}$$

$$1 - \frac{\omega_1^2 L_2 C_2}{\omega_0^2} = \frac{\omega_1 R C_2}{2}$$

$$1 - \frac{\omega_1^2}{\omega_0^2} = \frac{2\pi f_1 R C_2}{2}$$

$$1 - \frac{\omega_1^2}{\omega_0^2} = \pi f_1 C_2 R$$

$$C_2 = \frac{1}{\pi f_1 R} \left(1 - \frac{\omega_1^2}{\omega_0^2} \right) = \frac{1}{\pi R} \left(\frac{f_2 - f_1}{f_1 f_2} \right) \quad \text{--- (4)}$$

$$C_2 = \frac{1}{\pi R} \left(\frac{f_2 - f_1}{f_1 f_2} \right) \quad \text{--- (4)}$$

$$f_0 = \sqrt{f_1 f_2} = \frac{1}{2\pi\sqrt{L_2 C_2}}, \quad f_0^2 = \frac{1}{4\pi^2 L_2 C_2}$$

(a)

$$L_2 = \frac{1}{4\pi^2 f_0^2 C_2} \Rightarrow \frac{\pi R \cdot (f_1 f_2)}{4\pi^2 (f_1 f_2) (f_2 - f_1)}$$

$L_2 = \frac{R}{4\pi (f_2 - f_1)}$

(5)

from eqn ①,

$$\frac{L_1}{C_2} = R^2 ; \quad L_1 = R^2 C_2$$

$$L_1 = \frac{R^2 (f_2 - f_1)}{\pi \cdot R \cdot (f_1 f_2)} = \frac{R (f_2 - R)}{\pi \cdot f_1 f_2} \quad (6)$$

$$\frac{L_2}{C_1} = R^2 ; \quad C_1 = \frac{L_2}{R^2} = \frac{R}{R^2 4\pi (f_2 - f_1)}$$

$C_1 = \frac{1}{4\pi R \cdot (f_2 - f_1)}$

(7)

Attenuators. C4 terminal N/W

Amplifier \rightarrow used to ~~tre~~ the signal level by a given amount.
 Attenuators \rightarrow used to ~~tre~~ the signal level by a given amount.

* Usually resistive N/W.

\rightarrow introduce a given loss b/w

specified impedances.

classified into \rightarrow symmetrical &

Asymmetrical

\rightarrow Either fixed type or variable type.

Resistance attenuators — have only

resistive components —

\rightarrow introduce no phase shift $\therefore \beta = 0$

+ prop const $vt = \lambda$

\rightarrow e.g. volume control in Broad casting stations.

- Attenuators must satisfy:
- 1) give correct ip power
 - 2) give correct op power
 - 3) must provide specified att.

Capacitance Attenuators — HF Appl's.

Symmetrical Attenuators

* Used b/w two equal impedances
 * Since the attenuators have only resistive components, its charac. imp will also be resistive.

∴ Att is. usually in decibels & nepers

$$\text{Att } D = 10 \log_{10} \frac{P_1}{P_2}$$

$P_1 \rightarrow$ ip power, $P_2 \rightarrow$ op power.

$$\text{say } N = \sqrt{\frac{P_1}{P_2}}$$

$$\therefore D = 10 \log_{10} N^2 = 20 \log_{10} N$$

$$N = \text{Antilog}_{10} \left(\frac{D}{20} \right)$$

In case of symmetrical Att's both pair of terminals are matched to the same resistance — the charac. resistance of the attenuator.

$$\therefore \frac{P_1}{P_2} = \frac{R_o I_s^2}{R_o I_e^2} = \left(\frac{I_s}{I_e} \right)^2$$


$$N^2 = \left(\frac{I_s}{I_e} \right)^2$$

$$N = \frac{I_s}{I_e}$$

Types of Symmetrical attenuators

- 1) T
- 2) TI
- 3) Lattice
- 4) Bridged T

D) Symmetrical T-attenuators

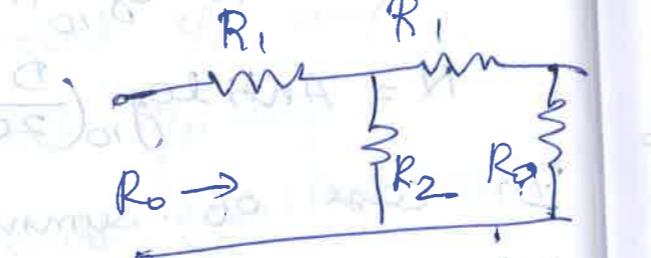

$$Z_2 = \frac{Z_0}{\sinh \alpha l}$$

$$Z_1 = Z_2 = Z_0 \left(\frac{e^{\frac{\alpha l}{2}} - e^{-\frac{\alpha l}{2}}}{e^{\alpha l/2} + e^{-\alpha l/2}} \right) = Z_0 \tanh \frac{\alpha l}{2}$$

$$R_1 = R_0 \tanh \frac{\alpha l}{2}$$

$$R_2 = R_0 / \sinh \alpha l$$

$$e^{\alpha l} = e^P = \frac{I_S}{I_R}, \quad P = \alpha l \text{ for resistance}$$

$$\text{Hence } e^{\alpha l} = \frac{I_S}{I_R} = N,$$

$$R_1 = R_0 \left(\frac{e^{\alpha l/2} - e^{-\alpha l/2}}{e^{\alpha l/2} + e^{-\alpha l/2}} \right)$$

$\times + \div$ by RHS by $e^{\alpha l/2}$. $R_1 = R_0 \left(\frac{e^{\alpha l/2} - e^{-\alpha l/2}}{e^{\alpha l/2} + e^{-\alpha l/2}} \right)$

$$R_1 = R_0 \frac{e^{\alpha l/2} - 1}{e^{\alpha l/2} + 1} = R_0 \frac{N - 1}{N + 1} \quad ; \quad e^{\alpha l/2} = N$$

$$R_2 = \frac{R_0}{e^{\alpha l/2} - 1} = \frac{2R_0}{e^{\alpha l/2} - e^{-\alpha l/2}} = \frac{2R_0}{N - 1/N}$$

$$= R_0 \cdot \frac{2N}{N^2 - 1} \quad \rightarrow (2)$$


Eqs (1) & (2) are called design eqns

of the symmetrical T-attenuator

The attn. introduced by a symmetrical T attenuator can be determined by,

$$\cosh \alpha l = \left(1 + \frac{Z_1}{2Z_0} \right) \text{ nepers} = \left(1 + \frac{R_1}{R_2} \right) \text{ nepers}$$
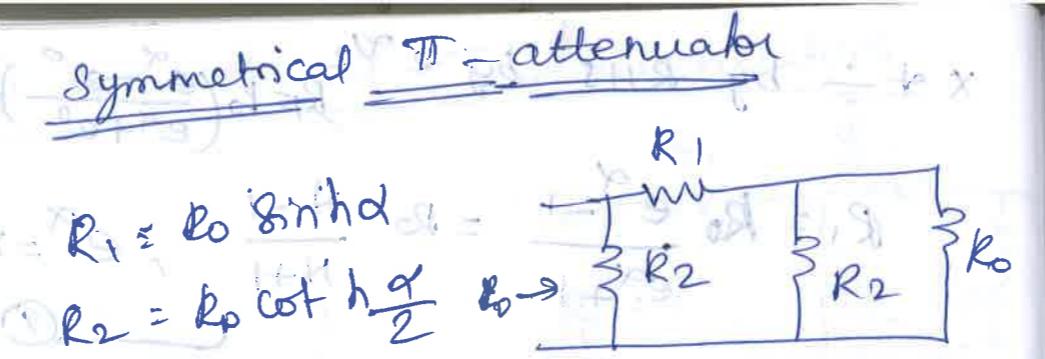
$$\text{If d.t. } \cosh^{-1} \left(1 + \frac{R_1}{R_2} \right) \text{ nepers} = x \text{ dB}$$



$$R_1 = R_0 \sinh d$$

$$R_2 = R_0 \coth \frac{d\alpha}{2} \rightarrow$$

$Z_{in} = R_0 + P - \alpha$ for resistance attenuator

By defn. of propagation const,

$$e^{pd} = e^P = \frac{I_s}{IR} \rightarrow \text{But } P = \alpha$$

$$e^d = \frac{I_s}{IR} = N.$$

The series and shunt arm may be written as,

$$R_1 = R_0 \frac{e^d - e^{-d}}{2} = R_0 \frac{N - \frac{1}{N}}{2}$$

$$\text{By } R_2 = R_0 \coth \frac{d\alpha}{2} = R_0 \frac{e^{\alpha/2} + e^{-\alpha/2}}{e^{\alpha/2} - e^{-\alpha/2}} = R_0 \frac{e^\alpha + 1}{e^\alpha - 1}$$


$$R_2 = R_0 \left(\frac{N+1}{N-1} \right) \quad \text{--- (4)}$$

eqns (3) & (4) are the design eqns for the symmetrical Π -attenuator.

Symmetrical Bridged T attenuator

It may be designed to have a central resistance R_0 but any desired attn. by making:
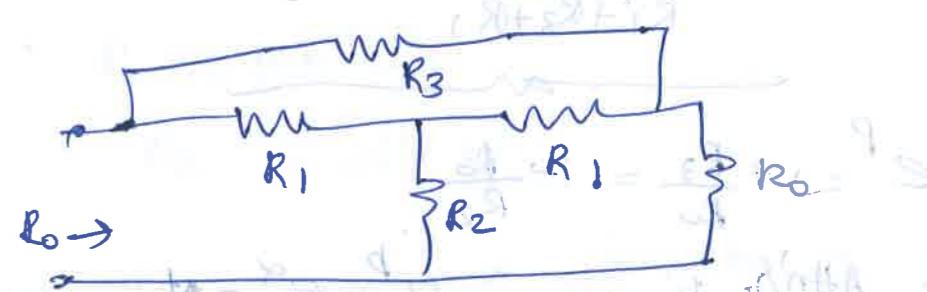
$$R_3 R_2 = R_1^2 = R_0^2 \quad \text{--- (5)}$$




The propagation const. can be expressed as,

case 1: when $R_1 = R_2$

$$P = \log_e \left(1 + \frac{R_3}{R_0} \right) +$$

$$P = \log_e \left(1 + \frac{R_0}{R_2} \right)$$

$$Z_3 = R_3 = Z_2 = R_2 + Z_0 = R_0$$

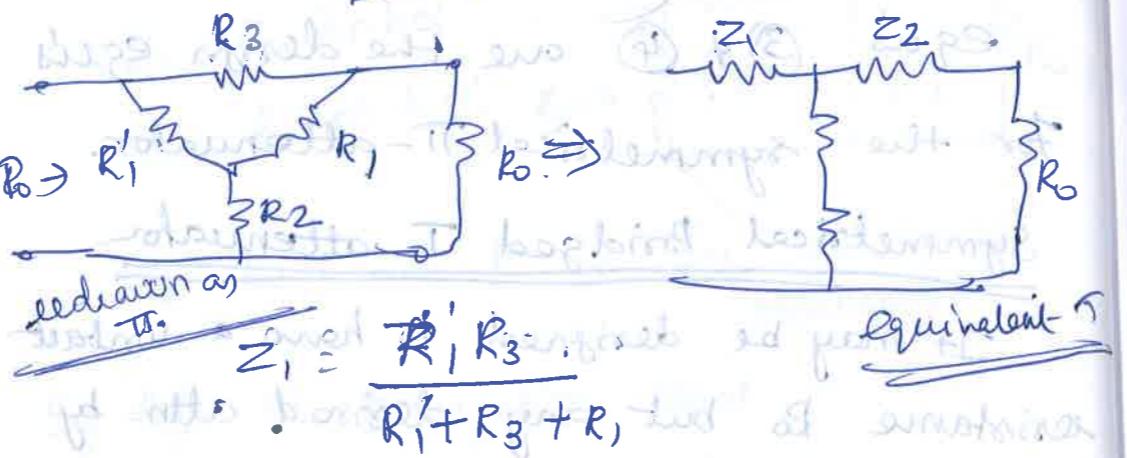

$$Z_2 = \frac{R_3 R_1}{R_1 + R_3 + R_0}$$

$$e^P = 1 + \frac{R_3}{R_0} = 1 + \frac{R_0}{R_2}$$


for Att'n, $P = \alpha \Rightarrow e^P = e^\alpha = N$.

$$N = 1 + \frac{R_3}{R_0} = 1 + \frac{R_0}{R_2}$$

$$R_3 = R_0(N-1) \quad ; \quad R_2 = \frac{R_0}{N-1} \quad \text{--- (7)}$$

from (6), $R_1 = R_0$,

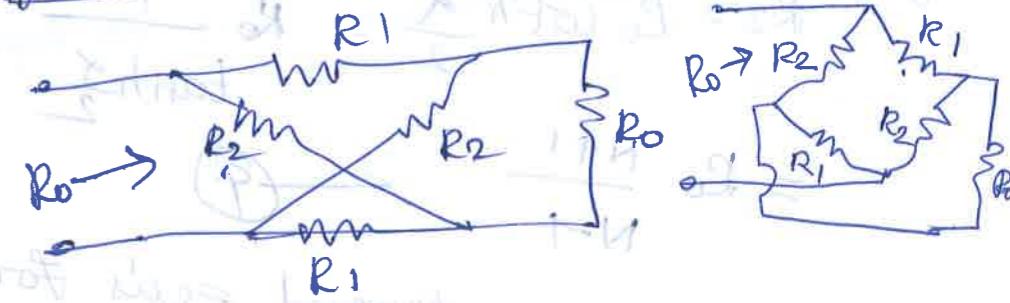(6) & (7) are design eqns for
bridged T symmetrical attenuator.
Symmetrical Lattice Attenuators



$$R_1 = Z_0 \tan \frac{h P}{2}$$

$$R_2 = Z_0 \cot \frac{h P}{2}$$

But for resistance attenuator, $Z_0 = R_0$,
and $P = \alpha$.
The series arm R_1 & shunt arm R_2
can be written as,

$$R_1 = \text{R}_0 \tanh \frac{\alpha}{2} = \frac{\text{R}_0 e^{\alpha/2} - e^{-\alpha/2}}{e^{\alpha/2} + e^{-\alpha/2}}$$

$$= \text{R}_0 \frac{e^\alpha - 1}{e^\alpha + 1} = \text{R}_0 \frac{N-1}{N+1}$$

Only $R_2 = R_0$ with $\frac{\alpha}{2} = \text{R}_0 \frac{1}{\tanh \frac{\alpha}{2}}$

$$= \text{R}_0 \frac{N+1}{N-1}$$

$\textcircled{8}$ & $\textcircled{9}$ are the designed eq's for symmetrical lattice attenuator.

Asymmetrical Attenuators

Att. & connected b/w two imp's of unequal value on asymmetrical att. may be designed to have image imp's equal to the given imp's

when N_a is the attn. of an asymmetrical attenuator.

$$N_a = \sqrt{\frac{P_1}{P_2}} = \sqrt{\frac{I_s^2 \cdot R_{i1}}{I_e^2 \cdot R_{i2}}} = \frac{I_s}{I_e} \sqrt{\frac{R_{i1}}{R_{i2}}}$$

where R_{i1} & R_{i2} are the image imp's of the asymmetrical attenuator.

Functional classification of N/W's

- ① Filters
- ② Attenuators
- ③ Equalizers - corrective N/W.
- ④ Matching N/W.