

$$k = |k| e^{j\phi}$$

$$\frac{a}{b} = |k| e^{j\phi}$$

$$a = b|k| e^{j\phi}$$

$$V_x = b e^{j\beta y} + b|k| e^{j\phi} e^{-j\beta y}$$

$$= b e^{j\beta y} \{ 1 + |k| e^{j\phi} e^{-j2\beta y} \}$$

taking only modulus

$$|V_x| = |b| \{ 1 + |k| e^{-j(2\beta y - \phi)} \}$$

for V_{max} $2\beta y_{max} - \phi = 2n\pi$

$$|V_{max}| = |b| \{ 1 + |k| \}$$

for V_{min}


$$2\beta y_{min} - \phi = (2n+1)\pi$$

$$|V_{min}| = |b| \{ 1 - |k| \}$$

$$S = \frac{1+|k|}{1-|k|}$$

first min and max at $n = 0$

open ckt load

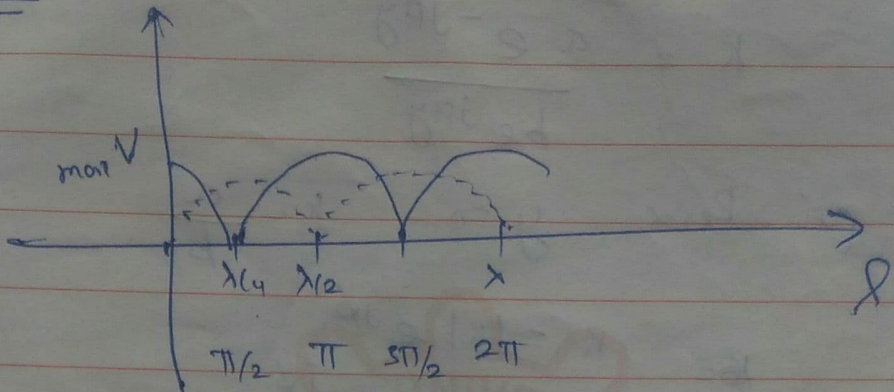

Transmitted I and reflected I equal 0
from load $\lambda/4$

$\lambda/2$

$$Z_{sc} = j \tan \beta l$$

βl

$$\frac{2\pi}{\lambda} \times \lambda/2$$

$$\pi = 0$$


$$= j \infty$$

$$= j 0$$

$$= -j \infty$$

$\lambda/2$

$j \infty$

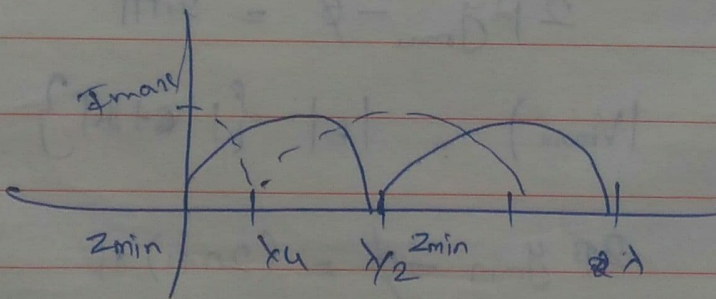

Properties of Smith chart

$$SWR = \frac{1+|k|}{1-|k|}$$

Normalised Impedance

R - Circle X - Circles

$$k = 0.91$$

$$8 \quad 1 \quad \infty$$

$$Z_0 = 300 \Omega$$

$$Z_R = 180 + j150$$

$$\text{Normalised } Z_r = \frac{180 + j150}{300} = 0.6 + j0.5$$

$$0.6 \quad R$$

$$0.5 \quad X$$

Determine SWR

0 Centre R = 1

Circle right hand Intersection VSWR. (5)

Determination of k in mag and direction

0.38 distance of 0.6 + j0.5 from centre.


113° angle

$$|k| = 0.38$$

Location of V max and V min

$$Z_{max} = 2.2 + j0$$

$$Z_{min} = 0.46 + j0$$

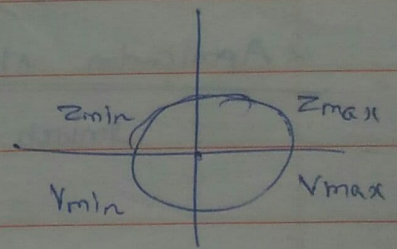

Voltage min from the load 0.0925 λ

First Voltage max at (0.0925 + 0.25) λ

$$= 0.3425 \lambda$$

Imped In
vision

open Ckt and short Ckt line

right hand side of horizontal axis

Value R & X ∞

$$Z = \infty$$

Open Ckt termination

$$Z_R = \infty$$

Left side horizontal axis

$$R=0 \quad x=0 \quad Z_R = R + jX$$

$$Z_R = 0$$

Short ckt termination on left side.

Movement along the periphery of chart

CW \curvearrowright → Wave begins towards generator
full rotation 0.5λ (or) $\lambda/2$

Impedance repeats itself every $\lambda/2$ distance.

Matched Load

$$R=1$$

$$R=Z_0$$

$$R/Z_0 = 1$$

Matched conditions

$$Z_R = \frac{Z_R}{Z_0} = 1 + j0$$

$X/Z_0 = 0$

$$Z_R = Z_0$$

Centre of chart is matched load. $Z_R = Z_0$

Application of Smith chart

Smith chart also uses as admittance chart

$$Y = g - jb$$

↓
normalised
conductance

↓ Normalised
susceptance.

Conversion of Impedance to admittance

$$\lambda/4 \text{ Impedance Inversion} \quad Z^{-1} = 1/Z$$

$$P = (0.6 + j0.5)$$

$$Q = (0.98 - j0.82)$$

Determination of I/p Impedance Z_L


Z_L given Z_{in} Calculated from Smith

Z_L find Z_{in}

travel towards Generator

2 CW

SWR Circle

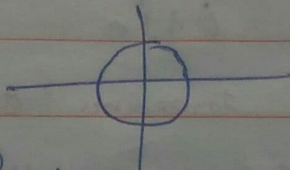

2 with Normalised I/p

Determination of Load Impedance Z_L

Impedance

If SWR and V_{max} min from the load given

Determine SWR of $Z_R = 800 + j0.0$ with $Z_0 = 400 \Omega$

$$Z_R = 650 - j175$$

$$Z_R = 2.0$$

$$SWR = 2$$

$$\rho = 2$$

$$= 1.625 - j1.18j$$

$$\rho = 2.747$$

Using Smith chart Convert Z to V .

$$0.5 + j0.3$$

$$2 - j0.5$$

$$1.5 - j0.1$$

$$0.48 + j0.11$$

Lossless line with $Z_0 = 70 \Omega$ terminated in an open circuit,

Determine the sending end Impedance for the following lengths of line.


(i) $\lambda/8$

(ii) $\lambda/4$

(iii) $\lambda/2$

$$0.125 \lambda$$

$$0 + j0.1$$

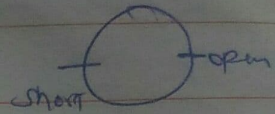

$$0.5 \lambda$$

$$j\infty$$

$$0.25 \lambda$$

$$0 + j0$$



Find the sending end impedance of the line with
 $Z_0 = 55 \Omega$ load impedance $115 + j75 \Omega$ length of
 line 1.183λ

$$Z_0 = 55 \Omega$$

$$Z_L = 115 + j75 \Omega$$

$$l = 0.983 \lambda$$

$$Z_{in} = \frac{115 + j75}{55} = 2.09 + j1.36$$

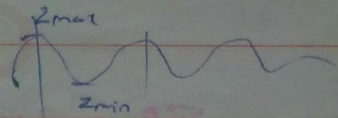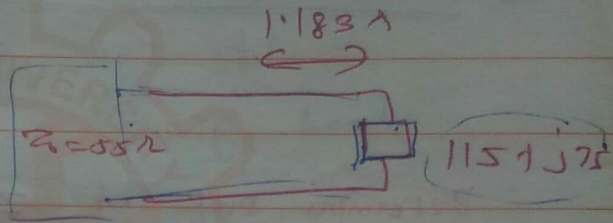

or 0.215λ

$$0.215$$

$$0.183$$

$$0.398$$


$$(0.48 - j0.65)$$

$$55 (0.48 - j0.65)$$

$$[26.4 - j35.75]$$

Find the load impedance at the end of
 $\lambda/8$ line if sending end impedance $(50 + j72)$
 with $Z_0 = 100 \Omega$.

$$Z_0 = 100 \Omega$$

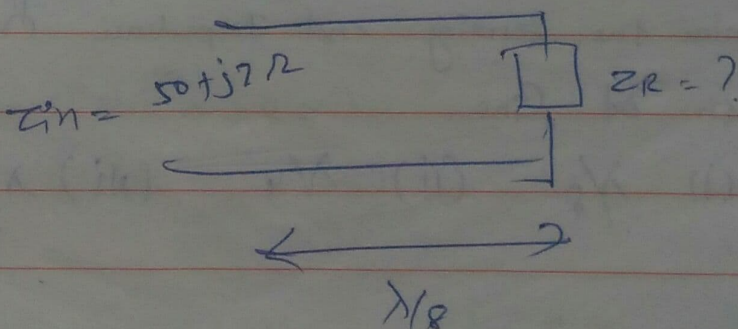

$$Z_0 = 100 \Omega$$

$$\frac{2 + j15}{2 - j15} =$$

$$Z_{in} = 50 + j12 \Omega$$

$$Z_{in} = \frac{Z_{in}}{Z_0} = \frac{50 + j12}{100}$$

$$= 0.5 + j0.12 \quad \text{at } 0.015 \lambda$$

Wavelength toward load.


$$\begin{array}{r} 0.125 \\ 0.015 \\ \hline 0.110 \end{array}$$

$$\begin{array}{r} 0.015 \\ 0.125 \\ \hline 0.110 \end{array}$$

$\lambda/8$

→ another $0.73 - j0.53$

$$Z_L = 73 - j53$$

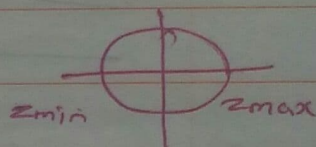


the VSWR is 5 with voltage min

occurring $\lambda/3$ from load. determine load

$$Z_{min} = \frac{1}{VSWR}$$

Impedance $Z_0 = 50 \Omega$

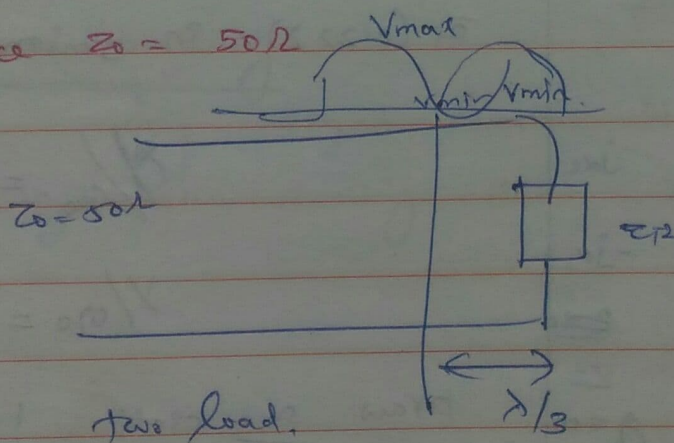

$$\begin{aligned} Z_{min} &= \frac{1}{VSWR} \\ &= \frac{1}{5} \\ &= 0.2 \end{aligned}$$

toward load

toward load 0.33λ


$$0.77 + j1.48$$

$$50 (0.77 + j1.48)$$

$$Z_L = 38.5 + j74$$

1x single stub matching at

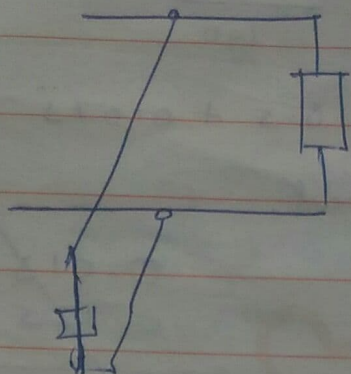
Stub out, R, L, C , length in $\lambda/2$



$$2.75 + j1.75$$

Location of stub = ?

and length of stub = ?

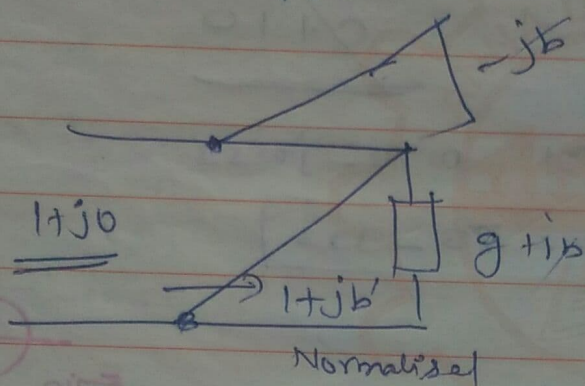

Resistive

on constant


value.

open

Admittance
 V_{min}
 V_{max}

$R=0$
 $X=0$

$R=\infty$
 $X=\infty$

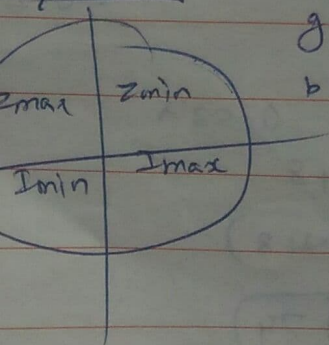

Note $2.75 + j1.75$

at (0.22λ) in Smith

$$V_{max}/V_{min} = 1 \text{ Circle}$$

$$V_{max}/V_{min} =$$

Draw SWR circle $1 +$
and V_{max}/V_{min}

Locate stub circle $(1 + j1.5)$
+

Stub susceptance as $+j1.5$

$$\begin{array}{r} \cancel{0.5} \\ - \cancel{0.324} \\ \hline \end{array}$$

Indurine shaptane -1.5 0.324

$$\begin{array}{r} \text{location of stub} \quad 0.324 \\ - 0.220 \\ \hline \end{array}$$

$$\text{location of stub} \quad \underline{\underline{0.102 \lambda}}$$

length of stub

+j1.5


$$\begin{array}{r} \text{length of stub} \quad 0.25 \lambda \\ \quad \quad \quad 0.156 \lambda \\ \hline 0.406 \lambda \\ \hline \end{array}$$

Double Stub matching

by changing location of stubs
In single stub matching from 2 stubs 90°

$\lambda/4$
distance

(Impedance Inversion)

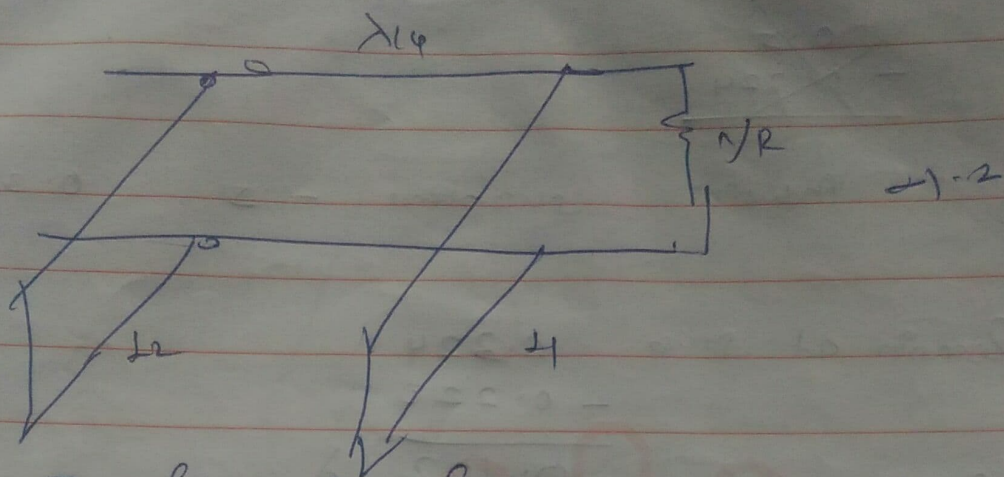


The line with load admittance of

$$Y/R = 0.4 - j1.2$$

0.4 Conductance

$-j1.2$

Inductive susceptance

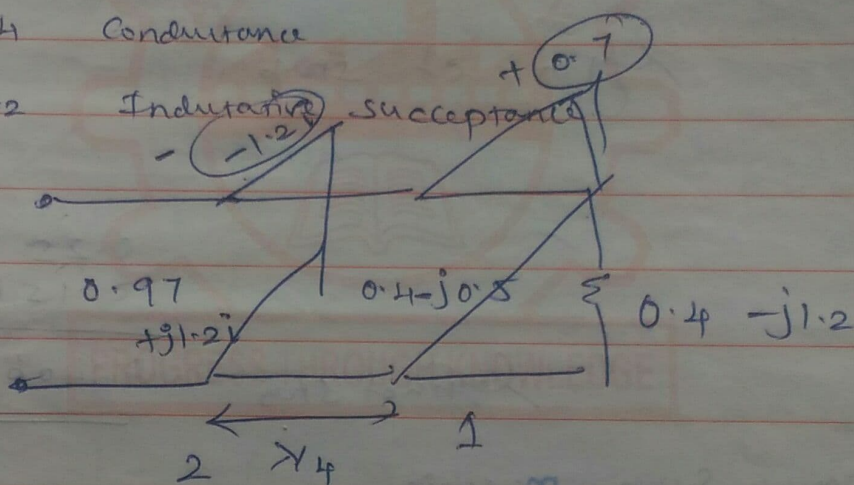

Unit circle
concept

$$\text{Not } 0.4 - j1.2$$

Stub 1 should not alter conductance

Hence

$$0.4 - j0.5$$

branch

length of Stub 1

equal to

Stub with susceptance

1

a) 0.7

$$\underline{\underline{+0.7}}$$

Cut at

$$0.098 \lambda$$

24

$$+ 0.25 \lambda$$

$$\underline{\underline{0.348 \lambda}}$$

Now Impedance to Admittance
by Inverse

Note

$$0.4 - j0.5j$$

to

$$0.97 + 1.2j$$

another row of $-1.2j$

Cancel

Hence

$$\text{cur at } \begin{array}{r} 0.36 \text{ A} \\ -0.25 \text{ A} \end{array}$$

$$\begin{array}{r} \text{Lynoh} \\ \text{of } \end{array} \begin{array}{r} 2\text{nd} \\ \text{(second step)} \end{array} \begin{array}{r} 0.11 \text{ A} \\ \hline \end{array}$$