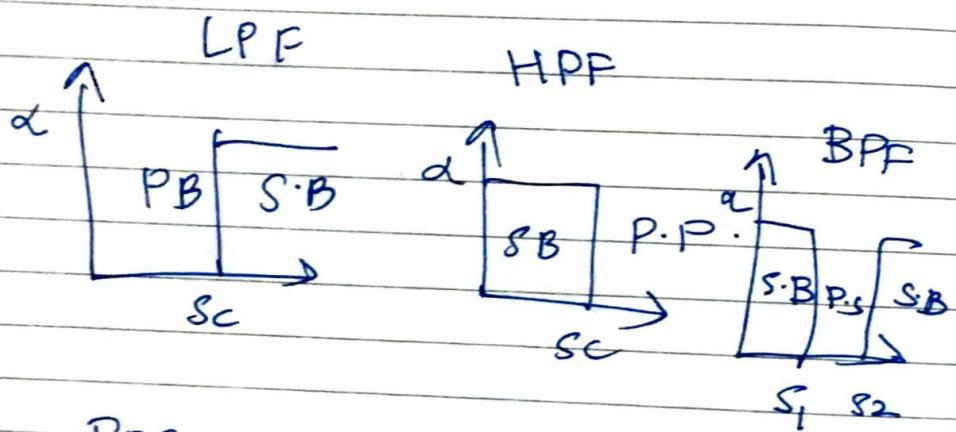


8/10.


Network Components.

filter:- A filter is a 4 terminal network designed with reactive elements. It is used to separate the electrical signals on basis of their signals.

Definition:



BSF

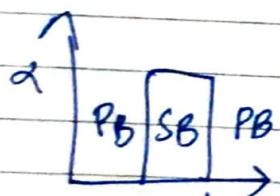

Due to losses in coils and capacitors, non zero attenuation exists in pass band and finite attenuation exists in stop band.

(ii) Propagation const. (γ) for a symmetrical reciprocal networks, γ is defined as natural logarithm of ratio of i/p to o/p current $P_2 \gamma = \log \left[\frac{I_1}{I_2} \right]$

$$\begin{aligned} P_1 &\rightarrow i/p \\ P_2 &= o/p \end{aligned}$$

P is complex no. = $\alpha + j\beta$

classmate

Date _____

(iii) α (proper) magnitudes b/w i/p & o/p quantity.

(iv) B (rad): Determines of the b/w i/p & o/p.


Characteristics

The behavior of any filter is calculated at any based on:-
 $Z_0, \gamma, \alpha, \beta$.

(i) Z_0 (Charac. Imp.)

Z_0 of 4 terminal sym. network is defined as its i/p imp. when such networks are connected at tandem (cascade). For sym. network Z_0 is referred as image impedance. For asym. network, Z_0 is referred as iterative imp.

charact. Imp. of sym. T-N/ ω .

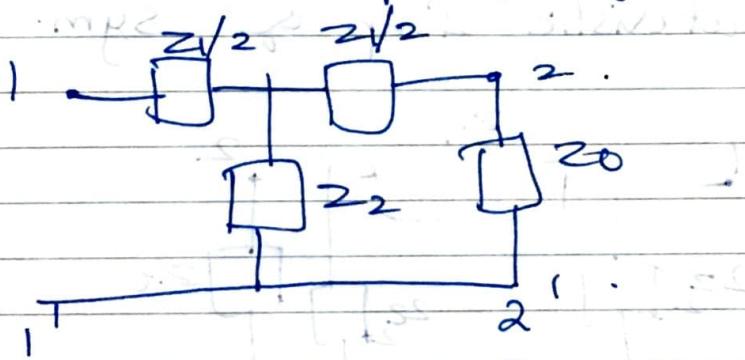

$$Z_{0T} = \frac{Z_1}{2} + Z_2 \parallel \left(\frac{Z_1}{2} + Z_0 \right)$$

$$= " + Z_2 \times \frac{\frac{Z_1}{2} + Z_0}{Z_2 + \frac{Z_1}{2} + Z_0}$$

$$\begin{aligned} Z_{0T} &= \underbrace{\frac{Z_1 Z_2}{2} + \frac{Z_1^2}{4}}_{Z_2 + \frac{Z_1}{2} + Z_0} + \frac{Z_1 Z_0}{2} + \frac{Z_1 Z_2 + Z_2 Z_0}{2} \\ &= \frac{Z_1 Z_2}{2} + Z_2 Z_0 + \frac{Z_1 Z_0}{2} + \frac{Z_1^2}{4} \end{aligned}$$

$$Z_2 + Z_1/2 + Z_0$$


$$\Rightarrow 20T \left(20 + \frac{z_1 + z_2}{2} \right) = 20 \left(z_2 + \frac{z_1}{2} \right) + \frac{z_1^2}{4} + z_1 z_2.$$

$$\Rightarrow 20 \left[1 - \left(z_2 + \frac{z_1}{2} \right) \right] = \frac{z_1^2}{4} + z_1 z_2 - 20T \frac{z_1}{2} + z_2 z_0$$

$$20 \left[20 + \frac{z_1}{2} + z_2 - z_2 - \frac{z_1}{2} \right] = \frac{z_1^2}{4} + z_1 z_2$$

$$20T = \sqrt{2z_2 T \frac{z_1^2}{4}}$$

Characteristic Imp of sym. π -network

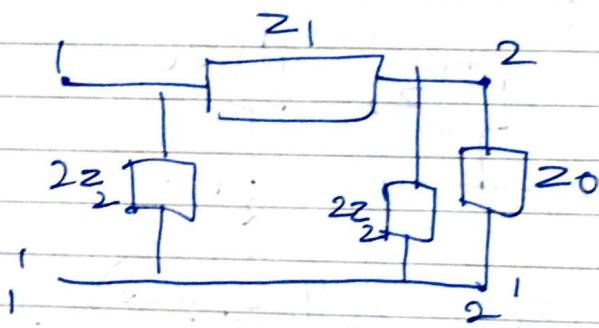

$$\frac{z_2 || z_0}{z_2 + z_0} = \frac{z_2 \times z_0}{z_2 + z_0}$$

$$\frac{2z_2 \times z_0 + z_1(z_2 + z_0)}{2z_2 + z_0} = \frac{2z_2 z_0 + 2z_2^2}{2z_2 + z_0} + z_1 z_0$$

$$\frac{2z_2 z_0 + 2z_1 z_2 + z_1 z_0 + (z_2)^2 + 2z_2 z_0}{(2z_2 z_0 + 2z_1 z_2 + z_1 z_0 + z_2)^2} = \frac{2z_2 z_0 + 2z_1 z_2 + z_1 z_0 + (z_2)^2 + 2z_2 z_0}{2z_2 + z_0 + z_2^2}$$

$$\Rightarrow u z_2^2 z_{20} + u z_1 z_2^2 + 2 z_2 z_1 z_{20} + 8 z_2^3.$$

$$z_{0T} = \boxed{\frac{z_1 z_2}{1 + \left(\frac{z_1}{u z_2}\right)}}$$


$$z_{0T} \times z_{0T} = z_1 z_2$$

Propagation const. of $T n/w \otimes \pi n/w$.
 $T n/w$.

$$P = \log_e \left(\frac{I_S}{I_R} \right)$$

$$I_R = I_S \left[\frac{z_2}{z_2 + \frac{z_1}{2} + z_{20}} \right]$$
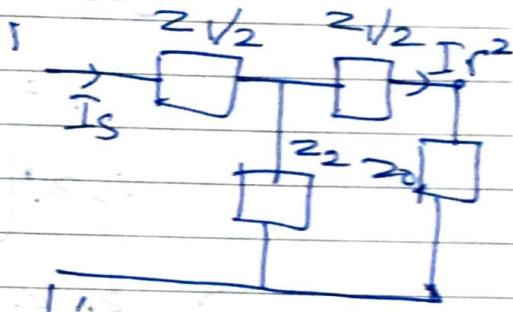
$$\frac{I_S}{I_R} = \frac{z_2 + \frac{z_1}{2} + z_{20}}{z_2}$$



$$= z_2 + \frac{z_1}{2} + \sqrt{z_1 z_2 + \frac{z_1^2}{4}}$$

$$\boxed{P = \log_e \left[\frac{z_2 + \frac{z_1}{2} + \sqrt{z_1 z_2 + \frac{z_1^2}{4}}}{z_2} \right]}$$

$$\text{let } x = \frac{z_2 + z_1/2}{z_2}$$


$$P = \log_e (x + \sqrt{x^2 - 1})$$

$$\boxed{P = \cosh^{-1}(x)}$$

$$\Rightarrow P = \cosh^{-1} \left[\frac{z_2 + z_1/2}{z_2} \right]$$

$$\Rightarrow P = \cosh^{-1} \left[1 + \frac{z_1}{2 z_2} \right]$$

Propagation const of a symmetrical Th.

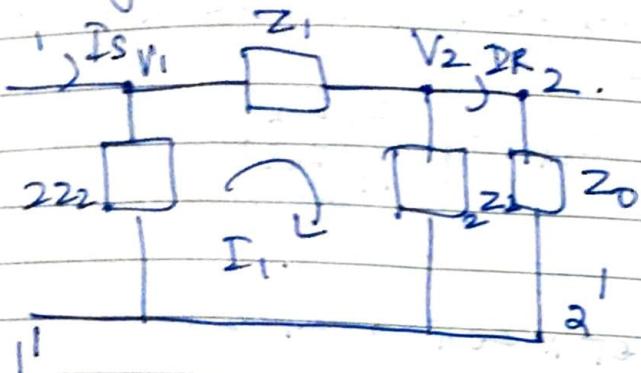

$$\frac{V_1}{z_0} + \frac{V_1 - V_2}{z_1} = I_S \Rightarrow \frac{V_2}{z_0} + \frac{V_2 + V_2 - V_1}{z_1} = I_S$$

$$V_2 \left[\frac{1}{z_0} + \frac{1}{z_1} + \frac{1}{z_2} \right] = \frac{V_1}{z_1} = 0$$

$$V_1 = z_1 V_2 \left[\frac{1}{z_0} + \frac{1}{z_1} + \frac{1}{z_2} \right]$$

$$V_2 z_1 \left[\frac{1}{z_0} + \frac{1}{z_1} \right] \left[\frac{1}{z_0} + \frac{1}{z_2} \right] - \frac{V_2}{z_1} = I_S$$

$$I_R z_0 z_1 \left[\frac{z_0 + z_2}{z_0 z_2} \right] \left[\frac{z_1 + z_2}{z_1 z_2} \right] - \frac{I_R z_0}{z_1} = I_S$$

$$I_R \left\{ \frac{z_0 z_1 [z_0 + z_2][z_1 + z_2]}{z_0 z_1 z_2 z_0} - \frac{z_0}{z_1} \right\} = I_S$$

$$\frac{I_S}{I_R} = "$$

$$\frac{I_S}{I_R} = \frac{(z_1^2 + z_2 z_2)(z_0^2 z_1 + z_2 z_2 z_0 z_1) - 4 z_0^2 z_2^2 z_1}{4 z_0^2 z_2^2 z_1}$$

$$= z_1^3 z_0^2 + z_2 z_2 z_0 z_1^3 + z_1^2 z_0^2 z_2 + 4 z_2^2 z_1^2 z_0 - 4 z_0^2 z_2^2 z_1$$

~~$$\rho = \log_e \left(\frac{I_S}{I_R} \right)$$~~

$$\begin{aligned}
 P &= \log_e \left(\frac{Z_2}{Z_{22}} \right) \\
 &= \log_e \left[\frac{Z_2^2 + Z_2 Z_{22}}{Z_{22}^2} + \frac{\frac{Z_2^2}{Z_{22}^2}}{1 + \frac{Z_2}{Z_{22}}} \right] \\
 &= \log_e \left[\left(1 + \frac{Z_2}{Z_{22}} \right) + \sqrt{1 + \frac{Z_2}{Z_{22}} \left(\frac{Z_2 + Z_{22}}{Z_{22}} \right)^2} \right] \\
 &= \log_e \left[\left(1 + \frac{Z_2}{Z_{22}} \right) + \sqrt{1 + \frac{Z_2^2 + Z_2 Z_{22}}{Z_{22}^2}} \right] \\
 &= \log_e \left[\left(1 + \frac{Z_2}{Z_{22}} \right) + \frac{Z_2 Z_{22} \sqrt{1 + \frac{Z_2}{Z_{22}}}}{Z_{22}} \right] \\
 &= \log_e \left[\left(1 + \frac{Z_2}{Z_{22}} \right) + \frac{Z_2 Z_{22} \sqrt{1 + \frac{Z_2}{Z_{22}}}}{Z_{22}} \right]
 \end{aligned}$$

Put $x = \frac{Z_2 + Z_{22}}{Z_{22}}$

Put $\log_e [x + \sqrt{x^2 - 1}] = \cosh^{-1}(x)$.

$$P = R_{22} \cosh^{-1} \left[1 + \frac{Z_2}{Z_{22}} \right]$$

Balanced n/w :- It is the one in which the corresponding Series impedance elements are identical and these elements are symmetrical with respect to the ground.


Symmetrical n/w :- It is the one in which the electrical properties are unaffected by interchanging the i/p and o/p terminals.

Equivalent n/w :- Two n/w's having same characteristic impedance and same propagation constant are said to be equivalent networks.

Constant k filter :- A constant k filter is a T / π n/w in which the series and shunt imp Z_1 and Z_2 are connected by the relationships $[Z_1 Z_2 = R_k^2]$ where $R_k = A$ real const. (i.e., resistance is independent of frequency).

Re it known as design 1
nominal impedance.

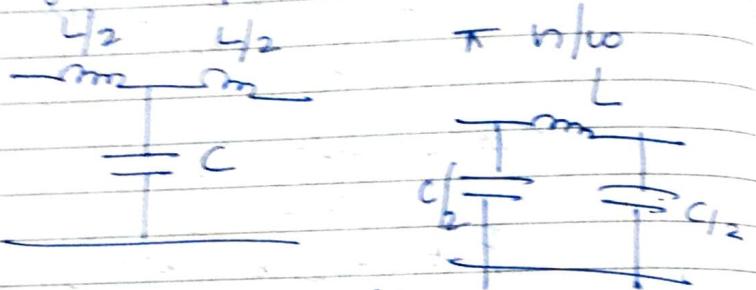→ Low pass filters:- since series
and shunt impedance of both
 T and π are same, they
will have the same design
impedance and cut-off freq.
- only $T = n/10$



$$Z_1 = j\omega L \quad Z_2 = j\omega C$$

$$Z_1 Z_2 = \frac{L}{C} = R_o^2 (\omega_0^2)$$

$$R_o = \sqrt{\frac{L}{C}}$$

To find the cut off freq:-

To find the lower cut-off


frequency

$$j\omega L - \frac{4j}{\omega C} = 0 \Rightarrow \left\{ \omega L = \frac{4}{\omega C} \right.$$

$$\omega^2 = \frac{4}{LC} \Rightarrow \omega = \frac{2}{\sqrt{LC}}$$

$$2\pi f_c = \frac{2}{\sqrt{LC}}$$

$$f_c = \frac{1}{\pi \sqrt{LC}}$$

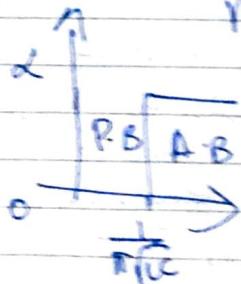

To find $Z_0(\omega)$
 $Z_{0T} = \sqrt{Z_1 Z_2 + Z_0^2}$

$$Z_0^2 = 4 - 4/C$$

$$Z_{0T} =$$

$$Z_{0T} = R_o$$

w.r.t

Design eqns
w.r.t $2\pi f_c$

At the

$$\Rightarrow j\omega L$$

\Rightarrow

$$\textcircled{1} \Rightarrow 4/C$$

$$\textcircled{2} \Rightarrow R_o$$

$$L = ?$$

To find z_0 (characteristic imp.):-

$$z_{OT} = \sqrt{z_1 z_2 + \frac{z_1^2}{4}} = \sqrt{\frac{L}{C} - \frac{\omega_c^2 L^2}{4}}$$

$$z_0^2 - \frac{L}{C} = \frac{\omega_c^2 L^2}{4}$$

$$z_{OT} = \sqrt{\frac{L}{C} \left[1 - \frac{\omega_c^2 L^2}{4} \right]}$$

$$z_{OT} = R_0 \sqrt{1 - \left(\frac{f}{f_c} \right)^2}$$

$$W.K.T \quad z_{OT} \cdot z_{OT} = z_1 z_2$$

$$z_{OT} = \sqrt{\frac{L}{C}}^2$$

$$= R_0 \sqrt{1 - \left(\frac{f}{f_c} \right)^2}$$

$$z_{OT} = \frac{R_0}{\sqrt{1 - \left(\frac{f}{f_c} \right)^2}}$$

Design eqns for LP.F

$$W.K.T \quad z_1 z_2 = \frac{L}{C} = R_0^2 (R_0^2)$$

$$\Rightarrow R_0 = \sqrt{L/C} \rightarrow ①$$

At the upper cut-off frequency, $z_1 = -z_2$

$$\Rightarrow j\omega L = \frac{4i}{\omega C}$$

$$\Rightarrow \omega^2 LC = 4 \rightarrow ②$$

$$① \Rightarrow L/C = R_0^2 \Rightarrow L = R_0^2 C$$



$$② \Rightarrow R_0^2 C^2 = \frac{4}{\omega^2} \Rightarrow C = \frac{2}{R_0 \omega}$$

$$L = R_0^2 \frac{2}{\omega C}$$

High Pass filter

CLASSMATE
Date _____
Page _____
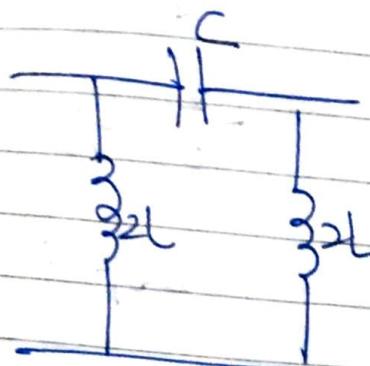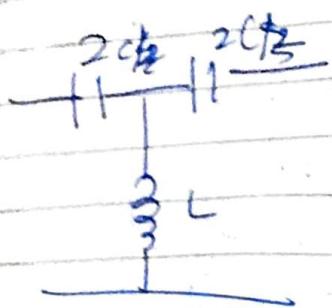
$$\tau = n/\omega \quad \pi = n/\omega.$$



$$Z_1 = -j\omega C$$

$$Z_2 = j\omega L$$

$$Z_1 Z_2 = \frac{L}{C} = R_o^2 (R_t^2) \Rightarrow R_o = \sqrt{\frac{L}{C}}$$

$$\frac{Z_1}{4Z_2} = \frac{-j}{\omega C (4j\omega L)} = \frac{-1}{4\omega^2 LC}$$

$$\boxed{\frac{Z_1}{4Z_2} = \frac{-1}{4\omega^2 LC}}$$

To find cut-off frequency.

By applying the condition of P.B, $\frac{Z_1}{4Z_2} = 1$ for f_1 (lower cut-off)

$\frac{Z_1}{4Z_2} = 0$ for f_2 (higher cut-off).


$$\Rightarrow \frac{-1}{4\omega^2 LC} = 1 \Rightarrow \omega = \frac{1}{2\sqrt{LC}} \Rightarrow f_1 = \frac{1}{4\pi\sqrt{LC}}$$

$$\Rightarrow \frac{-1}{4\omega^2 LC} = 0$$

$$\Rightarrow \boxed{f_2 = \infty}$$

To find Z_o :
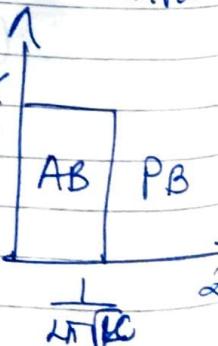
$$Z_o = \sqrt{Z_1 Z_2 + Z_1^2} = \sqrt{\frac{L}{C} + \frac{-1}{4\omega^2 LC}}$$



$$Z_{OT} = \boxed{\frac{R_o}{C_o + j\omega C}}$$

charge

$$\frac{1}{4\pi\epsilon_0 R^2 \times f_C^2 \times C_L}$$

$$\frac{1}{4\pi\frac{2\pi}{f_C} \frac{4\pi\epsilon_0}{C_L}}$$

$$Z_{OT} \cdot Z_{OT} = Z_{Z_2}$$

$$Z_{OT} = \frac{L}{C}$$

$$\boxed{\sqrt{\frac{L}{C}} \left[\sqrt{1 + \left(\frac{R_o}{f_C} \right)^2} \right]}$$

$$\Rightarrow Z_{OT} = \frac{R_o}{\sqrt{1 + \left(\frac{R_o}{f_C} \right)^2}}$$

Design eqn of h-pf.

$$W \cdot k_t : R_o^2 = L/C \rightarrow ①$$

$$At \rightarrow \text{lower cut-off freq } \omega = \frac{1}{2\sqrt{LC}} \rightarrow ②$$

$$① \rightarrow L = C R_o^2$$

$$② \rightarrow Z_1 = \frac{1}{j\omega} \rightarrow$$

$$j\omega/L = R_o/j\omega L$$

$$\omega^2 = \frac{1}{4LC} \Rightarrow \omega = \frac{1}{2\sqrt{LC}}$$

$$C = \frac{1}{2R_o\omega}$$

$$C = \frac{1}{2R_o^2\pi f_C} \Rightarrow$$

$$\boxed{C = \frac{1}{4\pi f_C R_o}}$$

$$\boxed{L = \frac{R_o}{4\pi f_C}}$$

10/10/2020

CLASSMATE

Date _____
Page _____

$$\sin \frac{\gamma}{2} = \sqrt{\frac{z_1}{2z_2}}$$

Book

chapter -17. filters and attenuation

Att. factor and of factor of a
const. k low-pass filter.

wkt: $\cos \beta = 1 + \frac{z_1}{2z_2}$.

$$z_1 = j\omega L + z_2 = -j\omega C$$

$$\cos \beta = 1 + \frac{j\omega L \times \omega C}{2 - j}$$

$$1 - \frac{\omega^2 LC}{2}$$

$$= 1 - \frac{\frac{1}{4\pi^2} \cdot \frac{1}{LC}}{\frac{1}{2}}$$

$$\cos \beta = 1 - \frac{2\omega^2}{\omega_c^2}$$

$$\beta = \cos^{-1} \left[1 - \frac{2\omega^2}{\omega_c^2} \right]$$

$$\beta = 28.37 \frac{\omega}{\omega_c} \text{ rad} \quad (\cos \beta = 1 - 28.37^2 \beta / 2)$$

$$\cosh \alpha = - \left[1 + \frac{z_1}{2z_2} \right]$$

$$= - \left[1 + \frac{j\omega L \cdot \omega C}{2 - j} \right]$$

$$= \left[1 - \frac{1}{2} \omega_0^2 L C \right]$$

$$= \left[1 - \frac{2\omega^2}{\omega_0^2} \right] = \frac{2\omega^2}{\omega_0^2} - 1.$$


$$\boxed{\begin{array}{l} \alpha = \cosh^{-1} \left[\frac{2(\omega)}{\omega_0} \right]^2 - 1 \quad | \text{ nepes.} \\ \alpha = 2 \cosh^{-1} \left(\frac{\omega}{\omega_0} \right) \quad | : \cosh x \\ \qquad \qquad \qquad = -1 + 2 \cosh^2 \frac{x}{2} \end{array}}$$

+ Hig P.F.


$$Z_1 = \frac{-j}{\omega_0} \quad Z_2 = j\omega L$$

Band pass filter.

T-section.

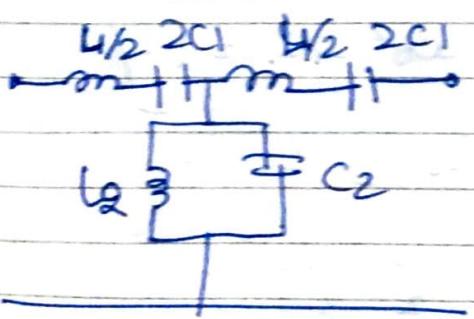

π section.

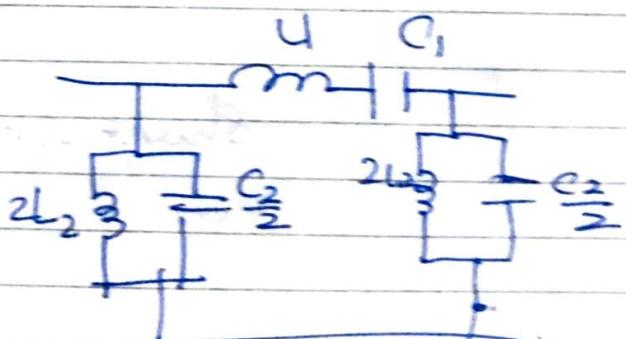

$$Z_1 = j\omega L + \frac{1}{j\omega C_1}$$

$$j \left(\omega L + \frac{1}{\omega C_1} \right)$$

$$Z_2 = \frac{j\omega L_2 \times \frac{1}{j\omega C_2}}{j\omega L_2 + \frac{1}{j\omega C_2}} = \frac{\frac{L_2}{C_2}}{j(\omega L_2 + \frac{1}{\omega C_2})}$$

$$Z_{22} = j\left(\omega L_1 - \frac{1}{\omega C_1}\right) \cdot \frac{L_2}{C_2 j(\omega L_2 + \frac{1}{\omega C_2})}$$

$$= \frac{[\omega^2 L_1 C_1 - 1] L_2}{\omega C_1 C_2 [\omega^2 L_2 C_2 - 1]} \cdot \frac{C_2}{C_1}$$

~~At resonance $X_L = X_C$~~
~~Series arm: $j\omega L_1$~~

$$= \frac{\omega^2 L_1 L_2 C_1 - L_2}{C_1 [\omega^2 L_2 C_2 - 1]}$$

$$Z_{22} = \frac{L_2 [\omega^2 L_1 C_1 - 1]}{C_1 [\omega^2 L_2 C_2 - 1]}$$

~~At resonance $X_L = X_C$~~
~~Series arm: $j\omega L_1 = \frac{1}{j\omega C_1}$~~

$$\boxed{\omega^2 L_1 C_1 = 1}$$

Shunt arm: $j\omega L_2 = \frac{-1}{j\omega C_2}$

$$\Rightarrow \boxed{\omega^2 L_2 C_2 = 1}$$

$$\therefore L_1 C_1 = L_2 C_2$$

$$\frac{L_2}{C_1} = \frac{L_1}{C_2} = R_0^2$$

$$\begin{aligned} z_1 &= -1 \Rightarrow z_1 = -4z_2 \\ u_{22} & \quad z_1^2 = -4z_1 z_2 \\ & \quad = -4R_o^2. \end{aligned}$$

$$z_1 = \pm j\sqrt{2}R_o$$

z_1 is fine from a particular frequency
and is a -ve for some other
frequency. W.K.T.

$$z_1 = j \left[\frac{\omega^2 L_1 C_1 - 1}{\omega C_1} \right] = j\sqrt{2}R_o$$

$$2R_o \omega C_1 = \omega^2 L_1 C_1 - 1.$$

$$\omega^2 L_1 C_1 - 2R_o \omega C_1 - 1 = 0.$$

$$\therefore \omega = \frac{2R_o C_1 \pm \sqrt{4R_o^2 C_1^2 + 4L_1 C_1}}{2L_1 C_1}$$

$$= \frac{2R_o C_1 \pm \sqrt{R_o^2 C_1^2 + L_1 C_1}}{2L_1 C_1}$$

$$f_1 = \frac{R_o + \sqrt{R_o^2 + 4/C_1}}{2\pi L_1}$$

Case(ii) when z_1 acts as in -ve
imp.

$$1 - 2jR_o = j \left[\frac{\omega^2 L_1 C_1 - 1}{\omega C_1} \right]$$

$$\Rightarrow -2R_o \omega C_1 = \omega^2 L_1 C_1 - 1$$

$$\omega^2 L_1 C_1 + 2R_o \omega C_1 - 1 = 0.$$

$$\omega = \frac{-2R_o C_1 \pm \sqrt{4R_o^2 C_1^2 + 4L_1 C_1}}{2L_1 C_1}$$

$$f_2 = \frac{-R_o + \sqrt{R_o^2 + L_1/C_1}}{2\pi L_1}$$

$$f_1 f_2 = \frac{(R_0 + \sqrt{R_0^2 + 4L_1 C_1})(-R_0 + \sqrt{R_0^2 + 4L_1 C_1})}{4\pi^2 L_1^2}$$

$$f_0^2 = \frac{1}{4\pi^2 L_1 C_1}$$

$$f_0 = f_1 f_2$$

$$f_0 = \frac{1}{2\pi\sqrt{L_1 C_1}}$$

Design eqn. for. B.P.F.

$$1 - \omega_2^2 L_1 C_1 = 2R_0 \omega_2 C_1$$

$$1 - \frac{\omega_2^2}{\omega_0^2} = 2R_0 \omega_2 C_1$$

$$1 - \frac{f_2^2}{f_0^2} = 4\pi R_0 f_2 C_1$$

$$W.K.T. \quad f_0^2 = f_1 f_2$$

$$1 - f_2/f_1 = 4\pi R_0 f_1 f_2 C_1$$

$$C_1 = \frac{f_1 - f_2}{4\pi R_0 f_0^2}$$

$$L_2 = \frac{R_0 \pi (f_1 - f_2)}{4\pi R_0 f_0^2}$$

$$(ii) \quad L_1 C_1 = R_0^2$$

$$L_1 = R_0^2 \frac{4\pi R_0 f_0^2}{f_1 - f_2}$$

$$L_1 C_1 = L_2 C_2 = R_0^2$$



$$L_2 = R_0^3 \cdot \frac{4\pi}{f_1 - f_2} \left(\frac{1}{4\pi C_1} \right)$$

$$= \frac{R_0^3 / R_0^2}{\pi f_1 f_2} = \frac{R_0}{\pi f_1 f_2}$$

$$C_2 = \frac{1}{R_0 \pi (f_1 - f_2)}$$

Band stop filter

T section

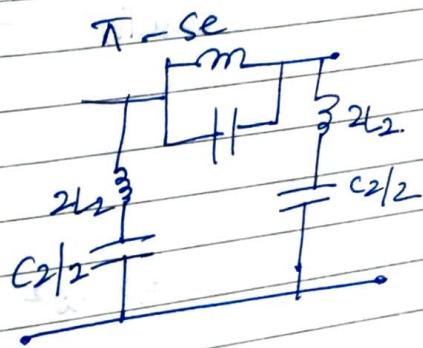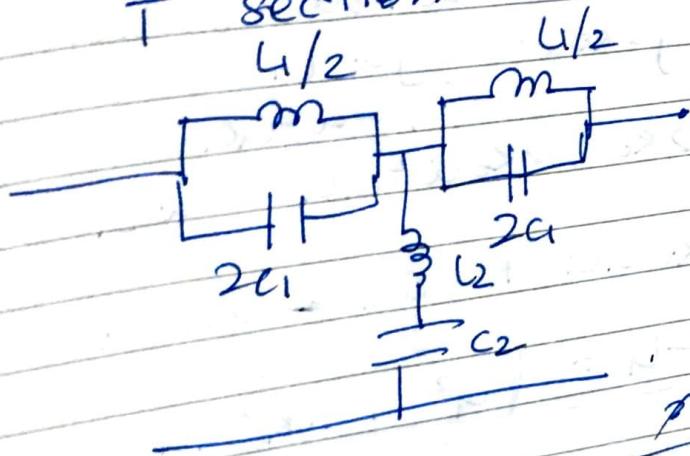

$$Z_1 = \left[\frac{j\omega L_1 \times \frac{R}{2j\omega C_1}}{j\omega L_2 + \frac{R}{2j\omega C_1}} \right] = \frac{1}{4C_1} \frac{-2\omega^2 L_1 C_1 + 2}{4j\omega}$$

$$Z_1 = \frac{j\omega L_1 w}{w(1 - \omega^2 C_1)}$$

$$Z_2 = j\omega L_2 + \frac{1}{j\omega C_2} = -\frac{\omega^2 L_2 C_2 + 1}{j\omega C_2}$$

$$\Rightarrow Z_1 = \frac{j\omega L_1}{1 - \omega^2 C_1} \quad \therefore Z_2 = \frac{j\omega L_2}{1 - \omega^2 C_1} \times \frac{1 + \omega^2 L_2 C_2}{j\omega C_2}$$

$$Z_{22} = \frac{U}{I} \left[\frac{\omega^2 L^2 C_2 - 1}{\omega^2 R_2 C_2 - 1} \right]$$

At resonance $\chi_L = \chi_C$

$$\text{series arm joc} = \frac{-1}{j\omega C_2}$$

$$4C_2 = L_2 C_2 = \omega_0^2$$

$$\frac{Z_1}{Z_{22}} = -1 \Rightarrow Z_1 = -4Z_{22}$$

$$Z_1^2 = -4Z_{22}^2$$

$$\Rightarrow Z_1 = \pm j 2\omega_0$$

(exh) Z_1 takes active value

$$j 2\omega_0 = \frac{j\omega_0 L_1}{1 - \omega_0^2 R_2 C_2}$$

$$2\omega_0 - 2R_2 \omega_0^2 L_1 C_2 = \omega_0 L_1$$

$$\Rightarrow \omega^2 2R_2 L_1 C_2 + \omega_0 L_1 - 2\omega_0 = 0$$

$$\Rightarrow f_2 = \frac{-1 \pm \sqrt{1 + 16R_2^2 C_2}}{2\pi(R_2 C_2) R_0}$$

$$= \frac{-1 \pm \sqrt{1 + 16R_2^2 C_2}}{2\pi R_2 C_2}$$

$$\therefore f_2 = \frac{-1 + \sqrt{1 + 16R_2^2 C_2}}{2\pi R_2 C_2}$$

$$f_1 f_2 = \frac{1 + 16R_2^2 C_2}{64\pi^2 R_2^2 C_2^2} - 1$$

$$f_2^2 = \frac{1}{4\pi^2 C_2} \Rightarrow f_0 = \frac{1}{2\pi f_2 C_2}$$

$$\omega = -1 \pm \omega_0 \sqrt{1 - 2R_2^2 \frac{C_2}{C}}$$

$$f_1 = -1 + \frac{4\pi R_0^2 C_1}{L} \quad \text{---}$$

Design Equation:-

$$w_{1,2} = 2\pi c_1 - 2\pi c_2 \omega^2 L_1$$

$$\Rightarrow w_{1,2} = 2\pi c_1 - 2\pi \left(\frac{\omega^2}{R_0^2} \right)$$

$$w_{1,2} = 2\pi c_1 \left[1 - \frac{\omega^2}{R_0^2} \right]$$

$$L_1 = \frac{2\pi c_1}{\omega} \left[1 - \frac{\omega^2}{R_0^2} \right]$$

$$= \frac{R_0}{\omega f_1} \frac{(Af_2 - f_1^2)}{Af_2}$$

$$L_1 = \frac{R_0}{\omega f_1^2} (Af_2 - f_1^2)$$

$$C_2 = \frac{f_2 - f_1}{R_0 \omega f_1^2}$$

$$f_0^2 = \frac{1}{4\pi^2 L_1 \omega}$$

$$C_1 = \frac{1}{4\pi^2 R_0 (f_2 - f_1) \omega}$$

$$C_1 = \frac{1}{4\pi R_0 (f_2 - f_1)}$$

$$L_2 = \frac{R_0}{4\pi (f_2 - f_1)}$$

CHINMAYA V
CHENNAI

TM mode \rightarrow magnetic field = 0.

$$(H_3 = 0)$$

$$\nabla^2 E = \Delta^2 E$$

$$\Rightarrow \frac{\partial^2 E_z}{\partial x^2} + \frac{\partial^2 E_z}{\partial y^2} + h^2 E_z = 0$$

$$E_z(x, y, z) = E_z^0(x, y) e^{-k_z z}$$

$$E_z^0 = XY$$

$$\frac{\partial^2 E_z^0}{\partial x^2} = \frac{\partial^2 XY}{\partial x^2}, \frac{\partial^2 E_z^0}{\partial y^2} = \frac{X \partial^2 Y}{\partial y^2}$$

$$\frac{Y \partial^2 X}{\partial x^2} + \frac{X \partial^2 Y}{\partial y^2} + h^2 XY = 0$$

\div by $X \cdot 2 \cdot Y$

$$\Rightarrow \frac{1}{X} \frac{\partial^2 X}{\partial x^2} + \frac{1}{Y} \frac{\partial^2 Y}{\partial y^2} + h^2 = 0$$

$$\frac{1}{X} \frac{\partial^2 X}{\partial x^2} = -h^2 \underbrace{\frac{\partial^2 Y}{\partial y^2}}_{= A^2} = -h^2 + A^2$$

$$\frac{\partial^2 X}{\partial x^2} = h^2 - A^2$$

$$\frac{\partial^2 X}{\partial x^2} + B^2 X = 0 \quad B^2 = h^2 - A^2$$

$$\text{Solv: } Y = C_1 \cos Bx + C_2 \sin Bx$$

$$\frac{\partial^2 Y}{\partial y^2} + A^2 Y = 0 \Rightarrow Y = C_3 \cos Ay + C_4 \sin Ay$$

$$E_z^0 = XY = C_1 C_3 \cos Bx \cos Ay$$

$$+ C_1 C_4 \sin Ay \cos Bx$$

$$+ C_2 C_3 \cos Ay \sin Bx + C_2 C_4 \sin Ax \\ \sin Ay$$

Boundary conditions:-

$$E_z = 0 \text{ at } x=0, x=a \Rightarrow B = \frac{m\pi}{a}$$

$$\int_b^0 Y = 0 \Rightarrow y = b \downarrow A = \frac{n\pi}{b}$$

$$C_2 = 0, C_3 = 0.$$


$$E_z^0 = C_1 \sin \frac{m\pi}{a} x \sin \frac{n\pi}{b} y$$

$$E_x^0 = -\frac{\gamma}{h^2} \frac{\partial E_z}{\partial z} = \cancel{j \omega \mu} \frac{\partial H_z}{\partial y} \text{ field component}$$

$$= -\frac{\gamma}{b^2} \frac{\partial}{\partial z} \left[C_1 \sin \frac{m\pi}{a} x \sin \frac{n\pi}{b} y \right]$$

$$= \frac{j\beta}{h^2} C_1 \sin \frac{m\pi}{a} x \sin \frac{n\pi}{b} y \cos \left(\frac{m\pi}{a} z \right)$$
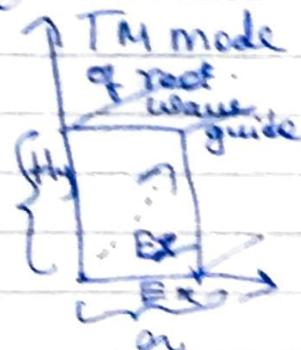
$$H_y^0 = -j \frac{\omega \epsilon c}{h^2} B \cos \left(\frac{m\pi}{a} x \right) \sin \left(\frac{m\pi}{b} y \right)$$



other parameters.

$$\omega^2 = r^2 + \omega^2 \mu E$$

$$\omega^2 = A^2 + B^2$$


$$\bar{D} = \sqrt{A^2 + B^2 - \omega^2 \mu E}$$

$$= \sqrt{\left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2 - \omega^2 \mu E}$$

at low freq $\bar{D} = \omega + j\beta = \text{real}$
 $\bar{D} = \omega + 0$.

@ high freq,
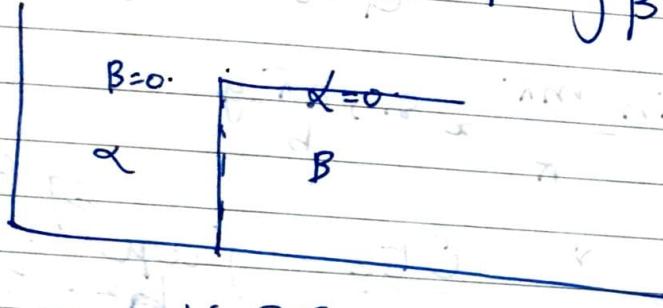
$$\gamma = j\beta \quad (\text{no real component})$$



HPF

finding cut-off frequency.

$$\omega^2 \mu E = \left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2$$

$$\Rightarrow f_L = \frac{1}{2\pi\sqrt{\mu E}} \sqrt{\left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2}$$

cut off λ .

$$\lambda_c = \frac{c}{f_c} = \frac{2\pi}{\sqrt{\left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2}}$$

$$c = \frac{1}{\sqrt{\mu E}}$$

$$V_p = \frac{\omega}{P} = \frac{v_0}{2\pi R E_0 \sin(\theta)}$$

$$\lambda_g = \frac{2\pi}{P}$$

$$y = \frac{d\phi}{dt}$$

Attenuation of TE₀₁ mode
At z, H_x, H_y

$$H_x = j\omega c \sin\left(\frac{\pi}{\lambda_g} z\right)$$

$$H_y = c \cos\left(\frac{\pi}{\lambda_g} z\right)$$

$$E_z = -j\omega \mu c \sin\left(\frac{\pi}{\lambda_g} z\right)$$

$$P_{avg} = \frac{1}{2} \operatorname{Re}[\vec{S} \cdot \vec{H}] \int dz \\ = \frac{1}{2} \operatorname{Re} \left[\left(\frac{\omega^2}{c} \right) \int dz \sin^2 \left(\frac{\pi}{\lambda_g} z \right) \right]$$

$$P_{avg} = \left(\frac{\omega^2}{c} \right) \frac{1}{2} \int dz$$

$$P_{avg} = 2 \left[\ln(1 + e^{-\alpha z}) + \alpha z \right]$$

CHINMAYA VILLAGE
CHENNAI

$$P_e(x=0) = \frac{1}{2} \int_0^b |Hy|^2 + |Hz|^2 R_s dy$$

$$= \frac{1}{2} \int_0^b c^2 R_s dy = \frac{b}{2} c^2 R_s$$

$$P_i(y=0) = \frac{1}{2} \int$$

$$= \frac{R_s}{2} \left[\frac{b^2 a}{2} + \left(\frac{\beta a c}{\pi} \right)^2 \frac{a}{2} \right]$$

$$\alpha = \frac{P_{log}}{P_{avg.}} = 2 \left[\frac{b}{2} c^2 R_s + R_s / 2 \left(\frac{c^2 a}{2} \right) \right]$$

$$1 + \left(\frac{\beta a}{\pi} \right)^2 = \left(\frac{f}{f_c} \right)^2$$

$$\alpha_{10} = R_s \left[1 + \frac{2b}{a} \left(\frac{f_c}{f} \right)^2 \right] \frac{b}{b \sqrt{1 - \left(\frac{f_c}{f} \right)^2}}$$

Weber