

INTERNAL ASSESSMENT - I

TRANSMISSION LINES AND WAVEGUIDES

19/9/20
Saturday

Padmaja Manikandan
2018105040
BE - ECE

Part - B :-

6)b) Lossless transmission line:

(i)

A transmission line is lossless if the conductors of the line are perfect ($\sigma_c \rightarrow \infty$) and the dielectric medium separating them is lossless ($\sigma \cong 0$). For such line,

$R = 0 = G$ is the necessary condition,

Then,

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = \alpha + j\beta$$

$\therefore R = 0 = G,$

$$\gamma = \sqrt{(j\omega L)(j\omega C)} = \alpha + j\beta = j\omega\sqrt{LC}$$

$$\Rightarrow \alpha = 0, \beta = \omega\sqrt{LC}, u = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} = f\lambda$$

$$\text{Also, } Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = R_0 + jX_0 = \sqrt{\frac{L}{C}}$$

$$\Rightarrow X_0 = 0, Z_0 = R_0 = \sqrt{\frac{L}{C}} //$$

6)b

$$ii) Z_i = 200 \Omega, Z_L = 600 - j150 \Omega$$

$$Z_0 = 400$$

$$\text{Normalised } Z_L = \frac{600 - j150}{200} = 3 - j(3/4)$$

$$\begin{aligned} \Gamma &= \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{3 - j(0.75) - 400}{3 - j(0.75) + 400} = \frac{-397 - j(0.75)}{403 - j(0.75)} \\ &= \frac{[-397 - j(0.75)][403 + j(0.75)]}{(403)^2 + (0.75)^2} = \frac{159990.4375 - j(1600)}{162408.4375} \\ &= \frac{159990.4375 - j(1600)}{162408.4375} \end{aligned}$$

$$\Gamma = 0.985 - j(0.00369)$$

$$|\Gamma| = \sqrt{0.97044 + 0.00001}$$

$$= 0.98511$$

$$\begin{aligned} \text{Return loss} &= 20 \log(0.98511) = 20 \times (-0.006511) \\ &= \underline{\underline{-0.130 \text{ dB}}} \end{aligned}$$

$$\begin{aligned} \text{Reflection loss} &= 20 \log(1 - \Gamma^2) \\ &= 20 \log(0.0295) = \underline{\underline{-15.295 \text{ dB}}} \end{aligned}$$

7)

1. Normalised impedance = $0.5 + 0.6j = A$

VSWR = 2.8

2. Normalized admittance
= $B = (0.84 - 0.96j)$

3. $S_1 = 0.84 + 0.01j$, $S_2 = 0.84 + 2j$

4. $S_1 - B = 0.84 + 0.01j - 0.84 + 0.96j = 0.97j$

$S_2 - B = 0.84 + 2j - 0.84 + 0.96j = 2.96j$

5. Since D_1 is nearer to the load surface


length of first stub = 0.35λ short circuit to D_1

6. OS_1 as radius, mark $TP_1 (1 + 0.21j)$ and $TP_2 (1 - 0.21j)$ as intersection of unit resistance circle and OS_1 radius circle.

7. As TP_1 is nearer to the load ^{reference} surface

Hence, length of second stub = 0.217λ
Short circuit to D_3

(3)

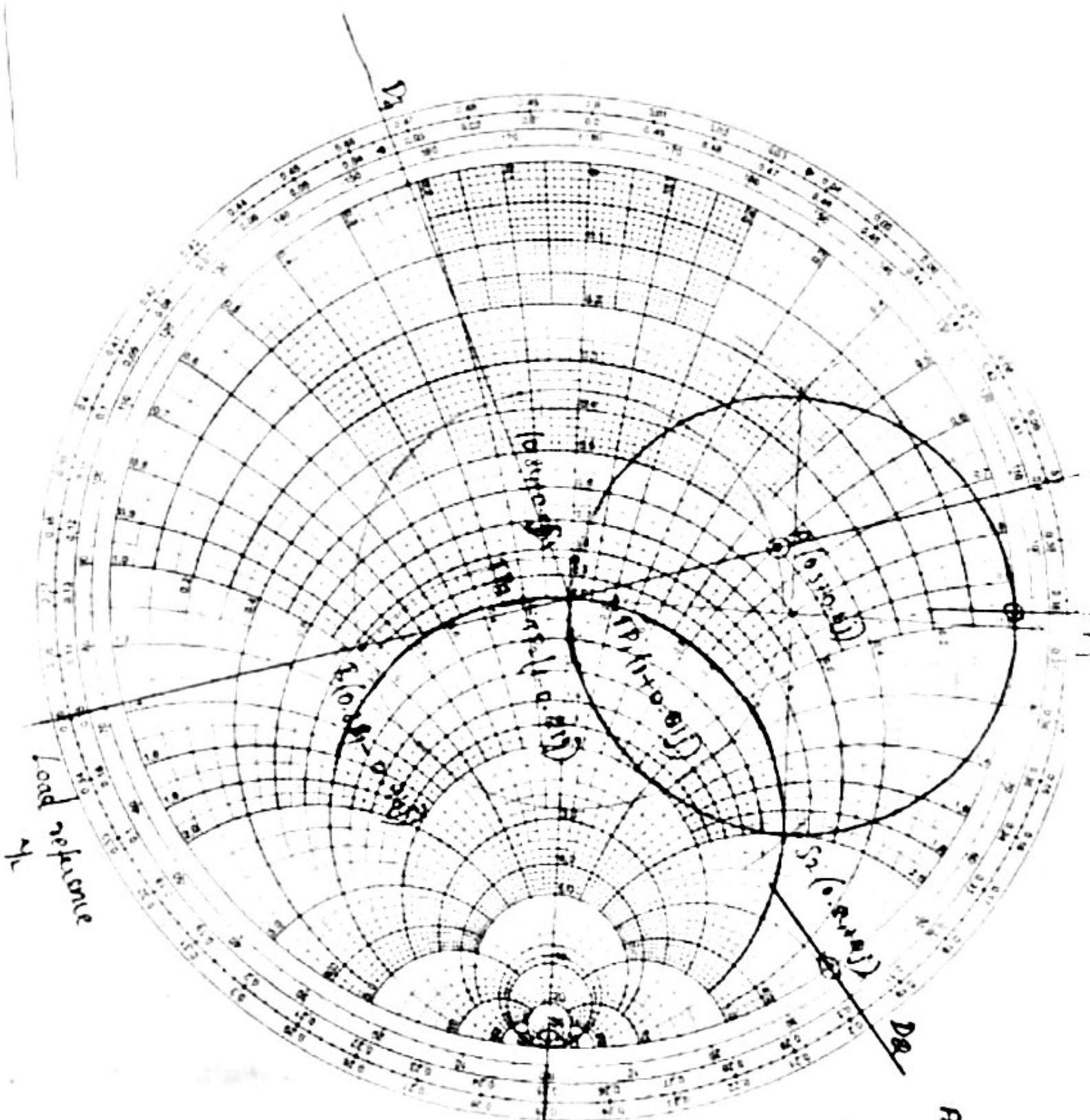


$A = 0.184 + j0.96$
 Normalized impedance
 $B = 0.084 + j0.96$
 Normalized admittance

$$\begin{aligned} B - S_1 &= 0.084 - 0.96j \\ &= -0.96j \\ S_1 - B &= 0.084 + 0.96j \\ &= 0.96j \\ S_2 - B &= 0.084 + 0.96j \\ &= 0.96j \end{aligned}$$


Part - A

3.

Short circuit

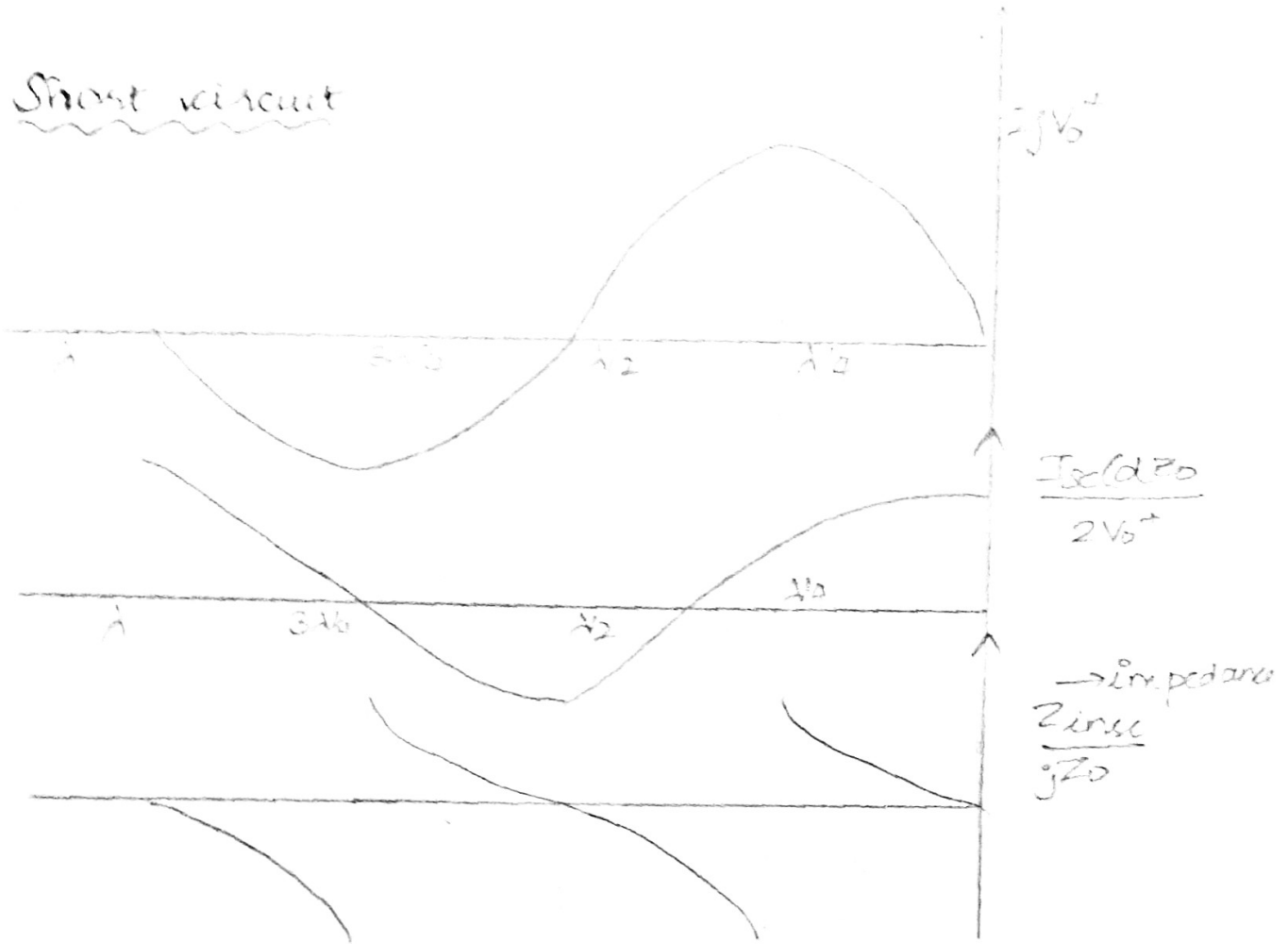

Open circuit

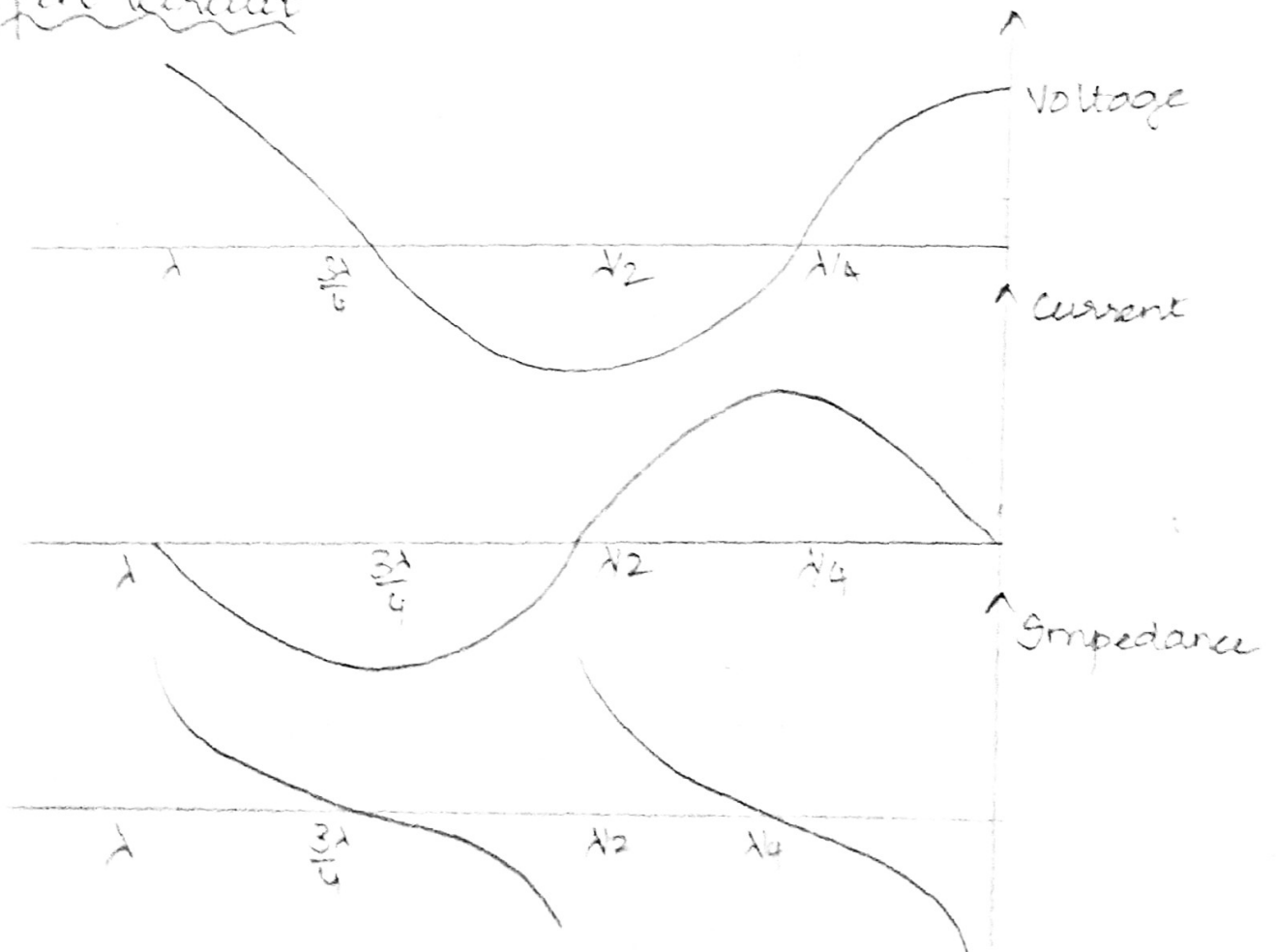

1.

$$Z_0 = 50 \Omega$$

$$Z_L = R + jX_L$$

$$\Gamma_L = 0.6$$

$$R = 50 \Omega$$

We know that

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{50 + jX_L - 50}{50 + jX_L + 50} = \frac{jX_L}{100 + jX_L}$$

$$\Rightarrow 0.6 = \frac{jX_L}{100 + jX_L}, \Rightarrow 60 + j(0.6)X_L = jX_L$$

$$\Rightarrow 60 = j(1 - 0.6)X_L = (0.4)jX_L$$

$$jX_L = \frac{60}{0.4} = \frac{600}{4} = 150$$

$$\Rightarrow X_L = -150j$$

$$\therefore Z_L = 50 + j(150) \Omega$$

2.

Coaxial cable impedance = 25Ω (on one end)
other end is short-circuited.

Impedance (when it is open circuited) = 100Ω

To find: characteristic impedance (Z_0)

$$Z_{sc} = jZ_0 \tan \beta l \quad Z_{oc} = -jZ_0 \cot \beta l$$

$$Z_0 = \sqrt{Z_{sc} \cdot Z_{oc}} = \sqrt{25 \times 100} = \sqrt{2500}$$

$$\Rightarrow \underline{50}$$

$$\underline{Z_0 = 50}$$

4) $L = 10 \mu\text{H/m}$ $f = 25 \text{ MHz}$
 $C = 40 \text{ pF/m}$ length = $100 \text{ cm} = l$

$$\omega = 2 \times 3.14 \times 25 \times 10^6$$

$$= 157 \times 10^6 \text{ rad/sec}$$

$$\beta = \omega \sqrt{LC} = 157 \times 10^6 \sqrt{10 \times 10^{-6} \times 40 \times 10^{-12}}$$

$$= 157 \times 10^6 \sqrt{400 \times 10^{-18}}$$

$$= 157 \times 10^6 \times 20 \times 10^{-9} = 3140 \times 10^{-3}$$

$$\Rightarrow \underline{\underline{\beta = 3.14}}$$

$$\text{Electrical length} = \beta l = 3.14 \times 100 \text{ cm}$$

$$= \underline{\underline{314 \text{ cm}}}$$

5) Condition for TE to exist in wave guide

$$E_z = + \frac{j\omega\mu}{h^2} \frac{\partial H_z}{\partial x}$$

$$H_x = - \frac{\gamma}{h^2} \frac{\partial H_z}{\partial x}$$

Condition for TM to exist in wave guide

$$H_y = - \frac{j\omega\epsilon}{h^2} \frac{\partial E_z}{\partial x}$$

$$E_x = - \frac{\gamma}{h^2} \frac{\partial E_z}{\partial x}$$