

Electrical Analogous of Mechanical-translational S/m.

→ The three basic elements mass, dash-pot & spring that are used in modelling mechanical-translational S/m's are analogous to resistance, inductance and capacitance of electrical S/m.

→ (i) Force - voltage analogy.

(a) Elements having same current \Rightarrow series connection.

Elements having same velocity \Rightarrow series connection.


(b) Each node in mechanical S/m ~~should~~ ~~have~~ corresponds to a closed loop in electrical S/m. A mass is considered as a node.

(c) No. of mesh currents = No. of velocities of nodes.



Mechanical S/m


i/p: force o/p: velocity

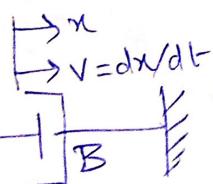

$$f = B \frac{dx}{dt} = Bv.$$


Electrical S/m

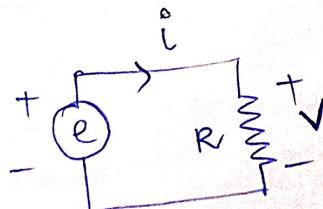i/p: voltage o/p: current thru the element




$$e = V = Ri$$

$$i = \frac{V}{R}$$

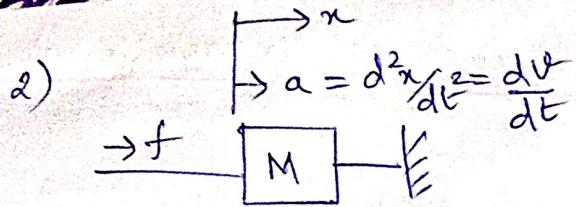

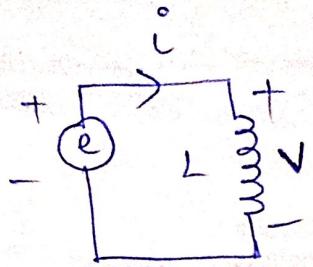
$$f = M \frac{d^2x}{dt^2} = M \frac{dv}{dt}$$




$$v = e = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int v dt$$

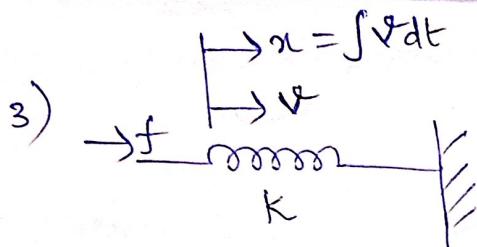

$$f = Kx = Kv$$

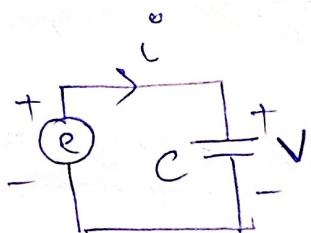

$$v = e = \frac{1}{C} \int i dt$$

$$i = C \frac{dv}{dt}$$

→ Analogous Quantities in Force-Voltage Analogy:
(I/p)

<u>Item</u>	<u>Mechanical s/m</u>	<u>Electrical s/m</u>
Independent variable (I/p)	Force, (f)	voltage (e, V)
Dependent variable (o/p)	velocity, (v)	current (i)
Dissipative element	Frictional co-ef of dash-pot (B)	charge (q)
Storage element	Mass, (M)	Resistance (R)
	stiffness of spring, (K)	Inductance (L)
		Inverse of capacitance (1/C)

physical law

Newton's second
law

$$\sum f = 0$$

KVL


$$\sum V = 0$$

(ii) Force - current Analogy

Mechanical s/m

i/p: force

o/p: velocity

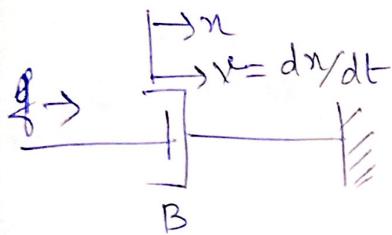


$$f = B \frac{dx}{dt} = BV$$

Electrical s/m


i/p: current source

o/p: voltage across the element.

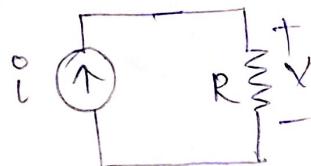


$$V = iR$$

$$i = V/R$$

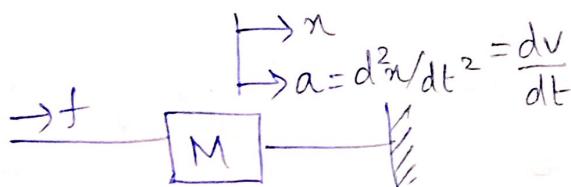

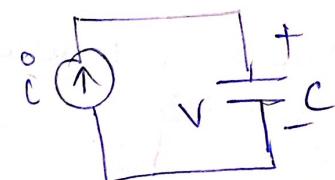
$$f = M \frac{d^2x}{dt^2} = M \frac{dv}{dt}$$




$$i = C \frac{dv}{dt}$$

$$V = \frac{1}{C} \int i dt$$

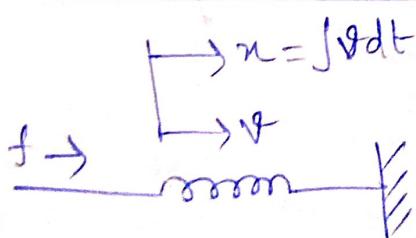

$$f = Kv = \int v dt$$

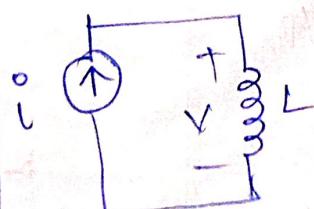

$$i = \frac{1}{L} \int V dt$$

$$V = L \frac{di}{dt}$$

→ Analogous Quantities in force-current analogy (i/p)


<u>Item</u>	<u>Mechanical s/m</u>	<u>Electrical s/m.</u>
Independent variable (i/p)	force (f)	current, i^o
Dependent variable (o/p)	velocity (v) Displacement, (x)	voltage (V) Flux (ϕ)
Dissipative element-	Frictional co-eff of Dashpot (B)	conductance ($G = Y_R$)
storage element .	Mass (M) Stiffness of spring (K)	capacitance (C) Inverse of Inductance, Y_L
physical law	Newton's II law $\sum f = 0$	KCL $\sum i^o = 0$

→ comparison:-

<u>M - s/m</u>	<u>F - V</u>	<u>F - C</u>
f (i/p)	V (i/p)	i^o (i/p)
v (o/p)	i^o (o/p)	V (o/p)
x	q	ϕ
B	R	Y_R
M	L	C
K	Y_C	Y_L


pbm

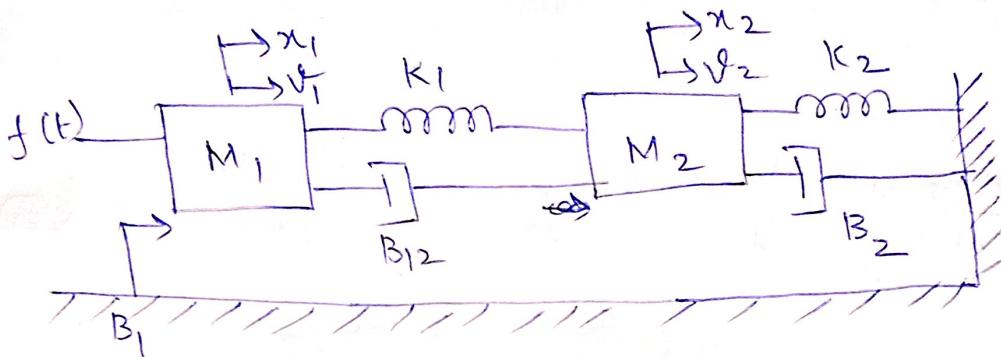- 1) Write the differential equations governing the mechanical s/m. Draw the F-V & F-C electrical analogous circuit & verify by writing Mesh and node equations.



Soln

$M_1 \rightarrow$ free body diagram.

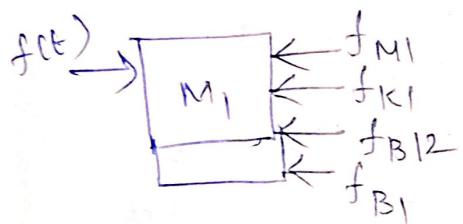

$$f_{M1} = M_1 \frac{d^2 x_1}{dt^2}$$

$$f_{K1} = K_1 (x_1 - x_2)$$


$$f_{B1} = B_1 \frac{dx_1}{dt}$$

$$f_{B12} = B_{12} \frac{d(x_1 - x_2)}{dt}$$

$$f(t) = M_1 \frac{d^2 x_1}{dt^2} + B_1 \frac{dx_1}{dt} + B_{12} \frac{d(x_1 - x_2)}{dt} + K_1 (x_1 - x_2)$$

— ①

$M_2 \rightarrow$ free body diagram.

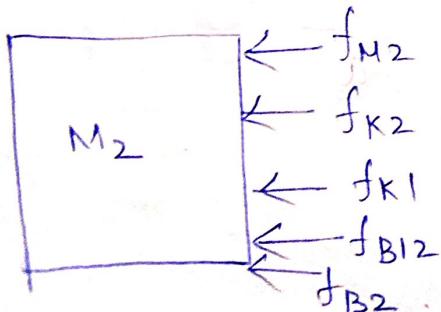

$$f_{M2} = M_2 \frac{d^2 x_2}{dt^2}$$

$$f_{K2} = K_2 (x_2 - x_1)$$

$$f_{B12} = B_{12} \frac{d(x_2 - x_1)}{dt}$$

$$f_{B2} = B_2 \frac{dx_2}{dt}$$

$$f_{K1} = K_1 (x_2 - x_1)$$

We know that

$$\Rightarrow \left. \begin{aligned} \frac{d^2x}{dt^2} &= \frac{dv}{dt} \\ \frac{dx}{dt} &= v \\ x &= \int v dt \end{aligned} \right\} \Rightarrow \textcircled{I}$$

$$\boxed{M_2 \frac{d^2x_2}{dt^2} + B_2 \frac{dx_2}{dt} + B_{12} \frac{d}{dt}(x_2 - x_1) + k_2 x_2 + k_1(x_2 - x_1) = 0} \quad \textcircled{2}$$

\rightarrow sub \textcircled{I} in $\textcircled{1}$ & $\textcircled{2}$.

$$\textcircled{1} \Rightarrow M_1 \frac{d^2v_1}{dt^2} + B_1 v_1 + B_{12} (v_1 - v_2) + k_1 \left(\int (v_1 - v_2) dt \right) = f(t) \rightarrow \textcircled{3}$$

$$\textcircled{2} \Rightarrow M_2 \frac{d^2v_2}{dt^2} + B_2 v_2 + k_2 \int v_2 dt + B_{12} (v_2 - v_1) + k_1 \int (v_2 - v_1) dt = 0. \rightarrow \textcircled{4}$$

(i) F-V Analogy

$f(t)$ = Voltage \times time, $v_1 \rightarrow i_1$ & $v_2 \rightarrow i_2$.
 no. of currents

$$M_1 = \text{inductance } L_1, \quad M_2 = L_2.$$

$$B_1 = \text{Resistance } R_1, \quad B_2 = R_2.$$


$$B_{12} = \text{Resistance Between 2 mesh or node}$$

$$R_{12}$$

$$k_1 = \text{inverse of capacitance } (1/C_1).$$

$$k_2 = 1/C_2.$$

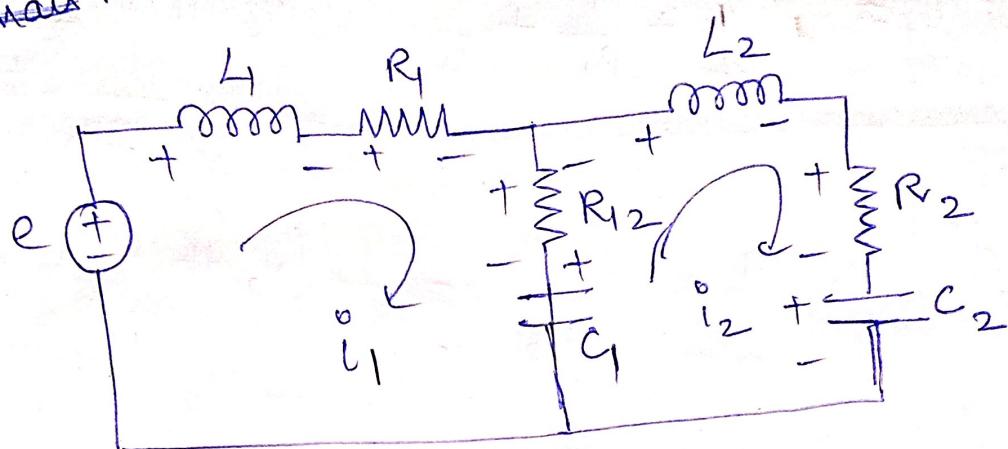$\alpha \rightarrow$ nodes \Rightarrow α -loop/mesh.
 ↑
 α -node.



$$e(t) = L_1 \frac{d^o i_1}{dt} + R_1 i_1 + R_{12} (i_1 - i_2) + \frac{1}{C_1} \int (i_1 - i_2) dt \quad \textcircled{5}$$

$$R_{12} (i_2 - i_1) + L_2 \frac{d^o i_2}{dt} + R_2 i_2 + \frac{1}{C_2} \int i_2 dt + \frac{1}{C_1} \int (i_2 - i_1) dt = 0 \quad \textcircled{6}$$

(ii) F-C Analogue circuit
 no. of voltages.

$$f(t) = i(t), \quad \boxed{v_1 = V_1 \text{ & } v_2 = V_2}$$


$$M_1 \rightarrow C_1 \quad M_2 \rightarrow C_2$$

$$B_1 = Y R_1 \quad B_2 = Y R_2 \quad B_{12} = Y R_{12}$$

$$K_1 = Y L_1 \Rightarrow \text{1st conn}$$

$$K_2 = Y L_2 \Rightarrow \text{2nd conn.}$$

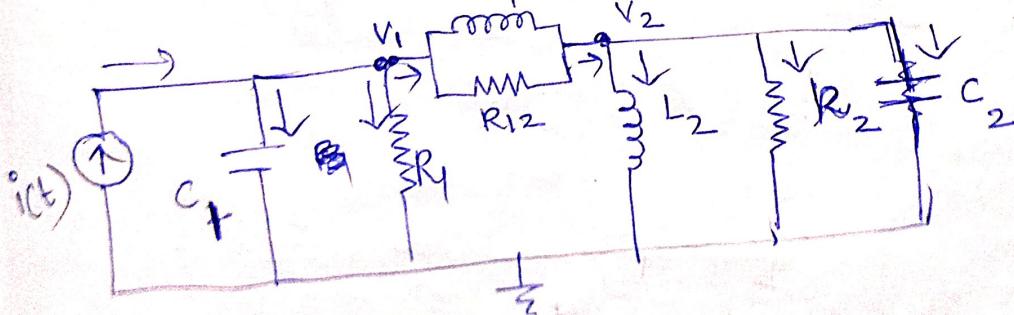α -node \Leftrightarrow α nodes in the electric ckt.



→ By KCL at node 1 & 2.

$$\text{node } ① \Rightarrow i(t) = C_2 \frac{dv_2}{dt} + \frac{v_1}{R_1} + \frac{1}{4} \int (v_1 - v_2) dt + \frac{v_1 - v_2}{R_{12}}$$

⑦

$$\text{node } ② \Rightarrow \frac{1}{4} \int (v_1 - v_2) dt + \frac{v_1 - v_2}{R_2} = \frac{1}{L_2} \int v_2 dt + \frac{v_2}{R_2} + C_2 \frac{dv_2}{dt}$$

⑧

$$C_2 \frac{dv_2}{dt} + \frac{v_2}{R_2} + \frac{1}{L_2} \int v_2 dt - \frac{1}{4} \int (v_1 - v_2) dt + \frac{v_2 - v_1}{R_2} = 0$$