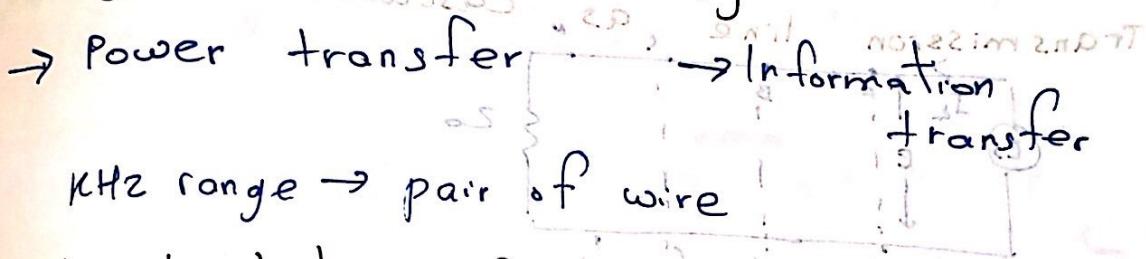


Transmission line Theory and parameters

Transmission Line:

A medium ϵ for propagating or guiding energy from one point to another.

Why propagation of energy:



why twisted pair?

\rightarrow Reduces interference

Optical $\rightarrow 10^{12}$ Hz (Higher freq)

$$SS = \text{Time} \quad T > t \quad \begin{matrix} \text{→ Time period} \\ \text{Time} \end{matrix}$$

$$\frac{1}{f} > \underline{l} \quad \begin{matrix} \text{→ Transit time} \\ \text{Time} \end{matrix}$$

$$\frac{V}{f} > l \quad \begin{matrix} \text{Distance} \\ \text{Time} \end{matrix} \rightarrow \text{Speed}$$

$$\underline{\lambda} = \frac{V}{f} > l \quad \begin{matrix} \text{Wavelength} \\ \text{Time} \end{matrix} \rightarrow \text{Time}$$

If $\lambda < l$, transit effect const

propagation can be ignored

(optical fiber) $t = \frac{2l}{c}$


Lumped and Distributive elec

\hookrightarrow cannot be seen


can be
physically
realised

$z_0 \rightarrow$ char impedance
 $\omega_0 \rightarrow$ High freq \rightarrow Highly R

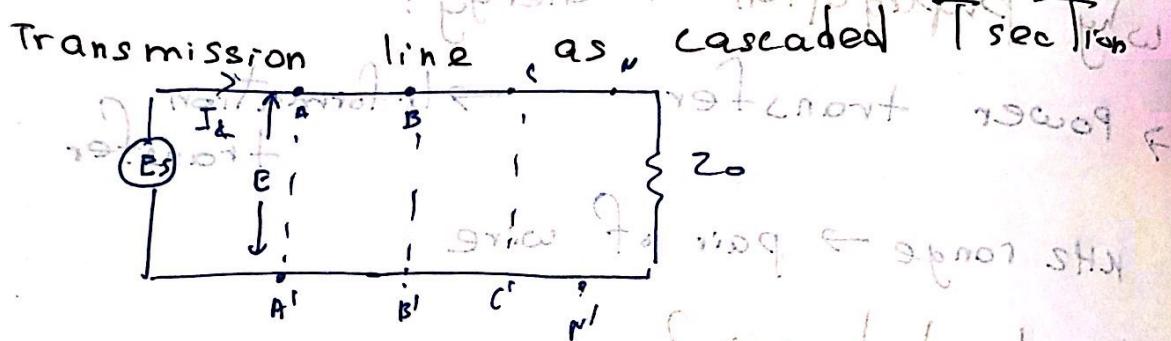Loss (dB/meter) is min at $\frac{27}{2}$ meter
 (in wires) \rightarrow Propagation loss \rightarrow minimum
 Power is max at $\frac{30}{2}$ m. \rightarrow max. power
 So z_0 is a compromise.



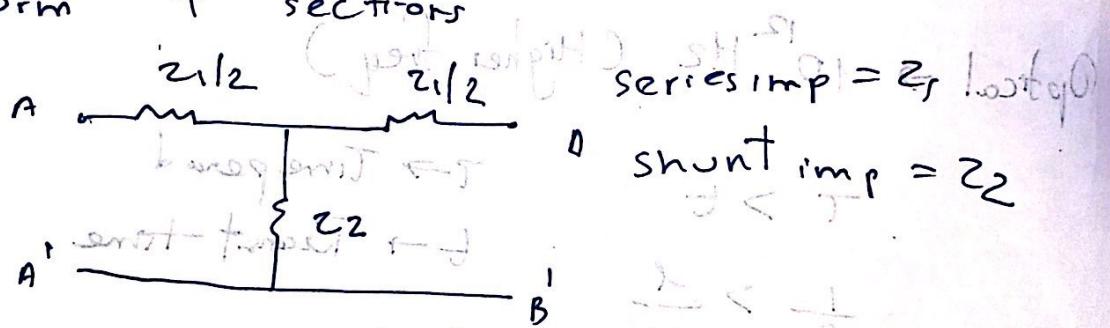We divide transmission line into uniform T sections



- AB, BC ... \rightarrow identical no. of sections
- ES \rightarrow voltage applied at end and terminated
- due to distributed phasor diff

$$\frac{I_s}{I_i} = e^{-\gamma l} \quad \begin{matrix} \text{where } \gamma \rightarrow \text{Propagation} \\ \text{constant per unit length} \end{matrix}$$

Net id. term \downarrow

Primary constants of transmission line
 Primary constants $\rightarrow R, L, G$ and C

secondary constants $\rightarrow Z_0 = \sqrt{\frac{\text{series imp}}{\text{shunt imp}}} = \sqrt{\frac{R+j\omega_0 L}{G+j\omega_0 C}}$

propagation constant \rightarrow Propagation constant (γ or T)


$$\gamma = \sqrt{\frac{\text{series}}{\text{series imp} \times \text{shunt imp}}}$$

[series impedance denoted by Z
 and shunt impedance by Y']

γ (or) $P = \alpha + j\beta$, $\alpha \rightarrow$ attenuation constant

$\beta \rightarrow$ propagation phase constant

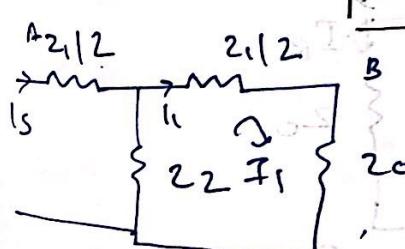In general, $\frac{I_{n-1}}{I_n} = e^{\gamma}$ no. of sub-sections



$$I_{1b} = I_s \cdot \frac{Z_2}{Z_{1/2} + Z_2 + Z_0}$$

$$\frac{I_s}{I_1} = 1 + \frac{Z_{1/2}}{Z_2} + \frac{Z_0}{Z_2} \quad \rightarrow ②$$

From ① and ② on solving for long λ

$$\frac{I_s}{I_1} = e^{\gamma} = \frac{Z_1}{Z_2} + \frac{Z_0}{Z_2}$$

$$\Rightarrow \gamma = \ln \left[1 + \frac{Z_1}{Z_2} + \frac{Z_0}{Z_2} \right]$$

$$\text{Also } \frac{I_s}{I_1} = e \quad \text{and} \quad \frac{I_s}{I_2} = \frac{I_s}{I_1} \cdot \frac{I_1}{I_2} = e \cdot e^{-1} = e^0 \leftarrow \begin{array}{l} \text{Invertors} \\ \text{cancel} \end{array}$$

$$\frac{I_5}{I_3} = e^{-3Y_{\text{general}}}$$

Hence in general

$$\frac{I_s}{I_{IN}} = e^{\frac{V_o}{NVT}}$$

$$I_n = I_s e^{-n\gamma}$$

qm1 line x qm123nor.


$$\text{Why } \frac{E_S}{I_S} = 20 = \frac{E_1}{I_1} = \frac{E_2}{I_2} \dots = \frac{E_n}{I_n}$$

before I_1 after I_1

$$\frac{E_S}{I_S} = \frac{E_2}{I_2}$$

$$\text{not } \frac{\mathbb{E}[S_{n+1}]}{\mathbb{E}[S_n]} = \frac{\mathbb{E}[S_n]}{\mathbb{E}[S]} \geq e^{N\eta} \text{ if } x = g(\eta) \checkmark$$

$$E_N = E_S e^{-N\gamma}$$

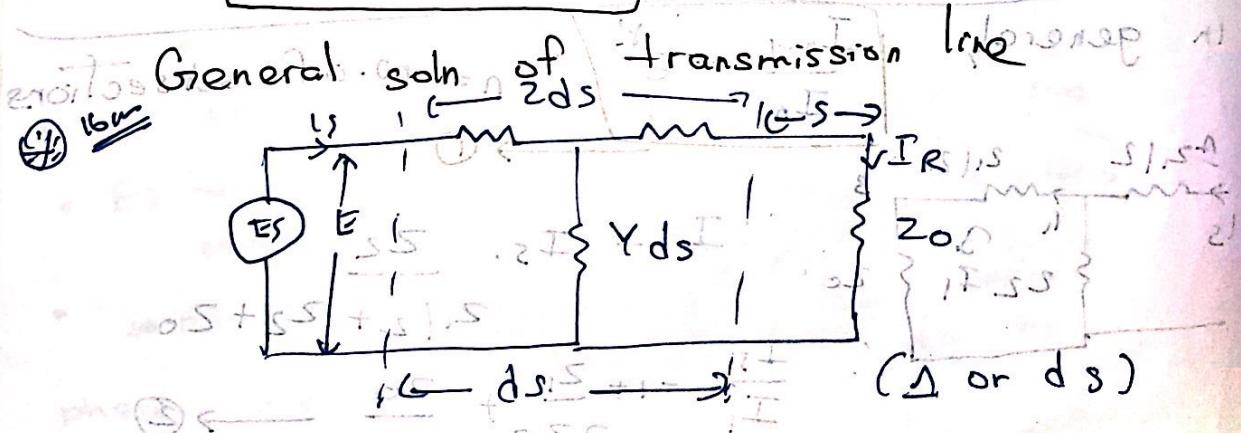

General soln gives the variation of I .

and V along the transmission line

length $l \rightarrow$ infinite T sections

$S \rightarrow$ [Distance from receiving end] $= 8$

$ds \rightarrow$ length of sectors

$$\text{series imp} : Z ds \quad \text{shunt imp} : Y ds \quad Z + Y = Z_A = Z$$

Elemental voltage drop in length $ds = E$

$$dE = I \cdot Z ds$$

$$\frac{dE}{ds} = I \cdot Z - \frac{1}{2} \left(\frac{dE}{ds} \right) \quad \text{at } s = 0$$

leakage current flowing through shunt admittance from one conductor to other

$$dI_L = E \cdot Y ds$$

$$\frac{dI_L}{ds} = E \cdot Y \quad \text{at } s = 0$$

biff ① and ② w.r.t s'

$$\frac{d^2 E}{ds^2} = Z ds \cdot \frac{dI}{ds} \quad \text{at } s = 0$$

$$\frac{d^2 I}{ds^2} = \frac{dE}{ds} \cdot Y \quad \text{at } s = 0$$

$$\text{sub ② in ③} \quad \frac{d^2 E}{ds^2} = Z ds \cdot \frac{dI}{ds} = Z ds \cdot Y \quad \text{at } s = 0$$

$$\text{sub ① in ④} \quad \frac{d^2 I}{ds^2} = I \cdot Z \cdot Y \quad \text{at } s = 0$$

⑤ and ⑥ core second order diff eqns:

$$\frac{d^2 E}{ds^2} - Z ds \cdot Y = 0$$

$$(m^2 - Z ds \cdot Y) E = 0 \Rightarrow m = \pm \sqrt{Z ds \cdot Y}$$

$$\frac{d^2 I}{ds^2} - Z ds \cdot Y = 0 \Rightarrow m = \pm \sqrt{Z ds \cdot Y}$$

$$(m^2 - Z ds \cdot Y) I = 0$$

$$m = \pm \sqrt{Z ds \cdot Y}$$

General soln for eqn for E and I

$$E = Ae^{(\sqrt{ZY})s} + Be^{(-\sqrt{ZY})s}$$

$$I = Ce^{(\sqrt{ZY})s} + De^{(-\sqrt{ZY})s}$$

$$\boxed{E = Ae^{rs} + Be^{-rs}} \rightarrow 7$$

$$\boxed{I = Ce^{rs} + De^{-rs}} \rightarrow 8$$

A, B, C, D are constants, we must find their values

At the receiving end $E = E_R \quad I = I_R \quad s = b$

$$E_R = Ae^0 + Be^0 = A + B \rightarrow 9$$

$$I_R = Ce^0 + De^0 = C + D \rightarrow 10$$

Again differentiating 7 and 8 w.r.t 's' :

$$\frac{dE}{ds} = Y Ae^{rs} - Y Be^{-rs}$$

$$IZ = Y Ae^{rs} - Y Be^{-rs}$$

$$\frac{dI}{ds} \Rightarrow I = \frac{A \sqrt{ZY}}{2} e^{rs} - \frac{B \sqrt{ZY}}{2} e^{-rs}$$

$$\boxed{I = A \sqrt{\frac{Y}{Z}} e^{rs} - B \sqrt{\frac{Y}{Z}} e^{-rs}} \rightarrow 11$$

$$\frac{dT}{ds} = Crem - Drem \quad T = (Ys - \omega)$$

$$e^V = C \sqrt{ZY} e^{rs} - B \sqrt{ZY} e^{-rs}$$

$$E = C \sqrt{\frac{Z}{Y}} e^{rs} - D \sqrt{\frac{Z}{Y}} e^{-rs} \quad (12)$$

Substituting boundary conditions in (11) and (12)

$$I_R = A \sqrt{\frac{Y}{Z}} e^s - B \sqrt{\frac{Y}{Z}} e^{-s} \quad (13)$$

$$E_R = C \sqrt{\frac{Z}{Y}} e^{rs} - D \sqrt{\frac{Z}{Y}} e^{-rs} \quad (14)$$

Solving (9) and (14)

$$E_R = A + B$$

$$I_R = A \sqrt{\frac{Y}{Z}} - B \sqrt{\frac{Y}{Z}} \quad (15)$$

$$E_R = \sqrt{\frac{Y}{Z}} (A + B \sqrt{\frac{Y}{Z}}) \quad (16)$$

$$(17) I_R = (A \sqrt{\frac{Y}{Z}} - B \sqrt{\frac{Y}{Z}}) \quad (17)$$

$$B = E$$

$$A = \frac{E_R}{\sqrt{\frac{Y}{Z}}} + \frac{I_R}{\sqrt{\frac{Y}{Z}}} \sqrt{\frac{Z}{Y}}$$

$$A = \frac{E_R}{2} \left[1 + \frac{Z_0}{Z_R} \right]$$

$$B = \frac{E_R}{2} \left[1 - \frac{Z_0}{Z_R} \right]$$

$$C = \frac{I_R}{2} \left[1 + \frac{Z_R}{Z_0} \right]$$

$$D = \frac{I_R}{2} \left[1 - \frac{Z_R}{Z_0} \right]$$

∴

$$\textcircled{1} \quad \delta = B - A = I$$

$$E = \frac{E_R}{2} \left[1 + \frac{Z_0}{Z_R} \right] e^{rs} + \frac{E_I}{2} \left[1 - \frac{Z_0}{Z_R} \right] e^{-rs}$$

$$I = \frac{I_R}{2} \left[1 + \frac{Z_R}{Z_0} \right] e^{rs} + \frac{I_R}{2} \left[1 - \frac{Z_R}{Z_0} \right] e^{-rs}$$

$$E = \frac{E_R (Z_R + Z_0)}{2 Z_R} \left[e^{rs} + \frac{(Z_R - Z_0)}{e^{-rs}} \right]$$

$$I = \frac{I_R (Z_R + Z_0)}{2 Z_0} \left[e^{rs} \right]$$

$$\frac{1}{2} + \frac{1}{2} = 1$$

$$E = I_R e^{\gamma s} \cosh \gamma s + I_R Z_0 \sinh \gamma s \quad \rightarrow 17$$

$$I = \frac{I_R Z_R e^{\gamma s}}{Z_0} + \frac{I_R Z_0 e^{\gamma s}}{Z_0} - \frac{I_R e^{\gamma s}}{Z_0} \frac{I_R Z_0 e^{-\gamma s}}{Z_0}$$

$$I = I_R \cosh \gamma s + E_R \sinh \gamma s \quad \rightarrow 18$$

(5), (6), (7), (8) \rightarrow General soln of Tenu 21

~~10~~ Physical significance of the eqn:

Case 1: Sending current

$$I_S = I_R \cosh \gamma l + \frac{E_R}{Z_0} \sinh \gamma l$$

length of transmssn
= line

Case 2: Sending end voltage

$$E_S = E_R \cosh \gamma l + I_R Z_0 \sinh \gamma l$$

$$E_S = E_R \left[\cosh \gamma l + \frac{Z_0}{Z_R} \sinh \gamma l \right]$$

$$E_S = I_R \left[Z_R \cosh \gamma l + Z_0 \sinh \gamma l \right]$$

Case 3: If pmp $Z_S = \frac{E_S}{I_R}$

$$Z_S = \frac{I_R \left[Z_R \cosh \gamma l + Z_0 \sinh \gamma l \right]}{I_R}$$

$$Z_S = \frac{I_R \left[\cosh \gamma l + \frac{Z_0}{Z_R} \sinh \gamma l \right]}{\cosh \gamma l + Z_0 \sinh \gamma l}$$

$$Z_S = \frac{Z_0 \left[Z_R \cosh \gamma l + Z_0 \sinh \gamma l \right]}{Z_R \cosh \gamma l + Z_0 \sinh \gamma l}$$

Note 1 = When line is terminated in Z_0 , $Z_s = Z_0$

$$Z_R = Z_0$$

$$\boxed{Z_s = Z_0}$$

It shows that line terminated in characteristic impedance, its input impedance is also its characteristic impedance.

Note 2:

Consider an infinite length $\lambda \rightarrow \infty$

$$Z_s = Z_0 \left[\frac{Z_R + Z_0 \tanh hYl}{Z_0 + Z_R \tanh hYl} \right]$$

$$\text{to solve } \rightarrow Z_0 + Z_R \tanh hYl = Z_s$$

assume

$$\text{end} = \left[\frac{Z_0 [Z_R + Z_0]}{(Z_0 + Z_R)} + hYl \right] I = ?$$

$$\boxed{Z_s = Z_0}$$

Finite line terminated in its characteristic impedance behaves like an infinite line to the sending end.

Wavelength and velocity of propagation

The distance the wave travels along the line when phase angle is changing through 2π radians is called wavelength
 $\lambda \rightarrow$ wavelength $\beta \rightarrow$ phase constant

$$s = \lambda \quad \boxed{\lambda = \frac{2\pi}{\beta}}$$

velocity of propagation along the line, based on observations of change in phase along the line

$$\boxed{v = \frac{\omega}{\beta}}$$

$$\omega = 2\pi f$$

condition for distortionless line:

Propagation constant

$$\alpha + j\beta = \sqrt{Z_0 - j\frac{R}{L}}$$

$$(R+j\omega L) = j\omega C \quad \text{series imp. } R+j\omega L = j\omega C$$

Ideal line: $R = 0$ and $G = 0$

$$\gamma = \alpha + j\beta = \sqrt{j\omega LC}$$

~~$$\alpha + j\beta = j\omega \sqrt{LC}$$~~

$$\boxed{\beta = \omega \sqrt{LC}}$$

$$\boxed{\alpha = 0}$$

for minimum attenuation

condition

and

$$R^2 = LG$$

$$(R+j\omega L) + (j\omega C - j\omega G) = 0$$

$$CR = CG$$

2018504501

ABDUR RAHMAN SHERIFF

condition for minimum attenuation:

$$\sigma_V = \alpha + j\beta$$

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$

$$(\alpha + j\beta)^2 = (R+j\omega L)(G+j\omega C)$$

$$\alpha^2 - \beta^2 + 2j\alpha\beta = RG - \omega^2 LC + j\omega RC + j\omega GL$$

Equating real and imaginary terms

$$\alpha^2 - \beta^2 = RG - \omega^2 LC \quad 2\alpha\beta = \omega(RC + GL)$$

$$\alpha^2 = \beta^2 + RG - \omega^2 LC \quad \alpha\beta = \frac{\omega}{2}(RC + GL)$$

$$\alpha^2\beta^2 = \beta^4 + RG\beta^2 - \omega^2 LC\beta^2 \quad \alpha^2\beta^2 = \frac{\omega^2}{2^2}(RC + GL)^2$$

$$\beta^4 + RG\beta^2 - \omega^2 LC\beta^2 = \frac{\omega^2}{2^2}(RC + GL)$$

$$\beta^4 + \beta^2(RG - \omega^2 LC) = \frac{\omega^2}{4}(RC + GL)$$

$$\beta^2 = \frac{-RG - \omega^2 LC \pm \sqrt{(RG - \omega^2 LC)^2 + \omega^2 (RC + GL)^2}}{2}$$

Neglect -ve term

$$\beta = \sqrt{\frac{(\omega^2 LC - RG)^2 + \omega^2 (RC + GL)^2}{2}}$$

$$\alpha = \sqrt{\frac{(RG - \omega^2 LC)^2 + \omega^2 (RC + GL)^2}{2}}$$

If a line is to have neither frequency nor delay & distortion & and γ cannot be functions of frequency

$$\gamma = \frac{\omega}{\beta} = 0, \quad \beta = \text{constant}$$

β must be a factor of frequency

$$(RG - \omega^2 LC)^2 + \omega^2 (RCL + GL)^2 \text{ must be equal}$$

$$\text{to } (RG + \omega^2 LC)^2$$

$$R^2 G^2 + \omega^4 L^2 C^2 - 2\omega^2 L C R G + \omega^2 L^2 G^2 + \omega^2 C^2 R^2 + 2\omega^2 L C R G = R^2 G^2 + \omega^4 L^2 C^2 + 2\omega^2 L C R G$$

$$\omega^2 L^2 G^2 + \omega^2 C^2 R^2 = 2\omega^2 L C R G$$

$$\omega^2 L^2 G^2 + \omega^2 C^2 R^2 - 2\omega^2 L C R G = 0$$

$$(LG - CR)^2 = 0$$

$$(LG - CR) = 0$$

$$LG = CR$$

$$\frac{R}{L} = \frac{G}{C}$$

$$\frac{G}{C} = \frac{R}{L}$$

$$jY_N \omega = \omega$$

Impedance in terms of ω and Z_0

Z_{SC} and Z_{OC}

$$Z_{OC} \rightarrow \infty \Rightarrow I_R = 0, Z_R = \frac{\omega}{\eta}$$

$$Z_{SC} \rightarrow E_R = 0, Z_R = 0$$

$$Z_S = \frac{Z_0(Z_R \cosh hYl + Z_0 \sinh hYl)}{(Z_R \cosh hYl + Z_0 \sinh hYl)}$$

$$Z_{SC}, Z_{OC}$$

$$Z_{OC} \rightarrow I_R = 0, Z_R = \infty$$

$$Z_{SC} \rightarrow E_R = 0, Z_R = 0$$

$$Z_{OC} = \lim_{Z_R \rightarrow \infty} \frac{Z_0 Z_R (\cosh hYl + \frac{Z_0}{Z_R} \sinh hYl) \omega}{Z_R (\frac{Z_0}{Z_R} \cosh hYl + \sinh hYl)}$$

$$\leftarrow = \lim_{Z_R \rightarrow \infty} \frac{Z_0 \left(1 + \frac{Z_0}{Z_R} \tanh hYl \right)}{\frac{Z_0}{Z_R} + \tanh hYl}$$

$$= \frac{Z_0}{\tanh hYl}$$

$$Z_{OC} = Z_0 \coth hYl$$

$$Z_{SC} = \frac{Z_0(\cosh Yl + Z_0 \sinh Yl)}{\cosh Yl + Z_0 \sinh Yl} \quad (1)$$

$$Z_R = 0 \quad \frac{Z_0}{\cosh Yl} + \frac{Z_0}{\sinh Yl} + \frac{Z_0}{\cosh Yl} - \frac{Z_0}{\sinh Yl} = 0$$

$$Z_{SC} = \frac{Z_0^2 \sinh Yl}{Z_0 \cosh Yl} = \frac{Z_0 \tanh Yl}{\cosh Yl} \quad (3)$$

$$Z_{SC} Z_{OC} = Z_0^2$$

$$Z_0 = \sqrt{Z_{SC} Z_{OC}}$$

propagation constant in terms of Z_{SC} and Z_{OC}

$$\frac{1}{Z_0} = \frac{1}{Z_1} + \frac{1}{Z_2} \quad \frac{1}{Z_0} = \frac{1}{Z_1} + \frac{1}{Z_2} = \gamma$$

$$e^\gamma = 1 + \frac{Z_1}{Z_2} + \frac{Z_2}{Z_1} \quad \frac{1}{Z_0} = \frac{1}{Z_1} + \frac{1}{Z_2} = \gamma$$

$$e^{-\gamma} = \left[1 + \frac{Z_1}{Z_2} + \frac{Z_2}{Z_1} \right]^{-1} \quad \frac{1}{Z_0} = \frac{1}{Z_1} + \frac{1}{Z_2} = \gamma$$

We know that for a section

$$Z_0 = \sqrt{\frac{Z_1^2 + 2Z_1 Z_2}{4Z_1 Z_2}} = \sqrt{\frac{Z_1^2 + 2Z_1 Z_2}{4Z_1^2 + 4Z_2^2}} = \sqrt{\frac{Z_1^2}{4Z_1^2 + 4Z_2^2} + \frac{2Z_1 Z_2}{4Z_1^2 + 4Z_2^2}}$$

$$e^{-\gamma} = \left[1 + \frac{Z_1}{Z_2} + \sqrt{\frac{Z_1^2 + 2Z_1 Z_2}{4Z_1^2 + 4Z_2^2}} \right]$$

$$= \left[1 + \frac{Z_1}{Z_2} + \sqrt{\frac{Z_1^2 + 2Z_1 Z_2}{4Z_1^2}} \right]^{-1}$$

By using binomial series and eliminating higher order terms

$$= 1 - \frac{z_1}{2z_2} - \sqrt{\frac{z_1^2}{4z_2^2} + \frac{z_1}{z_2}} + \frac{z_1^2}{4z_2^2} + \frac{z_1^2}{4z_2^2} + \frac{z_1^2}{4z_2^2}$$

$$\text{Eq } C = 1 + \frac{z_1}{2z_2} - \frac{z_1}{z_2} = \frac{2z_1 z_2}{2z_2 - z_1}$$

$$\boxed{\text{Eq } 1 + 2 = 0}$$

$$\boxed{-s_{0.5} = s_{0.5}}$$

$$e^{j\gamma} - e^{-j\gamma} = \left[C z_2 + \frac{z_1}{z_2} + \frac{z_0}{z_2} \right] + i \frac{z_1}{z_2} - \frac{z_0}{z_2}$$

$$2 \cosh \gamma = 2 \left(1 + \frac{z_1}{z_2} \right)$$

$$\boxed{\cosh \gamma = 1 + \frac{z_1}{z_2}} \quad \text{--- Eq 3}$$

$$e^{\gamma} - e^{-\gamma} = \frac{2z_0}{z_2}$$

$$\boxed{\sinh \gamma = \frac{z_0}{z_2}} \quad \text{--- Eq 4}$$

$$\text{Eq 4} + \text{Eq 3} \quad \tanh \gamma = \frac{z_0}{z_2} \times \frac{2z_2}{2z_2 + z_1}$$

$$\coth \gamma = \frac{z_0}{z_2 + z_1} = 0.5$$

$$\operatorname{coth} \gamma = \frac{\sqrt{2z_0 z_2 + z_0^2}}{z_0} = \frac{\sqrt{z_0^2 + z_0^2}}{z_0} = \frac{\sqrt{2} z_0}{z_0} = \sqrt{2}$$

$$\boxed{\frac{z_0^2 + z_0^2}{z_0^2} + \frac{z_0^2}{z_0^2} + \dots}$$

$$\tanh \beta = \sqrt{\frac{Z_{SC}}{Z_{OC}}} = \sqrt{\frac{R}{Y}} = \sqrt{R^2 + L^2}$$

variation of char impedance

when there is variation when freq changes, each component will undergo different attenuation.

$\beta \rightarrow$ phase distortion when all freq does not arrive at the same time reflection


now better to option to other e
new method to find it

27.

$$S \left[\frac{\omega}{\omega_0} - j \frac{R}{L} \right] + R \left[\frac{\omega}{\omega_0} + j \frac{R}{L} \right] = Z$$

between R & L

between C & L

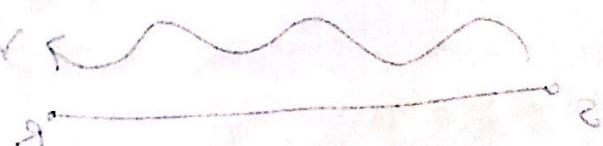

$$\beta = \omega \sqrt{LC}$$

transitions normalizing

$$V = \frac{\omega}{\beta} \left[\frac{\omega}{\omega_0} - j \frac{R}{L} \right] + R \sqrt{\frac{R}{L}}$$

$$\alpha = \sqrt{RL}$$

$$\gamma = \sqrt{\frac{\omega}{\omega_0}} \frac{\omega}{\sqrt{LC}} = \frac{1}{\sqrt{L/C}} \sqrt{R/L}$$

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R+j\omega L}{G+j\omega C}}$$

Since,

$$LG = CR$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

does not contain reactance terms so no distortion

No freq component w present in $\alpha \rightarrow$ no distortion


Uniform velocity velocity \rightarrow No phase distortion due to source for load distortion part do not do work

Reflection coefficient

\rightarrow Ratio of voltage of reflected wave to that of incident wave

$$E = \frac{E_R}{2} \left[1 + \frac{Z_0}{Z_R} \right] e^{jS} + \frac{E_R}{2} \left[1 - \frac{Z_0}{Z_R} \right] e^{-jS}$$

Incident wave *Reflected wave*

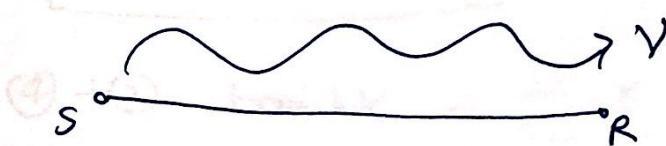

Reflection coefficient k

$$= \frac{E_R/2 \left[1 - \frac{Z_0}{Z_R} \right] e^{-jS}}{E_R/2 \left[1 + \frac{Z_0}{Z_R} \right] e^{jS}}$$

$$\frac{j\omega C}{j\omega C + j\omega L} = \frac{1}{1 + \frac{Z_0}{Z_R}}$$

Reflection occurs at $S=0$ (reflection end) $\Rightarrow P_0$

$$k = \frac{Z_R - Z_0}{Z_R + Z_0}$$

$$\frac{0.5 - 9.5}{0.5 + 9.5} = 1$$

$$\text{Cases} = \frac{0(5-5)}{9.5} + \frac{0(0.5+9.5)}{9.5} = \frac{0}{9.5} = 0$$

$$\frac{0.5}{0.5} = \frac{1}{1} = 1$$

1st case:

$$\begin{cases} \text{1st case: } & Z_R = Z_0 \\ Z_0 = Z_R & k \neq 0 \\ k = 0 & \end{cases}$$

Cases =

$$\begin{cases} \text{2nd case: } & Z_R = Z_0 \\ \text{Case 1: } & \text{When } Z_R = Z_0 \\ k = 0 & \end{cases}$$

Case 2: When $Z_R \neq 0$ (S.C)

$$\boxed{\begin{cases} k = -1 \\ \text{Case 3: When } Z_R = 0 \\ k = 1 \end{cases}}$$

∴ The reflection will be more

when the line is O.C

109 Impedance in term of reflection coefficient

$$k = \frac{Z_R - Z_0}{Z_R + Z_0}$$

$$Z_S = \frac{E}{I} = \frac{\frac{ER}{2Z_R} (Z_R + Z_0) e^{rl} + \frac{ER}{2Z_R} (Z_R - Z_0) e^{-rl}}{2Z_R}$$

$$= \frac{\frac{IR}{2Z_0} [Z_R + Z_0] e^{rl} - \frac{IR}{2Z_0} (Z_R - Z_0) e^{-rl}}{2Z_0}$$

$$= \frac{\frac{ER}{2Z_R} (Z_R + Z_0) e^{rl} + \frac{ER}{2Z_R} k(Z_R + Z_0) e^{-rl}}{2Z_R}$$

$$= \frac{\frac{IR}{2Z_0} (Z_R + Z_0) e^{rl} - \frac{IR}{2Z_0} k(Z_R + Z_0) e^{-rl}}{2Z_0}$$

$$= Z_0 \left[\frac{IR}{2Z_0} (Z_R + Z_0) e^{rl} + \frac{IRk}{2Z_0} (Z_R + Z_0) e^{-rl} \right]$$

$$(Q.2) Z_S = \frac{IR(Z_R + Z_0) e^{rl} - IRk(Z_R + Z_0) e^{-rl}}{2Z_0}$$

$$Z_S = \frac{Z_0 \left[e^{rl} + k e^{-rl} \right]}{e^{rl} + k e^{-rl}}$$

(final form)

From Q. 11.6 reflection coefficient

reflection coefficient \rightarrow w and I refl. not

reflection coefficient

w and I refl. not

reflection coefficient

Reflection loss
defined as no. of nepers or decibels by which the current in load under matched condition would exceed the current actually flowing in the load

$$\text{reflection loss} = \ln \left| \frac{I_2'}{I_2} \right| \text{nepers}$$


$$(K) = 20 \log \left| \frac{I_2'}{I_2} \right| \text{dB}$$

Reflection factor

$$k = \frac{2\sqrt{Z_R Z_0}}{Z_R + Z_0}$$

This ratio indicates the change in current in the load due to reflection at a

mismatched junction

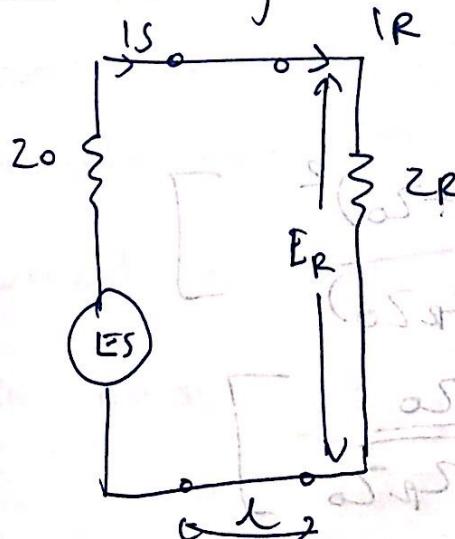

Let P_1 be the power at receiving end due

to the incident wave

P_2 → power absorbed by the load

P_3 → Power reflected down the line

$$P_1 = P_2 + P_3$$

$$P \propto I^2$$

$$I \propto (P)^{1/2}$$

$$\text{Reflection loss} = P_{\text{reflected}} = E_R \frac{I}{2} R$$

$$P_3 = k^2 |k| E_R \cdot k |k| I_R$$

reflection terms

$$P_3 = k^2 |k| E_R I_R$$

loss due to absorption
loss due to reflection
loss due to scattering

$$P_2 = P_1 - P_3$$

$$P_1 = P_1 \left(1 - \frac{|k|^2}{|k|^2 + 1}\right)$$

$$P_1 = P_1 \left(1 - \frac{1}{1 + |k|^2}\right)$$

Reflection loss

$$= 10 \log \left[\frac{P_1}{P_2} \right]$$

loss terms in series

$$\rightarrow \text{loss} = 10 \log \left[\frac{1}{1 - |k|^2} \right]$$

w.k.t: $k = z_r - z_0$

new setting, $\frac{z_r + z_0}{z_r - z_0}$

final eqn:

$$R.L = 10 \log \left[\frac{(z_r + z_0)^2}{4(z_r z_0)} \right]$$

$$= 20 \log \left[\frac{z_r + z_0}{2 \sqrt{z_r z_0}} \right]$$

$$R.L = 20 \log \left[\frac{1}{|k|} \right]$$

$$(q) \propto I$$

Return loss:

Ratio of power at the receiving end due to incident wave to the power reflected by the load.

$$\text{Return loss} = 10 \log \left| \frac{P_1}{P_2} \right| \text{dB}$$

$$= 10 \log \left| \frac{P_1}{K^2 P_1} \right| \text{dB}$$

$$= 10 \log \left| \frac{1}{K^2} \right| \text{dB}$$

$$\text{Return loss} = 10 \log \left| \frac{1}{K^2} \right| \text{dB}$$

$$= 20 \log \left| \frac{1}{K} \right| \text{dB}$$

$$\text{Return loss} = 20 \log \left[\frac{Z_L + Z_0}{Z_L - Z_0} \right] \text{dB}$$

Insertion loss:
In order to achieve matched

conditions, a phase shifter or a transformer is introduced. Ratio of


current in load without any insertion

in load

$$(0.9 + j) 0.5 + (j - 0.9) p.s$$

taking into account losses work

current at no load w/o insertion

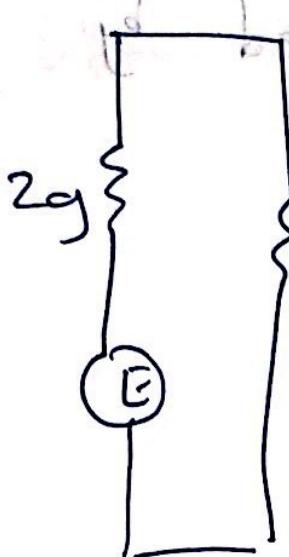


$$I = \frac{E}{Z_g + Z_L}$$

current at load with insertion :-

sending end current is given by

$$I_S = \frac{E}{Z_g + Z_{Sb}} \quad (Z_g \neq Z_s)$$
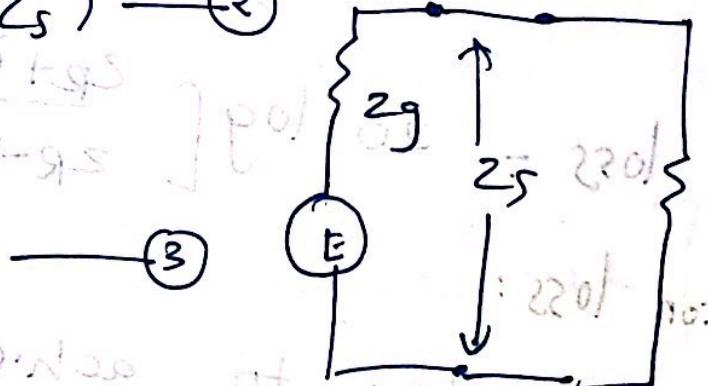
$$Z_S = Z_0 \left(e^{Yl} + k e^{-Yl} \right)$$



$$I_S^0 = \frac{E}{Z_g + Z_0} \left(e^{Yl} + k e^{-Yl} \right)$$

$$= \frac{e^{Yl} - k e^{-Yl}}{e^{Yl} + k e^{-Yl}}$$

$$= E \left(e^{Yl} - k e^{-Yl} \right)$$

$$I_s = \frac{I_{eS}}{2Z_0} (Z_R + Z_0) [e^{rL} - k e^{-rL}] \quad \textcircled{5}$$

By equating $\textcircled{4}$ and $\textcircled{5}$

$$E(e^{rL} - k e^{-rL})$$

$$(e^{rL} + k e^{-rL})$$

$$\frac{Z_g(e^{rL} - k e^{-rL}) + Z_0(e^{rL} + k e^{-rL})}{Z_R(Z_R + Z_0)} = \frac{V_L}{V_L - V_L}$$

$$I_R = \frac{E \cdot 2Z_0}{(Z_R + Z_0)} \left[\frac{(e^{rL})}{(e^{rL} - k e^{-rL})} + \frac{(k e^{-rL})}{(e^{rL} - k e^{-rL})} \right]$$

$$= \frac{2Z_0 (Z_g + Z_R)}{(Z_R + Z_0)(Z_0 + Z_g)}$$

$$= \frac{(Z_R + Z_0)(Z_0 + Z_g)e^{rL} + (Z_0 - Z_g)(-Z_0 + Z_R)e^{-rL}}{(Z_R + Z_0)(Z_0 + Z_g)}$$

$$\frac{I_o}{I_R} = \frac{(Z_R + Z_0)(Z_0 + Z_g)e^{rL} + (Z_0 - Z_g)(-Z_0 + Z_R)e^{-rL}}{2Z_0(Z_g + Z_R)}$$

If we consider a very long line ($\lambda \gg rL$)

$$\frac{I_o}{I_R} = \frac{(Z_R + Z_0)(Z_0 + Z_g)e^{rL}}{2Z_0(Z_g + Z_R)}$$

multiplying λ and dividing by $(s + s)$ 2 $\int_{Z_R}^{Z_L}$

$$\frac{I_0}{I_R} = \frac{(Z_L + Z_0) (Z_R + Z_0)}{2Z_0 (Z_R + Z_L)} e^{\gamma L} \cdot \frac{2 \int_{Z_R}^{Z_L} e^{\gamma L}}{2 \int_{Z_R}^{Z_L}}$$

$$= \frac{Z_L + Z_0}{2 \int_{Z_R}^{Z_L}} \cdot \frac{(Z_R + Z_0)}{2 \int_{Z_R}^{Z_L}} \cdot e^{\gamma L} \cdot \frac{2 \int_{Z_R}^{Z_L} e^{\gamma L}}{Z_R + Z_L}$$

(load end) (source end) (line)

$$= \left(\frac{1}{k_R} \right) \left(\frac{1}{k_S} \right) (k_{RS}) e^{\gamma L}$$

$k \rightarrow$ Reflection factor

From the definition of insertion loss, it is given by

$$I_{loss} = \ln \left[\frac{I_0}{I_R} \right]$$

$$I = \ln \left\{ \left[\frac{1}{k_R} \frac{1}{k_S} \cdot k_{RS} \right] e^{\gamma L} \right\}$$

$$I = \ln(k_{RS}) - \ln(k_R) - \ln(k_S) + \gamma L$$

$$\frac{2 \int_{Z_R}^{Z_L} e^{\gamma L}}{(Z_R + Z_L)(s + s)} = \frac{I}{I_0}$$

Impedance Matching and Transformation

7

03/02 PS Unit - I

77

voltage and current eqn on a zero
dissipation line:

77

$$E = E_R \cosh \gamma s + I_R Z_0 \sinh \gamma s$$

$$I = I_R \cosh \gamma s + \frac{E_R}{Z_0} \sinh \gamma s, \quad j = \beta l$$

7

when $\gamma s = l$

$$E = E_R \cosh \gamma l + I_R Z_0 \sinh \gamma l$$

$$I = I_R \cosh \gamma l + \frac{E_R}{Z_0} \sinh \gamma l$$

$$Z_0 = R_0, \quad \gamma = \alpha + j\beta = j\beta$$

$$\Rightarrow E = E_R \cosh j\beta l + I_R R_0 \sinh j\beta l$$

16 rad

$$E = E_R \cos \beta l + [0] I_R R_0 \sin \beta l, \quad (\text{sin odd fw})$$

$$I = I_R \cos \beta l + [0] \frac{E_R}{R_0} \sin \beta l$$

-1

Case (i):

When line is open circuited at the receiving end, the voltage and current

eqn is given by $I_R = 0$

$$E_{OC} = E_R \cos \beta l$$

$$\frac{E}{Z_0} \cos \beta l = \frac{E}{Z_0}$$


$$I_{OC} = j \frac{E_R}{R_0} \sin \beta l$$

$$\beta = \frac{2\pi}{\lambda}$$

we know that

$$E_{OC} = E_R \cos \frac{2\pi}{\lambda} l$$
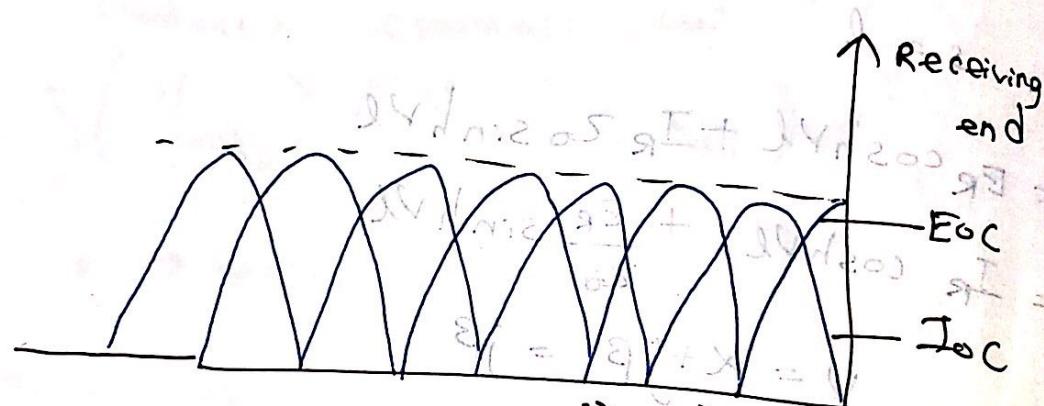
$$I_{OC} = j \frac{E_R}{R_0} \sin \frac{2\pi}{\lambda} l$$



Case-ii) When line is short circuited at the receiving end, the voltage and current is given by eqn


$$E_{SC} = j \frac{I_R}{R_0} \sin \beta l$$

$$I_{SC} = \frac{I_R}{R_0} \cos \beta l$$

$$\beta = \frac{2\pi}{\lambda}$$

$$E_{SC} = j \frac{I_R}{R_0} \sin \frac{2\pi}{\lambda} l$$
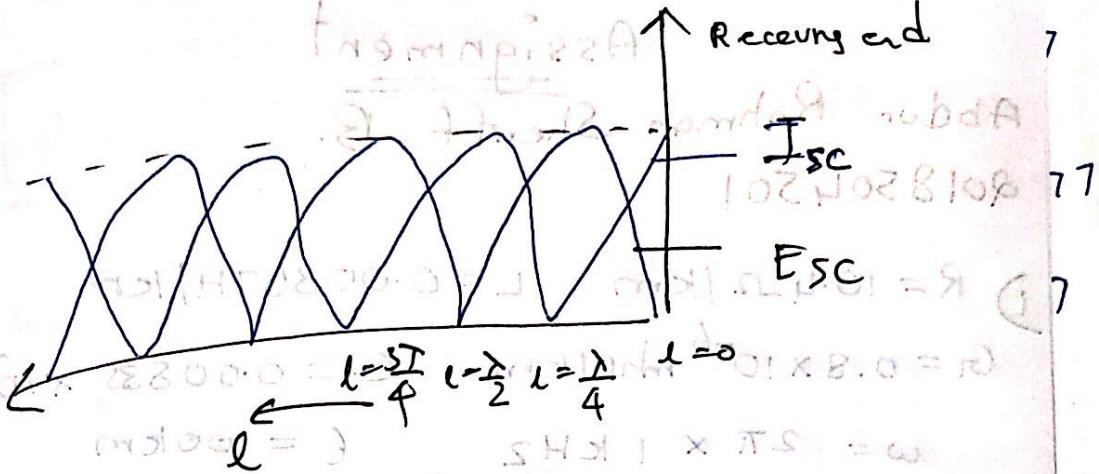
$$I_{SC} = \frac{I_R}{R_0} \cos \frac{2\pi}{\lambda} l$$



Case (iii) :-

When the line is terminated in reflected wave is absent
 $(K=0)$

voltage and current equation in terms of

k :

$$E = \frac{E_R}{2} \left(1 + \frac{Z_0}{Z_R} \right) e^{j(kl + \phi)} + \frac{Z_0}{2} \left[\frac{Z_R + Z_0}{Z_R - Z_0} \right] e^{-j(kl + \phi)}$$

$$= \frac{E_R}{2} \left[\frac{2n + 2o}{Z_R} \right] e^{j(kl + \phi)} + \frac{E_R}{2} \left[\frac{Z_R - Z_0}{Z_R + Z_0} \right] e^{-j(kl + \phi)}$$

$$= \frac{E_R (Z_R + Z_0)}{2 Z_R} \left[e^{j(kl + \phi)} + e^{-j(kl + \phi)} \right]$$

$$I = \frac{I_R (Z_R + Z_0)}{2 Z_R} \left[e^{j(kl + \phi)} - e^{-j(kl + \phi)} \right]$$

$$= \frac{I_R (Z_R + Z_0)}{2 Z_R} \cdot 2 Z_0 \cdot \sin(kl + \phi)$$

$$= I_R \sin(kl + \phi)$$


when there is no reflection, it will be ideal case

$$Z_R = Z_0$$

$$\Rightarrow \alpha = 0$$

$$E = E_R e^{j\phi_R} \text{ similarly } I = I_R e^{j\phi_R}$$
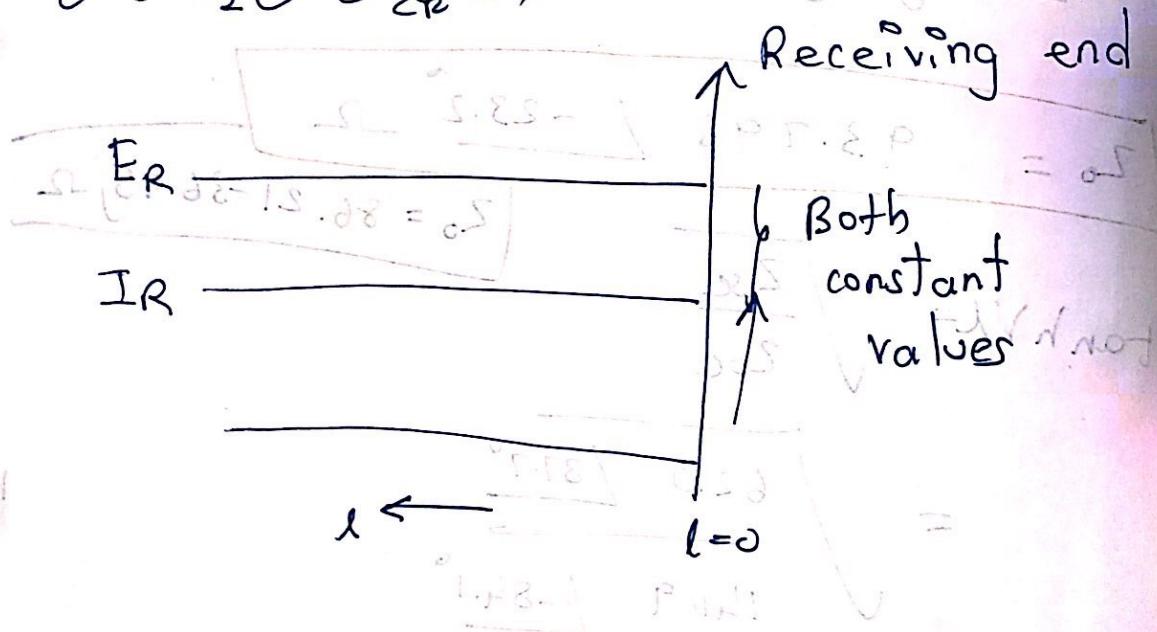
$$E = E_R \sqrt{1 + \frac{Z_0}{Z_R}} e^{j\phi_R}$$



Note: In case of open circuit, current is minimum at load point at a distance of $\frac{\lambda}{4}$ from the load point we have current maximum

Distance between two successive

$$\text{minima or maxima} = \frac{\lambda}{2}$$

Distance b/w maxima and minima $= \frac{\lambda}{2}$

$$= \frac{\lambda}{4}$$

$$|+3\rangle + |+3\rangle = \text{minima}$$

08/09

Standing Waves

→ stationary wave

A → antinodes

Max current or $|+3\rangle - |-3\rangle$ in standing wave

N → nodes or current $|+3\rangle + |-3\rangle$ in standing wave

O voltage or $|+3\rangle - |-3\rangle$ at nodal point

When no standing wave is present,
it means there isn't any reflection.

That line is called smooth line:

That ratio (SWR) :

standing wave ratio of max to min magnitudes

of V or I standing wave ratio

waves is called standing wave ratio

and it is denoted by $S = \frac{|+3\rangle - |-3\rangle}{|+3\rangle + |-3\rangle}$

$$S = \left| \frac{E_{\max}}{E_{\min}} \right| \quad \text{or} \quad S = \left| \frac{\frac{I_{\max}}{I_{\min}}}{\frac{I_{\min}}{I_{\max}}} \right|$$

consider

$|E^+| \rightarrow$ magnitude of incident voltage

$|E^-| \rightarrow$ magnitude of reflected voltage

$$E_{\max} = |E^+| + |E^-|$$

$$E_{\min} = |E^+| - |E^-|$$

$$S = \frac{|E^+| + |E^-|}{|E^+| - |E^-|}$$

Now substitute in $S = \frac{|E^+| + |E^-|}{|E^+| - |E^-|}$

÷ throughout by $|E^+|$

$$S = \frac{1 + \frac{|E^-|}{|E^+|}}{1 - \frac{|E^-|}{|E^+|}}$$

$$S = \frac{1 + k}{1 - k}$$

$k = \text{reflection coefficient}$

Now $S = S/k + k$ in terms of S

$$S - S/k = 1 + k$$

$$k = \frac{S-1}{S+1}$$

Case 2

(ii) When $Z_R = Z_0$

$$k=0 \Rightarrow \boxed{S=1}$$

(iii) $k_C = 1$

but $k_C = \frac{s-1}{s+1}$ to get option

$s+1 = s-1$

$\boxed{S=\infty}$

(iv) $k_C = -1$ for $S_R I + (Z_R)_{\text{d.c.}} = 0$

$$\left(\frac{s-1}{s+1} \right) S_R I + \left(\frac{Z_R}{s+1} \right)_{\text{d.c.}} = 0$$

$$-s+1 = \frac{s-1}{s+1}$$

$$\boxed{S=0}$$

S will range from 0 to ∞

(v) When $\phi Z_R > 20$

$$k > \frac{Z_R - 20}{Z_R + 20} \Rightarrow 0 < k < 1 \Rightarrow 0 < S < \infty$$

$$\boxed{S = \frac{R_R (s+1) Z_R}{R_0}}$$

$\phi = \sqrt{\text{Imaginary component}} = \sqrt{Z_R^2 - R_R^2}$

$$(iii) Z_R < Z_0$$

$$k = \frac{Z_R - Z_0}{Z_R + Z_0} \Rightarrow -1 < k < 0$$

$0 < k < 1$

$$S = \frac{R_o}{R_R}$$

voltage eqⁿ of zero dissipation line
in terms of k' : $1-k = 1+k'$

$$E = E_R e^{j\beta l}$$

$$\infty = 2$$

$$E = E_R \cosh(j\beta l) + I_R Z_0 \sinh(j\beta l)$$

$$= E_R \left(\frac{e^{j\beta l} + e^{-j\beta l}}{2} \right) + I_R Z_0 \left(\frac{e^{j\beta l} - e^{-j\beta l}}{2} \right)$$

$$= \frac{e^{j\beta l}}{2} [I_R Z_R + I_R Z_0] + \frac{e^{-j\beta l}}{2} [I_R Z_R - I_R Z_0]$$

$$= \frac{e^{j\beta l}}{2} I_R \left[(Z_R + Z_0) + e^{-2j\beta l} \frac{(Z_R - Z_0)}{(Z_R + Z_0)} \right]$$

~~$$= \frac{I_R (Z_R + Z_0)}{2} e^{j\beta l} \left[1 + \frac{Z_R - Z_0}{Z_R + Z_0} e^{-j\phi} \right]$$~~

$$= \frac{I_R (Z_R + Z_0)}{2} e^{j\beta l} \left[1 + \frac{Z_R - Z_0}{Z_R + Z_0} e^{-j\phi} \right]$$

$\frac{Z_R - Z_0}{Z_R + Z_0}$ = reflection coeff Magnitude of $k = \phi$

$$\begin{aligned}
 &= \frac{I_R}{2} e^{j\beta l} \left[\frac{(1 + jk)^{-j(\phi - 2\beta l)}}{1 + jk} \right] \\
 &= \frac{I_R}{2} e^{j\beta l} \left[\frac{(1 + jk)^{-j(\phi - 2\beta l)}}{1 + jk} \right] \\
 &\quad \text{at } q = 2.25 \quad \text{distancia} \\
 &\quad E_I = \frac{I_R}{2} e^{j\beta l} \left[1^0 + jk \right] \frac{\phi - 2\beta l}{1 + jk} \\
 &\quad \text{first term represents the incident wave} \\
 &\quad + \text{second term represents the reflected wave.}
 \end{aligned}$$

Voltage will be maximum when both incident and reflected wave are in phase

$$\phi - 2\beta l = 0$$

$$\Rightarrow E_{max} = \frac{I_R}{2} e^{j\beta l} \left[1^0 + jk \right]$$

for voltage minimum, $I\omega$ and $R\omega$

will be out of phase

$$\phi - 2\beta l = \pi$$

$$E_{min} = \frac{I_R}{2} e^{j\beta l} \left[1^0 + jk \right] \pi$$

$$E_{min} = \frac{I_0}{2} (Z_R + Z_0) e^{j\beta l} [1 - |k|]$$

$$S = \frac{E_{max}}{E_{min}} = \frac{1 + |k|}{1 - |k|}$$

Input impedance line: $Z_S = \frac{E_S}{I_S}$

of a zero dissipation system

distortionless

$$V = j\beta l$$

$$\sinh j = \cos j$$

$$\sinh j = j \sin$$

$$\frac{E_S}{I_S} = \frac{E_R \cos \beta l + j I_R R_o \sin \beta l}{I_R \cos \beta l + j \frac{E_R}{R_o} \sin \beta l}$$

$$H_d = \frac{E_R + j I_R R_o \tan \beta l}{I_R + j \frac{E_R}{R_o} \tan \beta l}$$

$$Z_S = \frac{j k [Z_R + j R_o \tan \beta l]}{j k [1 + j \frac{Z_R}{R_o} \tan \beta l]}$$

$$Z_{in} = \frac{R_o [Z_R + j R_o \tan \beta l]}{R_o + j Z_R \tan \beta l}$$

I/p imp. terms of k

$$z_s = z_0 \frac{[z_R \cosh j\beta l + z_0 \sinh j\beta l]}{[z_0 \cosh j\beta l + z_R \sinh j\beta l]}$$
$$= z_0 \cdot \frac{[z_R \cdot \frac{e^{j\beta l} + e^{-j\beta l}}{2} + z_0 \cdot \frac{e^{j\beta l} - e^{-j\beta l}}{2}]}{[z_0 \cdot \frac{e^{j\beta l} + e^{-j\beta l}}{2} + z_R \cdot \frac{e^{j\beta l} - e^{-j\beta l}}{2}]}$$
$$= z_0 \frac{\left[\frac{e^{j\beta l}}{2} (z_R + z_0) + \frac{e^{-j\beta l}}{2} (z_R - z_0) \right]}{\left[\frac{e^{j\beta l}}{2} (z_0 + z_R) - \frac{e^{-j\beta l}}{2} (z_R - z_0) \right]}$$
$$= z_0 \left[\frac{e^{j\beta l}}{2} (z_R + z_0) \right] \frac{\left[1 + \frac{e^{-2j\beta l}}{2} \left(\frac{z_R - z_0}{z_R + z_0} \right) \right]}{\left[1 - \frac{e^{-2j\beta l}}{2} \left(\frac{z_R - z_0}{z_R + z_0} \right) \right]}$$
$$z_s = z_0 \frac{\frac{e^{j\beta l}}{2} (z_R + z_0)}{\left[1 - \frac{e^{-2j\beta l}}{2} \left(\frac{z_R - z_0}{z_R + z_0} \right) \right]}$$
$$k = \frac{z_R - z_0}{z_R + z_0}$$

$$z_s = z_0 \frac{\left[1 + |k| e^{j\phi} e^{-j2\beta l} \right]}{\left[1 - |k| e^{j\phi} e^{-j2\beta l} \right]}$$
$$z_s = z_0 \frac{\left[1 + |k| e^{j(\phi - 2\beta l)} \right]}{\left[1 - |k| e^{j(\phi - 2\beta l)} \right]}$$
$$z_s = z_0 \left[\frac{1 + |k| \overbrace{e^{j(\phi - 2\beta l)}}^{\phi - 2\beta l}}{1 - |k| \overbrace{e^{j(\phi - 2\beta l)}}^{\phi - 2\beta l}} \right]$$

$$Z_S = \frac{R_o}{1 + k} \left[\frac{\phi - 2\beta l}{\phi + 2\beta l} \right]$$

$$Z_{in} = R_o \left[\frac{e^{j\phi} + k}{e^{j\phi} - k} \right] \left[\frac{\phi - 2\beta l}{\phi + 2\beta l} \right]$$

case-i:

I_p imp. will be maximum when they are in phase (i.e) $\phi - 2\beta l = 0$ or $\phi = 2\pi l$.

$$(Z_{in} - Z_{in\max}) = R_o \left[\frac{1 + jk}{1 - jk} \right]$$

$$\boxed{Z_{in\max} = R_o S} \quad S = SWR$$

case-ii:

I_p impedance will be minimum

at a distance of $\frac{\lambda}{4}$, from maximum point.

$$s = \frac{\phi}{2\beta} + \frac{\lambda}{4} \Rightarrow s = \frac{\phi}{2(\frac{2\pi}{\lambda})} + \frac{\lambda}{4} = \frac{\phi}{4\pi} + \frac{\lambda}{4}$$

$$s = \frac{\frac{\phi\lambda}{4\pi} + \frac{\lambda}{4}}{\lambda + \frac{4\pi}{\lambda}} = \frac{\lambda(\phi + \pi)}{\lambda^2 + 4\pi^2}$$

$$\boxed{s = \frac{\phi + \pi}{2\beta}}$$

$$z_{in_m} = R_o \left[\frac{1 + |k| \sqrt{\phi - 2\beta l}}{1 - |k| \sqrt{\phi - 2\beta l}} \right]$$

$$= R_o \left[\frac{1 + |k| \frac{1}{\pi}}{1 - |k| \frac{1}{\pi}} \right]$$

$$= R_o \left[\frac{1 + |k|}{1 + |k|} \right]$$

$\phi - 2\beta l = \pi$

$$\phi = \pi + 2\beta l$$

~~At end of loop from left to right~~

Input impedance of open and short circuited

line: and both ends are 90° (i)

Short circuited line: $+jS$

$$Z_S = R_o \left[\frac{Z_R + jR_o \tan \beta S}{R_o + jZ_R \tan \beta S} \right] \quad R_o = 25$$

For S.C $Z_R = 0 \Rightarrow Z_{SC} = jR_o \tan \beta S$


$$\frac{Z_{SC}}{R_o} = j \tan \beta S$$

$$S = 0 \Rightarrow j \tan 0 = 0$$

$$S = \frac{\lambda}{4} \Rightarrow j \tan \frac{\lambda}{4} \cdot \frac{62.8 \text{ rad}}{\lambda} = j\infty$$

$$S = \frac{\lambda}{2} \Rightarrow j \tan \frac{\lambda}{2} \cdot \frac{62.8 \text{ rad}}{\lambda} = 0$$
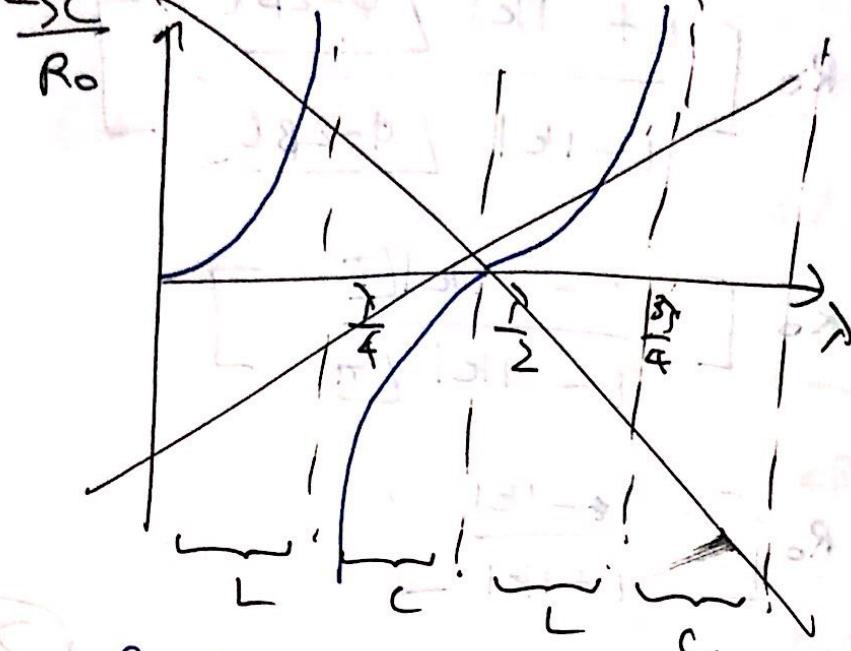
$$S = \frac{3\lambda}{4} \Rightarrow j \tan \frac{3\lambda}{4} \cdot \frac{62.8 \text{ rad}}{\lambda} = -j\infty$$



For the first quarter wavelength, a sc line acts as an inductance.
for the next quarter it acts as a capacitance

i) Open circuited line:

$$Z_S = R_0 \left[\frac{Z_R + jR_0 \tan\beta s}{R_0 + jZ_R \tan\beta s} \right]$$

$Z_R = \infty$ for OC

$$Z_{S_{OC}} = Z_R R_0 \left[\frac{1}{1 + j \frac{R_0}{Z_R} \tan\beta s} \right]$$

$$= R_0 \left[\frac{jZ_R}{Z_R} \left[\frac{1 + j \frac{R_0}{Z_R} \tan\beta s}{\frac{R_0}{Z_R} + j \tan\beta s} \right] \right]$$

$$Z_{R_{oc}} = R_0 \left[\frac{1}{j \tan\beta s} \right]$$

$$\boxed{Z_{OC} = -j R_0 \cot\beta s}$$

At infinity impedance \rightarrow parallel
LC circuit


Low impedance \rightarrow series
LC circuit

$$s = \infty \Rightarrow -j \cot \alpha = -j \infty$$

$$s = \frac{\lambda}{4} \Rightarrow -j \cot \frac{\lambda}{4} \cdot \frac{2\pi}{\lambda} = 0$$

$$s = \frac{\lambda}{2} \Rightarrow -j \cot \frac{\lambda}{2} \cdot \frac{2\pi}{\lambda} = j \infty$$
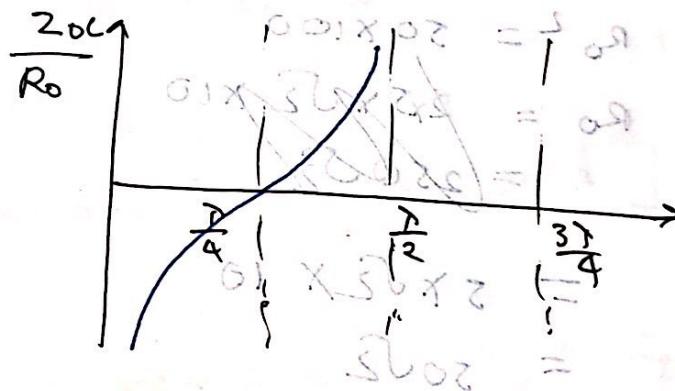
$$s = \frac{3\lambda}{4} \Rightarrow -j \cot \frac{3\lambda}{4} \cdot \frac{2\pi}{\lambda} = 0 \quad = \infty$$



Impedance Matching

\rightarrow In order to have (max) power transfer

~~what are wave lines?~~

i) Quarter wavelength: $\left[\frac{\lambda}{4} \right]$


$$Z_{in} = R_o \left[\frac{Z_R + j R_o \tan\left(\frac{2\pi}{\lambda}\right)\left(\frac{\lambda}{4}\right)}{R_o + j Z_R \tan\left(\frac{2\pi}{\lambda}\right)\left(\frac{\lambda}{4}\right)} \right]$$

Remove common factor one of two

$$= R_o \left[\frac{Z_R + j R_o}{R_o + j Z_R} \right] \stackrel{Z_R}{=} \frac{R_o^2}{Z_R}$$

$$Z_{in} = \frac{R_o^2}{Z_R}$$

$$R_o = 70.71\Omega$$

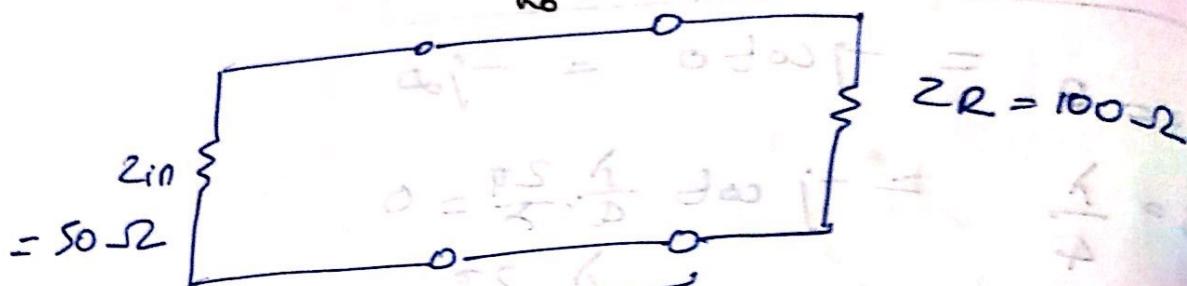

$$50 = \frac{R_o^2}{100}$$

$$R_o^2 = 50 \times 100$$

$$R_o = \sqrt{25 \times 50} \times 10$$

$$= 250\sqrt{2}$$

$$= 5 \times \sqrt{2} \times 10$$

$$= 50\sqrt{2}$$

$$R_o = 70.71\Omega$$

ii) Half wavelength: $(\frac{\lambda}{2})$ and $\frac{Z_o + jR_o \tan(\frac{2\pi}{\lambda})(\frac{\lambda}{2})}{Z_o - jR_o \tan(\frac{2\pi}{\lambda})(\frac{\lambda}{2})}$

$$Z_{in} = R_o \frac{Z_o + jR_o \tan(\frac{2\pi}{\lambda})(\frac{\lambda}{2})}{Z_o - jR_o \tan(\frac{2\pi}{\lambda})(\frac{\lambda}{2})}$$

$$Z_{in} = R_o \left(\frac{Z_o}{R_o} \right)$$

$$Z_{in} = Z_R$$

when no match is possible, half wavelength is used as a one-to-one transformer

iii) Eighth waveline:

$$Z_{in} = R_0 \left[\frac{Z_R + j R_0 \tan \left(\frac{2\pi}{\lambda} \right) \left(\frac{1}{8} \right)}{R_0 + j Z_R \tan \left(\frac{2\pi}{\lambda} \cdot \frac{\lambda}{8} \right)} \right]$$

$$Z_{in} = R_0 \left[\frac{\frac{Z_R + j R_0}{(S+1)}}{\frac{R_0 + j Z_R}{(S+1)}} \right] \quad |Z_{in}| = R_0 \frac{\sqrt{Z_R^2 + R_0^2}}{\sqrt{R_0^2 + Z_R^2}}$$

$$|Z_{in}| = R_0$$

If transforms any resistance to an impedance with a magnitude equal to R_0 of the line.

[Quarter waveline is usually used]

problem:
A lossless transmission line with $Z_0 = 50\Omega$ is terminated in a load $50 + j50\Omega$. Find the following:
(i) Reflection at load

(ii) VSWR

(iii) Admittance of load at a distance $\lambda/4$

$$Z_L = 50 + j50\Omega$$

$$Z_0 = 50\Omega$$

$$Z_L' = \frac{Z_L - Z_0}{Z_0} = 1 + j$$

(normalized load imp)

$$K = \frac{Z_R - Z_0}{Z_R + Z_0} = \frac{50 + 50j - 50}{50 + 50j + 50} = \frac{j50}{100 + 50j}$$

$$= \frac{j}{2+j} = \frac{1}{1-2j} \cdot \frac{1+2j}{1+2j} = \frac{1+2j}{5}$$

$$k = \frac{1+2j}{5}$$

$$k = 0.2 + 0.4j \quad |k| = \sqrt{0.4^2 + 0.2^2} = \sqrt{0.24} = 0.49$$

$$k = 0.44 \quad |k| = 0.44$$

(iii)

$$S = \frac{v_s \omega R}{1 - |k|}$$

$$S = \frac{1 + 0.44}{1 - 0.44} = \frac{1.44}{0.56} = 2.57$$

$$S = 2.57$$

Range
Normalized
 $\rightarrow 1-20$
 $k \rightarrow 0-1$

$$(iii) Y_L' = \frac{1}{Z_L'}$$

$$\text{(Normalized load admittance)} = \frac{1}{1+j} = \frac{1-j}{(1+j)(1-j)} = \frac{1-j}{2} = 0.5 - 0.5j$$

~~0.5 - 0.5j~~

$$y_L' \times 50 = Y_L$$

$$Y_L = 25 - 25j \text{ (load admittance)}$$