


Electrical analogues of Mechanical Rotational Systems

(1) Torque - Voltage duality

Mechanical Rotational S/m

i/p: torque

o/p: angular velocity

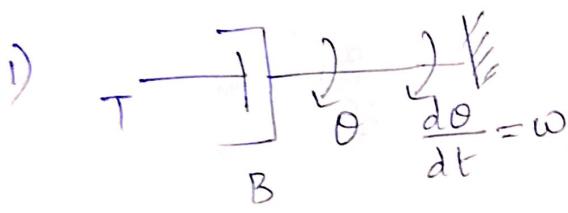


$$T = J \frac{d\omega}{dt} = J \omega$$

Electrical S/m


i/p: voltage

o/p: current

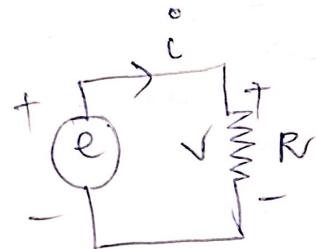


$$V = e = iR$$

$$i = \frac{V}{R}$$

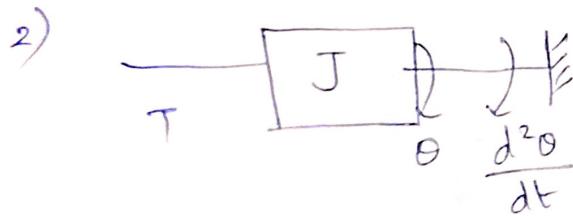

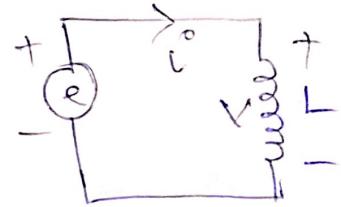
$$T = J \frac{d^2\theta}{dt^2} = J \frac{d\omega}{dt}$$




$$V = e = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int V dt$$

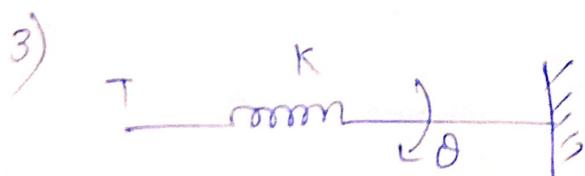

$$T = K\theta = K \int \omega dt$$

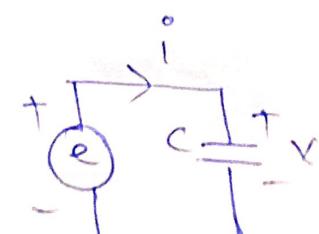

$$V = e = \frac{1}{C} \int i dt$$

$$i = C(V/dt)$$

Torque - Voltage Analogy - Quantities


Item	Mechanical	Electrical s/m.
	Rotational s/m	voltage (e, v)
Independent variable (θ_{ip})	Torque, T	
Dependent variable (ϕ_{sp})	Angular velocity (ω)	current (i)
	Angular displacement (θ)	charge (q)
Dissipative element	Rotational co-eff of dash-pot (B)	Resistance (R)
Storage element	Moment of Inertia (J)	Inductance (L)
	Stiffness of spring (K)	Inverse of capacitance (Y_C)
Physical law	Newton's second law $\sum T = 0$	KVL $\sum V = 0$

2) Torque-current analogy


Mechanical rotational s/m

i/p: Torque

o/p: Angular velocity (ω)

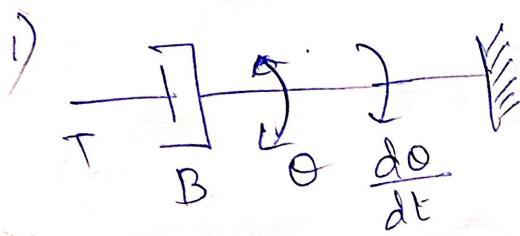


$$T = B \frac{d\theta}{dt} = B\omega$$

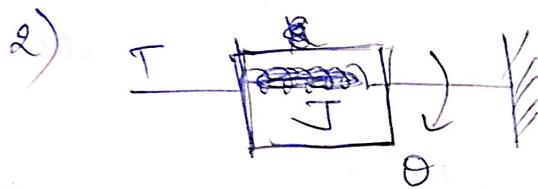

$$T = J \frac{d^2\theta}{dt^2}$$

$$T = J \frac{d\omega}{dt}$$

3)

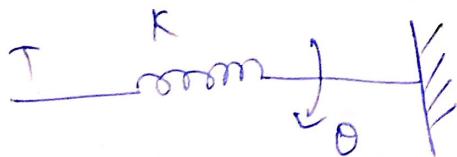


$$T = K\theta$$

$$= K \int \omega dt$$

Electrical s/m


i/p: current

o/p: voltage

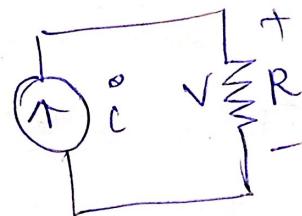


$$V = iR$$

$$V = iR$$

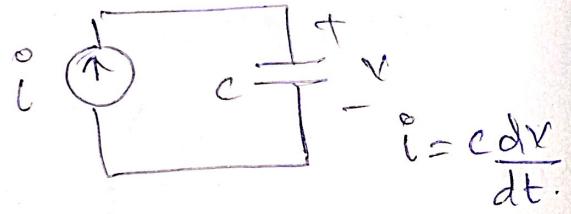

$$i = c \frac{dv}{dt}$$

$$V = \frac{1}{c} \int i dt$$

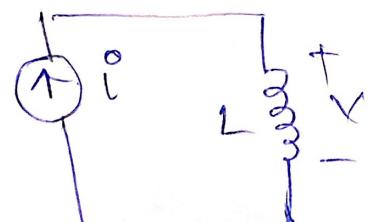

$$i = L \int v dt$$

$$V = L \frac{di}{dt}$$

Analogy Quantities in Torque - current

<u>Item</u>	<u>Mechanical</u> Rotational S/m	<u>Electrical</u> S/m.
Independent Variable (i/p)	Torque (T)	current (i)
Dependent variable (o/p)	Angular velocity (ω) Angular displacement (θ)	voltage (V) flux (ϕ)
Dissipative element	Damper (B)	conductance (Y_R) $= Y_R$.
Storage element	Moment of Inertia (J) Stiffness of spring (K)	capacitance (C) Inverse of inductance (Y_L)
Physical law	Newton's II. law $\sum T = 0$.	KCL $\sum i = 0$.

comparison

P-R S/m

T (i/p)

ω (o/p)

θ

B

J

K

F-X

V

q

R

L

Y_C

F-C

i

V



ϕ

Y_R

C

Y_L

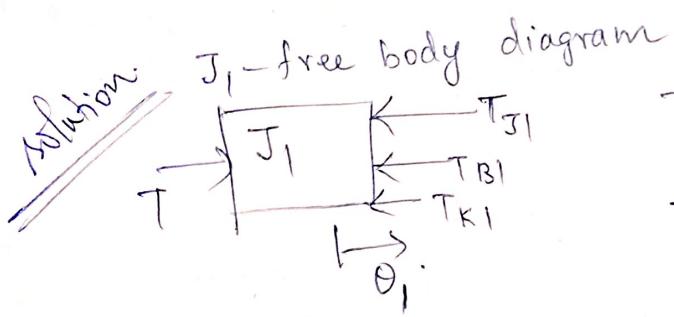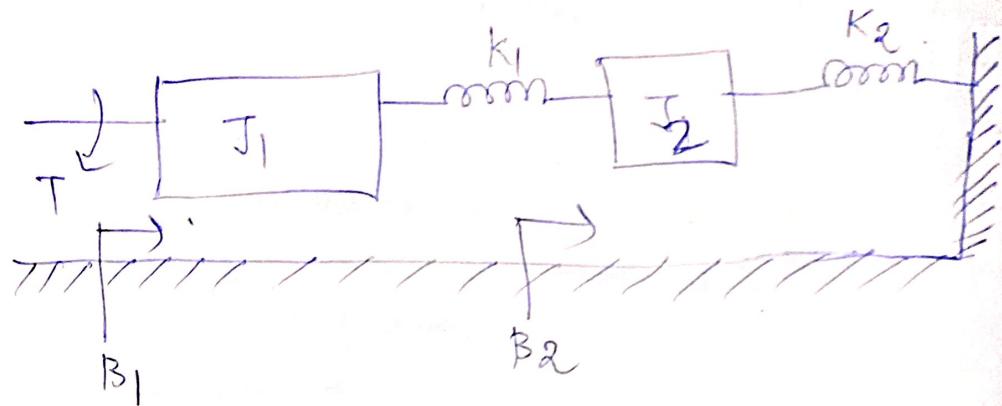Eg:
1) Write the differential equation of the mechanical-rotational sys, Draw T-V & T-e analogous circuits and verify using mesh and node equations.




$$T_{J1} = J_1 \frac{d^2\theta_1}{dt^2}$$

$$T_{B1} = B_1 \frac{d\theta_1}{dt}$$

$$T_{K1} = K_1 (\theta_1 - \theta_2)$$

J_2 → free-body diagram

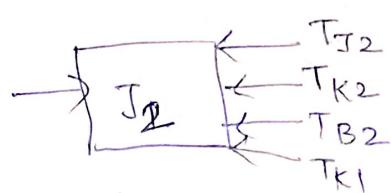

$$T_{J2} = J_2 \frac{d^2\theta_2}{dt^2}$$

$$T_{K2} = K_2 \theta_2$$

$$T_{B2} = B_2 \frac{d\theta_2}{dt}$$

$$T_{K1} = K_1 (\theta_2 - \theta_1)$$

$$\textcircled{1} \Rightarrow J_1 \frac{d^2\theta_1}{dt^2} + B_1 \frac{d\theta_1}{dt} + K_1 (\theta_1 - \theta_2) = T$$


$$\textcircled{2} = J_2 \frac{d^2\theta_2}{dt^2} + B_2 \frac{d\theta_2}{dt} + K_2 \theta_2 + K_1 (\theta_2 - \theta_1) = 0$$

→ Rewrite everything - in terms of angular velocity.

$$\text{wkt} \quad \theta = \int \omega dt \quad \frac{d^2\theta}{dt^2} = \frac{d\omega}{dt} \quad \frac{d\theta}{dt} = \omega$$

$$\begin{aligned} \therefore J_1 \frac{d\omega_1}{dt} + B_1 \omega_1 + K_1 \int (\omega_1 - \omega_2) dt &= T \quad \text{--- (3)} \\ J_2 \frac{d\omega_2}{dt} + B_2 \omega_2 + K_2 \int \omega_2 dt + K_1 \int (\omega_2 - \omega_1) dt &= 0 \quad \text{--- (4)} \end{aligned}$$

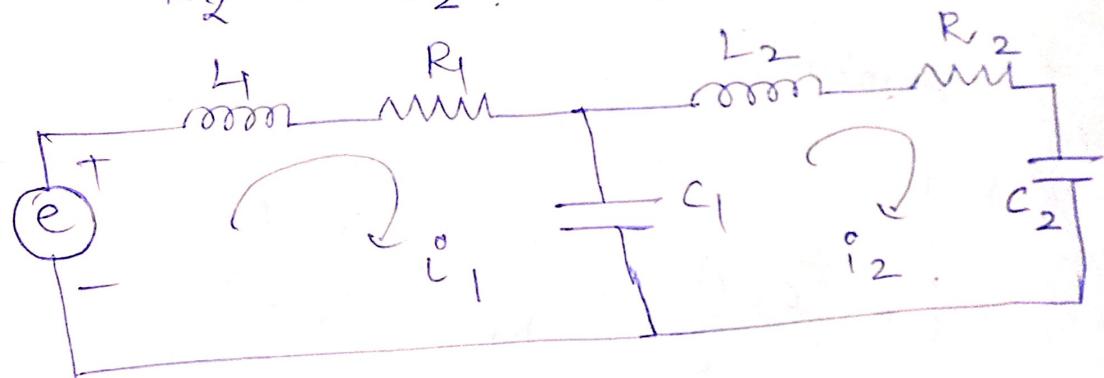(i) $\underline{T = V}$: $J_1 \rightarrow L_1, T \rightarrow V \text{ or } e, J_2 \rightarrow L_2$
 $B_1 \rightarrow R_1, B_2 \rightarrow R_2, K_1 \rightarrow C_1$
 $K_2 \rightarrow C_2$. & $\omega_1 = i_1, \omega_2 = i_2$.



$$\text{KVL} \quad \begin{aligned} L_1 \frac{di_1}{dt} + R_1 i_1 + \frac{1}{C_1} \int (i_1 - i_2) dt &= e \quad \text{--- (5)} \end{aligned}$$

$$\begin{aligned} L_2 \frac{di_2}{dt} + i_2 R_2 + \frac{1}{C_2} \int i_2 dt + \frac{1}{C_1} \int (i_2 - i_1) dt &= 0. \end{aligned}$$


→ (6)

(ii) T-C analogy

$$J_1 \rightarrow C_1 \quad B_1 = \frac{V}{R_1}$$

$$J_2 \rightarrow C_2 \quad B_2 = \frac{V}{R_2}$$
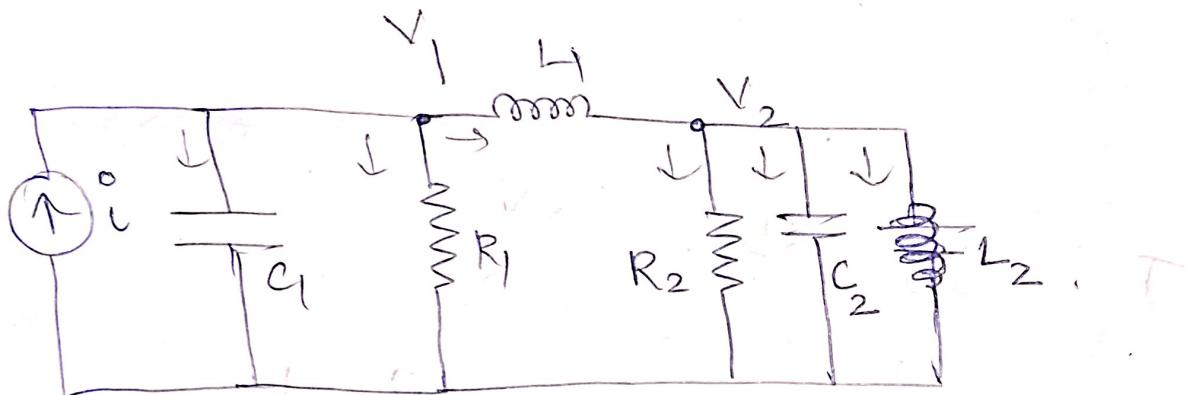
$$T \rightarrow i^o \quad \omega_1 \rightarrow V_1 \quad \omega_2 \rightarrow V_2$$



node equations

KCL

$$i^o = C_1 \frac{dV_1}{dt} + \frac{V_1}{R_1} + \frac{1}{L_1} \int (V_1 - V_2) dt \quad \textcircled{7}$$

$$\frac{1}{L_1} \int (V_1 - V_2) dt = \frac{V_2}{R_2} + C_2 \frac{dV_2}{dt} + \frac{1}{L_2} \int V_2 dt.$$

$$C_2 \frac{dV_2}{dt} + \frac{V_2}{R_2} + \frac{1}{L_2} \int V_2 dt + \frac{1}{L_1} \int (V_2 - V_1) dt = 0 \quad \textcircled{8}$$