

Date:

Dr. S. Vasuki

Electronics Engg.

MIT Campus.

Transmission Lines and Wave Guides.

Unit-I

**CADD<sup>®</sup>**  
CENTRE

[www.caddcentre.ws](http://www.caddcentre.ws)

4/7/15

## Unit - I

Date:

### Introduction to transmission lines

\* Tr-ions S/m's are used to transfer energy from one point to another.

\* The energy may be

- Sound
- Electrical power
- Digital / Analog / optical signal
- Or any combination of the above
- Audio / video / Data.

### \* General properties of tr-ion S/m's

#### Incident waves - Waves



emerging directly from the sender.

\* The signal propagate along a tr-ion path down the length of the tunnel (tr-ion line)

\* Impedance - opposition caused by the air mass in the tunnel.

\* Imp. is determined by the physical characteristics of the tunnel. (width, height....)

**CADD®  
CENTRE**

[www.caddcentre.ws](http://www.caddcentre.ws)

- \* characteristics imp ( $z_0$ ) → The imp. related to the characteristics of the tunnel.
- \* Bend or discontinuities along the line walls cause a change - reflections in the signal propagation path.
- \* The walls do absorb some energy - weaken - attenuated the propagated energy.
- \* amplitude attn./unit length =  $\alpha$
- \* frequency attenuation - dispersion
- \* propagation velocity - speed.
  - velocity of sound waves - 331 m/sec
  - velocity of electrical waves -  $3 \times 10^8$  m/sec
- \* Tunnel is infinitely long → Signal will totally attenuated or absorbed
- \* Tunnel is not infinitely long - Signal will be reflected
- Reflection co-efficient = 
$$\frac{\text{Reflected wave}}{\text{Incident wave}}$$
- \* To avoid this → Put some good absorption material at the end of the tunnel.

+ creating matching termination match off

The propagation characteristics of a long tunnel in a tunnel of finite length.

$$\text{Tr.-in co-eff} = \frac{\text{Received Signal}}{\text{Incident Signal}}$$

\* Time propagation delay can be specified by,

- seconds

- Periodic Time ( $T$ ) =  $(1/f)$  Sec's

- Phase delay -  $2\pi$  radians in a period Time  $T$ .

Standing wave Ratio(SWR) =  $\frac{V_{max}}{V_{min}}$

# Types of Electrical transmission line

## 1. Twin lines


- \* Twin line spaced by a polyethylene dielectric.

- \* Used at relatively low frequencies.

$$\text{ch. imp. } Z_0 = 300 \Omega$$

$$f_{\text{req}} = \text{VHF}$$

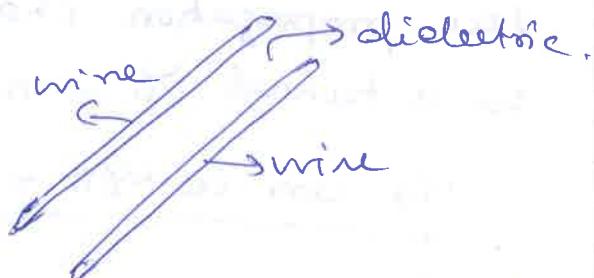also used at Low & Medium freq  
radio tr-eis




\* TP lines & overhead power lines.

## 2. Co-axial cable

- \* Carrying HF signals

- \* Connects TV sets to antenna

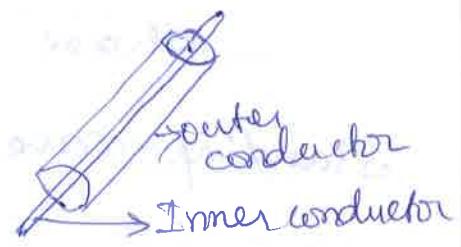- \* Two wire line, but the outer conductor forms a ~~outer~~ shield around the inner conductor to prevent radiation.



outer conductor

Inner conductor


## 3. Metallic wave guide

- \* Tuned or. w/c

- \* HF Tr-cos line  $\approx$  Low attn. & radiation losses

- \* But expensive  $\therefore$  it metallic construction (copper)

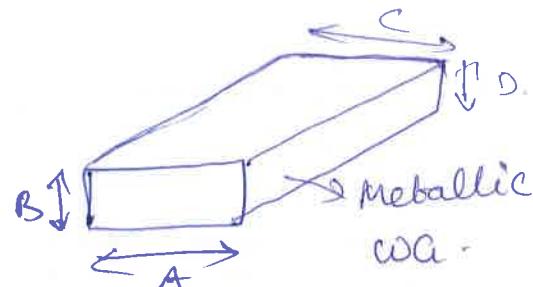
- \* Also relatively heavy & lacks flexibility


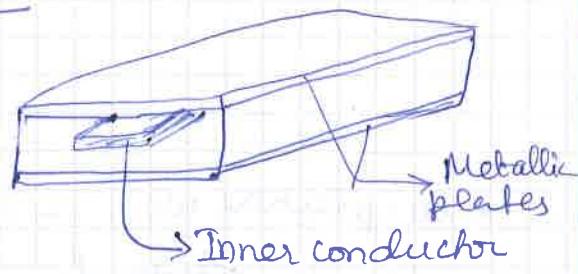
#### 4. Strip line

\* Similar to a flattened co-axial line.

\* Advantage - it can be easily constructed with Integrated Circuits.



#### 5) Micro-strip line

\* Variant of the strip line, with part of the "shield" removed.



#### (A) Slot line


\* Useful line for HF transmission



#### (B) Co-planar waveguide

\* One variant of the WCA.

\* Used for MIC.

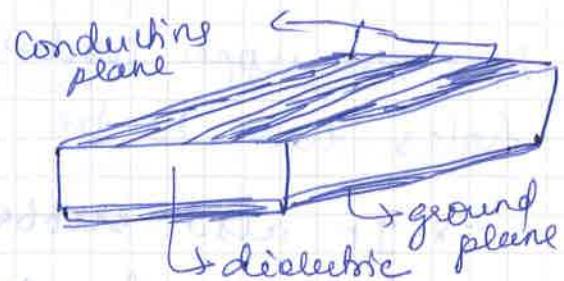

\* For minimum loss

→ W<sub>4</sub>, co-axial line and strip line

find difficult in connecting external comp. to the inner conductor

\* Co-planar wave → Better in this respect

    | finds favour in Monolithic MIC (MMIC)

\* ∵ It allows easy series and  $\Pi$ d connections to external electrical components.

\* Microstrip line: - Useful for making series connections but not  $\Pi$ d connections.

\* ∵ the only way through to the gnd. plane is either through or around the edge of the substrate.

\* This is true ∵ when a sc is required b/w the upper conductor and the gnd plane, holes have to be drilled through the substrate.

\* It also suffers from radiation losses.

\* can be made easily & conveniently & it is ∴ used extensively.

## Transmission Line - General Solution

Date:

\* Lumped ckt elements

\* Distributed elements

\* Analysis of the circuit is also different.

\* The voltage drop across each series increment of line, the voltage applied to each increment of shunt admittance is a variable.

∴ The shunted current is a variable along the line.

Hence, the  $\Delta V$  around the loop is not a constant, but varies from pt to pt along the line.

Notations used will be defined as follows

R - series Resistance  $\Omega/\text{unit length of line}$

L - series Inductance  $H/\text{unit length}$

C - capacitive b/w conductors Farads/

G - Shunt leakage conductance b/w conductors,  $\frac{A}{V}/\text{unit length}$

$\omega L$  - series reactance,  $\Omega/\text{unit length}$

$Z = R + j\omega L$  - series impedance,  $\Omega/\text{unit length}$

$\omega C$  - shunt susceptance,  $\frac{1}{A}/\text{unit length}$

**CADD®  
CENTRE**

[www.caddcentre.ws](http://www.caddcentre.ws)


$$Y = G + jWC = \text{Shunt admittance, } \text{mho/unit length}$$

$s$  = Distance to the point of observation, measured from the receiving end of the line.

$I$  - current in the line at any point.

$E$  - Voltage b/w conductors at any point.

$l$  - length of line.

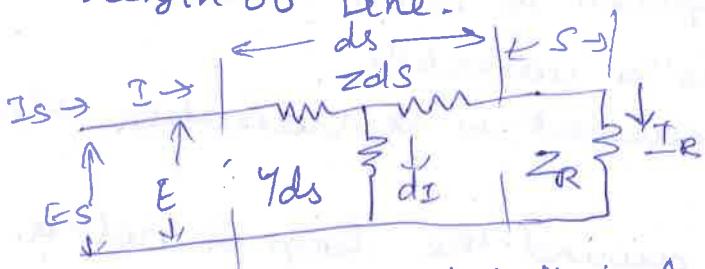

long line, with the elements of one of the infinitesimal sections.

(line made up of infinitesimal T sections)

- \* This elemental section is of length  $ds$  and carries a current  $I$ .
- \* The series line imp. being  $Z_r$ /unit length.
- \*  $Z_{ds} \rightarrow$  series imp. of the element
- \* The voltage drop in the length  $ds$  is

$$dE = I \cdot Z_{ds}$$

$$\frac{dE}{ds} = IZ \quad \text{--- (1)}$$

\*  $Y$  - shunt admittance mho/unit length

$Y_{ds}$  - admittance of the element of line

meant  
Date:

$dI$  flows across the line or from one conductor to the other.

$$ds = EY ds$$

$$\frac{dI}{ds} = EY \quad \text{--- (2)}$$

Eqs (1) & (2) differentiated w.r.t s

$$\frac{d^2E}{ds^2} = Z \frac{dI}{ds} = ZYE \quad \text{--- (3)}$$

$$\frac{d^2I}{ds^2} = Y \frac{dE}{ds} = ZYI \quad \text{--- (4)}$$

(3) + (4) → differential eqns of the transmission line.

$E$  &  $I$  should be represented in the form of wave eqns.

$$\therefore E = E_0 e^{j\omega t} \quad + \quad I = I_0 e^{j\omega t}$$

Say  $\frac{d^2}{ds^2} = m^2$  → the operator,

$$(3) \text{ becomes } m^2 E - ZYE = 0 ; [m^2(ZY)] E = 0$$

$$m = \pm \sqrt{ZY} \quad \text{--- (5)}$$

This result indicates 2 solutions, i.e. + sign & - sign

The solutions of the differential eqns are,

$$E = A e^{\sqrt{ZY} s} + B e^{-\sqrt{ZY} s} \quad \text{--- (6)}$$

$$I = C e^{\sqrt{ZY} s} + D e^{-\sqrt{ZY} s} \quad \text{--- (7)}$$

where  $A, B, C \& D \Rightarrow$  arbitrary constants of integration.

\* Since distance is measured from the receiving end of the line, To assign the conditions,

$$s=0, I=I_R, E=E_R.$$

$$\therefore (6) + (7) \text{ becomes, } E_R = A+B, I_R = C+D \quad \text{--- (8)}$$

\* A second set of boundary conditions is not available.

\* But the same set may be used once again if a new set of eqns are formed by differentiation of (6) + (7)

$$(6) \rightarrow \frac{dE}{ds} = A \sqrt{ZY} e^{\sqrt{ZY} s} - B \sqrt{ZY} e^{-\sqrt{ZY} s} = IZ \quad (\text{from (1)})$$

$$(7) \rightarrow \therefore I = A \int_Z^Y e^{\sqrt{ZY} s} - B \int_Z^Y e^{-\sqrt{ZY} s} \quad \text{--- (9)}$$

$$\frac{dI}{ds} = C \sqrt{ZY} e^{\sqrt{ZY} s} - D \sqrt{ZY} e^{-\sqrt{ZY} s} = EY \quad (\text{from (2)})$$

$$E = C \sqrt{\frac{Z}{Y}} e^{\sqrt{ZY} s} - D \sqrt{\frac{Z}{Y}} e^{-\sqrt{ZY} s} \quad \text{--- (10)}$$

s are,

At  $\theta = 0$ , equ's (9) & (10) becomes,

Date:

$$IR = A \sqrt{\frac{Y}{Z}} - B \sqrt{\frac{Y}{Z}} \quad \text{--- (11)}$$

$$ER = C \sqrt{\frac{Z}{Y}} - D \sqrt{\frac{Z}{Y}} \quad \text{--- (12)}$$

$ER = IR Z_R + \sqrt{\frac{Z}{Y}}$  has been identified as  $Z_0$  of the line

The solutions for the constants of the above eqn  
as, ~~A  $\neq$  ER~~

Let  $x = \sqrt{\frac{Z}{Y}}$  and  $\frac{1}{x} = \sqrt{\frac{Y}{Z}}$

from (11) & (12)  $IR = \frac{A}{x} - \frac{B}{x} = \frac{1}{x}(A - B) \quad \text{--- (13)}$

$$ER = CX - DX.$$

$$A + B = CX - DX \quad \text{--- (14)}$$

$$C + D = \frac{1}{x}(A - B) \quad (\text{from (8)})$$

$$x(C + D) = A - B \quad \text{--- (15)}$$

(from (1))

(from (9))

(from (2))

(from (10))

Add (13) & (15) we have,

$$A - B = CX + DX$$

$$A + B = CX - DX$$

$$\underline{2A = 2CX}$$

$$\boxed{A = CX} \rightarrow \text{--- (15)}$$

Sub (13) & (14) we have,

$$A - B = CX + DX$$

$$A + B = CX - DX$$

$$\underline{-2B = 2DX}$$

$$\boxed{B = -DX}$$

From ⑬  $XIR = A - B = CX + DX$ .

$$ER = \frac{CX - DX}{2}$$

(add)  $ER + XIR = 2CX$  (15)

(sub)  $XIR - ER = 2DX$  (17)

$$C = \frac{ER}{2x} + \frac{IR}{2}$$

sub  $x = \sqrt{\frac{Z}{Y}} = z_0$

$$C = \frac{IR}{2} + \frac{ER}{2} \sqrt{\frac{Y}{Z}}$$

$$ER = IR Z_R$$

$$= \frac{IR}{2} + \frac{IR}{2} \frac{Z_R}{z_0} \Rightarrow \boxed{\frac{IR}{2} \left[ 1 + \frac{Z_R}{z_0} \right] = C} \quad (18)$$

(17)  $\Rightarrow$

$$XIR - ER = 2DX \quad ; \quad D = \frac{IR}{2} - \frac{ER}{2x}$$

$$D = \frac{IR}{2} - \frac{ER}{2} \sqrt{\frac{Y}{Z}} \Rightarrow \frac{IR}{2} - \frac{ER \cdot Z_R}{2 z_0} \Rightarrow \boxed{\frac{IR}{2} \left[ 1 - \frac{Z_R}{z_0} \right] = D} \quad (19)$$

(15)  $\Rightarrow A = CX = \frac{IR}{2} + \frac{ER}{2} = \frac{IR}{2} \sqrt{\frac{Y}{Z}} + \frac{ER}{2}$

$$= \frac{ER}{2} \cdot z_0 + \frac{ER}{2} \Rightarrow \boxed{ER}$$

$$\Rightarrow \frac{ER}{2} \left[ 1 + \frac{z_0}{Z_R} \right] \quad (20)$$

$$\begin{aligned}
 (15) \quad B &= -DX = \frac{ER}{2} - \frac{IRx}{2} = \frac{ER}{2} - \frac{IR}{2} \cdot \sqrt{\frac{Z}{Y}} & \text{Date: } \\
 B &= \frac{ER}{2} - \frac{ER}{2} \cdot \frac{Z_0}{Z_R} \Rightarrow \frac{ER}{2} \left[ 1 - \frac{Z_0}{Z_R} \right] \quad \rightarrow (21)
 \end{aligned}$$

$$-ER = 2DX$$

L(17)

$$-\sqrt{\frac{Z}{Y}} = Z_0$$

Z\_R

$$= C \quad \rightarrow (18)$$

$$\begin{aligned}
 \text{From (6)} \quad E &= A e^{\sqrt{ZY}s} + B e^{-\sqrt{ZY}s} \\
 &= \frac{ER}{2} \left( 1 + \frac{Z_0}{Z_R} \right) e^{\sqrt{ZY}s} + \frac{ER}{2} \left[ 1 - \frac{Z_0}{Z_R} \right] \cdot e^{-\sqrt{ZY}s} \\
 &= \frac{ER}{2} \left[ \left( 1 + \frac{Z_0}{Z_R} \right) e^{\sqrt{ZY}s} + \left( 1 - \frac{Z_0}{Z_R} \right) \cdot e^{-\sqrt{ZY}s} \right]
 \end{aligned} \quad \rightarrow (22)$$

$$\begin{aligned}
 \text{From (7)} \quad I &= C e^{\sqrt{ZY}s} + D e^{-\sqrt{ZY}s}
 \end{aligned}$$

$$\begin{aligned}
 &= \frac{IR}{2} \left[ 1 + \frac{Z_R}{Z_0} \right] e^{\sqrt{ZY}s} + \frac{IR}{2} \left[ 1 - \frac{Z_R}{Z_0} \right] \cdot e^{-\sqrt{ZY}s} \\
 &= \frac{IR}{2} \left[ \left( 1 + \frac{Z_R}{Z_0} \right) e^{\sqrt{ZY}s} + \left[ 1 - \frac{Z_R}{Z_0} \right] e^{-\sqrt{ZY}s} \right]
 \end{aligned} \quad \rightarrow (23)$$

From (22)  $E = \frac{E_R}{2} \left[ \left( \frac{Z_R + Z_0}{Z_R} \right) e^{\sqrt{ZY} s} + \left( \frac{Z_R - Z_0}{Z_R} \right) e^{-\sqrt{ZY} s} \right]$

 $= \frac{E_R (Z_R + Z_0)}{2 Z_R} \left[ e^{\sqrt{ZY} s} + \left( \frac{Z_R - Z_0}{Z_R} \right) e^{-\sqrt{ZY} s} \right]$ 
 $E = \frac{E_R (Z_R + Z_0)}{2 Z_R} \left[ e^{\sqrt{ZY} s} + \left( \frac{Z_R - Z_0}{Z_R + Z_0} \right) e^{-\sqrt{ZY} s} \right] \quad \rightarrow (24)$

From (23)  $I = \frac{I_R}{2} \left[ \left( \frac{Z_0 + Z_R}{Z_0} \right) e^{\sqrt{ZY} s} + \left( \frac{Z_0 - Z_R}{Z_0} \right) e^{-\sqrt{ZY} s} \right]$

 $= \frac{I_R (Z_R + Z_0)}{2 Z_0} \left[ e^{-\sqrt{ZY} s} + \left( \frac{Z_0 - Z_R}{Z_R + Z_0} \right) e^{-\sqrt{ZY} s} \right] \quad \rightarrow (25)$

The equations (24) & (25) provide voltage and current at any point on a transmission line  
 Equs (22) & (23) Also be arranged as,  $\frac{I_R}{E_R} = \frac{Z_R}{Z_R + Z_0}$

$E = \frac{E_R}{2} e^{\sqrt{ZY} s} + \frac{I_R Z_0}{2} e^{\sqrt{ZY} s} + \frac{E_R}{2} e^{-\sqrt{ZY} s} - \frac{I_R Z_0}{2} e^{-\sqrt{ZY} s}$ 
 $= E_R \left[ \frac{e^{\sqrt{ZY} s} + e^{-\sqrt{ZY} s}}{2} \right] + I_R Z_0 \left[ \frac{e^{\sqrt{ZY} s} - e^{-\sqrt{ZY} s}}{2} \right]$

$$e^{-\sqrt{Z_0} s}$$

$$\sqrt{Z_0} s$$

$$\sqrt{Z_0} s$$

— (24)

$$\sqrt{Z_0} s$$

— (25)

voltage and  
current line

$$I_R = \frac{E_R}{Z_0}$$

$$\frac{I_R Z_0 e^{-\sqrt{Z_0} s}}{2}$$

$$E = E_R \cosh \sqrt{Z_0} s + I_R Z_0 \sinh \sqrt{Z_0} s \quad — (26)$$

Date:

$$\text{By (23)} \Rightarrow I = \frac{I_R e^{\sqrt{Z_0} s}}{2} + \frac{E_R}{2 Z_0} e^{\sqrt{Z_0} s} + \frac{I_R}{2} e^{-\sqrt{Z_0} s} - \frac{E_R}{2 Z_0} e^{-\sqrt{Z_0} s}$$
$$= I_R \left[ \frac{e^{\sqrt{Z_0} s} + e^{-\sqrt{Z_0} s}}{2} \right] + \frac{E_R}{2 Z_0} \left[ e^{\sqrt{Z_0} s} - e^{-\sqrt{Z_0} s} \right]$$

$$I = I_R \cosh \sqrt{Z_0} s + \frac{E_R}{Z_0} \sinh \sqrt{Z_0} s \quad — (27)$$

Equations (26) & (27) also useful form for the voltage and current values at any point on a transmission line.

**CADD  
CENTRE**

[www.caddcentre.ws](http://www.caddcentre.ws)

Physical significance of the equations: The infinite line

Eqn (27) may be written for the sending end current  $I_s$  of a line of length  $l$  as -

$$I_s = I_R \left[ \cosh \sqrt{Z_y} l + \frac{Z_R}{Z_0} \sinh \sqrt{Z_y} l \right] \quad Z_R = I_R Z_0$$

If the line is terminated in  $Z_R = Z_0$ , then

$$I_s = I_R \left[ \cosh \sqrt{Z_y} l + \sinh \sqrt{Z_y} l \right]$$

$$\frac{I_s}{I_R} = e^{\sqrt{Z_y} l} = e^{\alpha l} \quad \text{--- (28)}$$

where,  $\sqrt{Z_y} = \alpha$  = propagation constant of per unit length of line.  $\alpha = \alpha + j\beta$ .

P 147  
 $\alpha$  - amp. atts. constant  
 $\beta$  - ~~propagation~~ phase const.

Division of eqns (26) by (27) leads to an expression for the ip impedance of line of length  $l$ ,

$$Z_0 = \frac{E_s}{I_s} = Z_0 \left[ \frac{Z_R \cosh \alpha l + Z_0 \sinh \alpha l}{Z_0 \cosh \alpha l + Z_R \sinh \alpha l} \right] \quad \text{--- (29)}$$

The

In different form, this result may be obtained by division of (24) by (25) +  $\frac{E_R}{I_R} = Z_R$

Date:

sending

as,

J.

then

as load  
- such

at, per

expression  
l,

$\sinh \delta l$

$\rightarrow (29)$

$$Z_S = \frac{E_S}{I_S} = Z_0 \left[ \frac{e^{\delta l} + \left( \frac{Z_R - Z_0}{Z_R + Z_0} \right) e^{-\delta l}}{e^{\delta l} - \left( \frac{Z_R - Z_0}{Z_R + Z_0} \right) e^{-\delta l}} \right] \quad (30)$$

$$\rightarrow \frac{E}{I} = \frac{E_R (Z_R + Z_0)}{I_R (Z_R + Z_0)} \left( \frac{e^{\sqrt{Z_R} \cdot S} + \left( \frac{Z_R - Z_0}{Z_R + Z_0} \right) e^{-\sqrt{Z_R} \cdot S}}{e^{\sqrt{Z_R} \cdot S} - \left( \frac{Z_R - Z_0}{Z_R + Z_0} \right) e^{-\sqrt{Z_R} \cdot S}} \right)$$


$$= \frac{\frac{E_R}{I_R} Z_0}{Z_R + Z_0} \left( \frac{e^{\sqrt{Z_R} \cdot S} + \left( \frac{Z_R - Z_0}{Z_R + Z_0} \right) e^{-\delta l}}{e^{\sqrt{Z_R} \cdot S} + \left( \frac{Z_R - Z_0}{Z_R + Z_0} \right) e^{-\delta l}} \right)$$

To find the value of sending end  $\eta$ /P imp.  
 expression  
 $Z_S$ , when the line is terminated in its  
 characteristics impedance  $\xrightarrow{l} Z_R = Z_0$ , equ (3)  
 becomes,  $Z_S = Z_0$ .

A line of infinite length, terminated  
 in a load equivalent to its characteristics imp.  
 appears to the sending end just as an infinite  
 line.
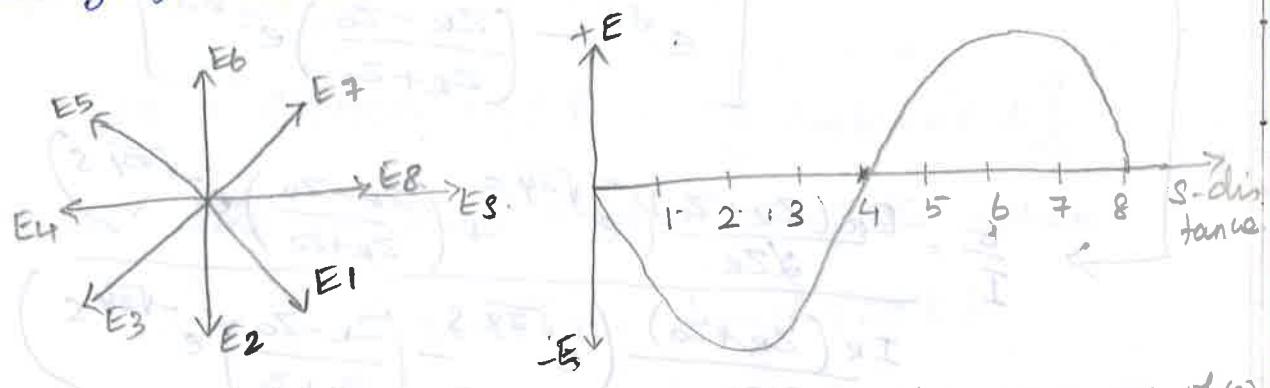
## Wavelength & Velocity of propagation

wavelength: The distance, the wave travels along the line, while the phase angle is changing through  $2\pi$  radians, is called wavelength.



8 wr points along a line  
at a particular time instant  
(a)

plot of the phasors of (a)  
showing voltage on the line  
as a function of distance.

wavelength is represented by  $\lambda$ .

$\therefore$  distance  $s = \lambda$

$$\beta d = 2\pi \quad ; \quad \boxed{\lambda = \frac{2\pi}{\beta}} \quad \text{--- ①}$$

Since, the change of  $2\pi$  in phase angle represents one cycle in time and occurs in a distance of one wavelength, then,  $\lambda = vt$

$$\boxed{\lambda = \frac{vt}{f}} \quad \text{--- ②}$$

The velocity can be expressed in terms of  
line constants.

Date:

$$v = \lambda f = \frac{2\pi f}{\beta} \quad \therefore v = \frac{\omega}{\beta} \quad \text{--- (3)}$$

This is velocity of propagation along the line.

$$Z = R + j\omega L \quad Y = G + j\omega C$$

$$\alpha^2 = \alpha + j\beta = \sqrt{ZY} = \sqrt{RG - \omega^2 LC + j\omega(LG + CR)} \quad \text{--- (4)}$$

Squaring on both sides,

$$\alpha^2 + j^2 \alpha \beta - \beta^2 = RG - \omega^2 LC + j\omega(LG + CR)$$

equating the real and Imaginary parts,

$$\alpha^2 = \beta^2 + RG - \omega^2 LC \quad \text{--- (5)}$$

$$2\alpha\beta = \omega(LG + CR)$$

$$\text{Squaring, } 4\alpha^2\beta^2 = \omega^2(LG + CR)^2 \quad \text{--- (6)}$$

Sub. (5) into (6), we have,

$$4(\beta^2 + RG - \omega^2 LC)\beta^2 = \omega^2(LG + CR)^2$$

$$\beta^4 + \beta^2(RG - \omega^2 LC) - \frac{\omega^2}{4}(LG + CR)^2 = 0$$

A solution for  $\beta$ , neglecting the -ve values,

$$\beta^2 = \frac{(RG - \omega^2 LC) \pm \sqrt{(RG - \omega^2 LC)^2 + 4\omega^2(LG + CR)^2}}{2}$$

$$\beta = \sqrt{\frac{w^2 LC - RA + \sqrt{(RA - w^2 LC)^2 + w^2 (LG + CR)^2}}{2}} \quad \text{--- (7)}$$

Using From equ (5)

$$\alpha = \sqrt{\frac{RA - w^2 LC + \sqrt{(RA - w^2 LC)^2 + w^2 (LG + CR)^2}}{2}} \quad \text{--- (8)}$$

In a perfect line  $R=0$ ;  $C=0$  then (7) becomes

$$\beta = w \sqrt{LC} \quad \text{--- (9)}$$

$$\sqrt{\frac{w^2 LC + (w^2 LC)^2}{2}} = \sqrt{2w^2 LC}$$

The velocity of propagation for such an ideal line is,  $v = \frac{w}{\beta} = \frac{1}{\sqrt{LC}}$  m/sec. --- (10)

which shows the line parameter values

fix the velocity of propagation

$$L = \frac{\lambda}{I} = \left( 2 \frac{\mu}{8\pi} + \frac{\mu_v}{2\pi} \ln \frac{d}{a} \right)$$

$$C = \frac{\pi \epsilon}{\ln \frac{d}{a}} \quad \text{farads/m}$$

$$LC = \frac{\pi \epsilon}{\ln \left( \frac{d}{a} \right)} \left[ \left( \frac{\mu}{4\pi} + \frac{\mu_v}{2\pi} \ln \left( \frac{d}{a} \right) \right) \right]$$

for a line of non-magnetic material with air spacing,  $LC = \frac{\mu_0 \epsilon_0}{4 \ln(\frac{d}{a})} + \mu_0 \epsilon_0$  — (11)

$$\therefore v = \frac{1}{\mu_0 \epsilon_0 \left[ \frac{1}{4 \ln(\frac{d}{a})} + 1 \right]} \text{ m/sec} — (12)$$

(7) becomes,

$$\sqrt{\omega^2 LC}$$

an ideal

(10) values

$\mu_0$  = Magnetic permeability of space

$$= 4\pi \times 10^{-7} \text{ in KMS unit.}$$

a - radius of the conductor

d - distance b/w conductors of a II wire line

$\frac{1}{4 \ln \frac{d}{a}}$  → Internal inductance of the conductors

This internal inductance is fixed, as by skin effect, the velocity rises and reaches the limiting condition of,

$$v = \frac{1}{\sqrt{\mu_0 \epsilon_0}} \text{ m/sec}$$

which in space becomes,  $3 \times 10^8 \text{ m/sec} = c$

which is identified as velocity of light in space.

waveform distortion

## The distortionless Line

If a line is to have neither frequency nor delay distortion, then  $\alpha$  and the velocity of propagation can't be fn. of frequency.

$$v = \frac{\omega}{\beta} \quad \beta \rightarrow \text{Direct fn. of freq.}$$

$$\beta = \sqrt{\frac{\omega^2 LC - R_h + \sqrt{(R_h - \omega^2 LC)^2 + \omega^2 (L_h + C_r)^2}}{2}}$$

Shows that if the term under the second radical be reduced to equal  $(R_h + \omega^2 LC)^2$  — ?

Then the required condition on  $\beta$  is obtained.

\* Expanding the terms under the internal radical,  $(R_h - \omega^2 LC)^2 + \omega^2 (L_h + C_r)^2 = (R_h + \omega^2 LC)^2$

$$\begin{aligned} & R_h^2 - 2\omega^2 R_h L C + \omega^4 L^2 C^2 + \omega^2 L^2 C^2 + \omega^2 C^2 R^2 + \\ & 2\omega^2 L_h C_r = (R_h + \omega^2 LC)^2 \\ & = R_h^2 + 2\omega^2 L C R_h + \omega^4 L^2 C^2 \end{aligned}$$

$$\omega^2 L^2 C^2 + \omega^2 C^2 R^2 - 2\omega^2 L C R_h = 0$$

$$\omega (L_h - C_r)^2 = 0$$

This condn. will make  $\beta$ , a direct fn. of frequency.  $L_h = C_r$  A hypothetical line might be built to fulfill this condn.

no delay  
attn

$$v = \frac{\omega}{\beta} = \frac{1}{VLC} ; \quad \boxed{\beta = \omega \sqrt{LC}}$$
$$v = \frac{1}{VLC}$$

Date:

which is same for all frequencies, thus eliminating delay dispersion.

$$\text{Hence } \alpha = \frac{R_a - \omega^2 LC + \sqrt{(R_a - \omega^2 LC)^2 + \omega^2 (L_a + CR)^2}}{2}$$

The internal radial is forced to lead to,  
 $(R_a + \omega^2 LC)^2$

w.k.t  $L_a = CR$

$$\cancel{R^2 a^2 - 2\omega^2 L_a C R_a + \omega^4 C^2 + \omega^2 L^2 a^2 + \omega^2 C^2 R^2 + 2\omega^2 C R_a}$$
$$= \cancel{R^2 a^2} + 2\omega^2 L_a C R_a + \omega^4 C^2$$

$$\omega^2 (L_a - CR)^2 = 0 ; (L_a - CR)^2 = 0.$$

It is possible to make  $\alpha$

$\alpha = \sqrt{R_a}$  and the velocity independent of freq simultaneously.

$L_a = CR$   $\rightarrow$  which is independent of freq

$\frac{L}{C} = \frac{R}{a}$  requires large value of  $L$  since  $a$  is small.

$a$  is fixed  $\alpha$  & attn. is fixed  $\rightarrow$  resulting poor line efficiency.  
To  $\downarrow$   $R$  raises the size & cost of conductors above economic limits, so the hypothetical results can't be achieved.

## The Telephone Cable

Consider ordinary TP cable. wires are insulated with paper & twisted in pairs.

→ :- negligible values of inductance & conductance.  $\therefore L = G = 0$ .

$$\therefore Z = R \quad \text{and} \quad Y = j\omega C \quad \text{--- (2)}$$

$$Zl = \alpha + j\beta = \sqrt{ZY} = \sqrt{RC - \omega^2 LC + j\omega(LG + CR)}$$

$$\text{when } L = G = 0 \quad Zl = \sqrt{j\omega CR} = \sqrt{\frac{j2\omega CR}{2}} \quad \text{--- (3)}$$

$$Zl = \alpha + j\beta = (1+j1) \sqrt{\frac{WCR}{2r}} \quad (1+j1)^2 = 1+j^2+2j = 2j$$

$$\alpha = \sqrt{\frac{WCR}{2r}} \quad \beta = \sqrt{\frac{WCR}{2r}}$$

The velocity of propagation is

$$v = \frac{w}{\beta} = \sqrt{\frac{w}{WCR}} = \sqrt{\frac{2w}{CR}}$$

It is observed that both  $\alpha$  & velocity are fns. of freq.,  $\therefore$  the higher freqs are attenuated more & travel faster than lower freqs.  $\therefore$  considerable fading & delay distortion is the result on TP cable.

## Inductance Loading of TP cables

It is necessary to  
use the L ratio to  
achieve distortionless  
condn.

\* consider a uniformly loaded cable circuit

\* Assume  $C_1 = 0$

L has been  $\uparrow$ ed, so that  $WL$  is large w.r.t R.

$$\text{Then, } Z = R + j\omega L$$

$$Y = j\omega C$$

$$\tan^{-1} \frac{1}{x} = \frac{\pi}{2} - \tan^{-1} x$$

$$Z = \sqrt{R^2 + \omega^2 L^2} \quad \boxed{\frac{\pi/2 - \tan^{-1} \frac{R}{\omega L}}{}} \quad \text{--- (1)}$$

$$Z = \sqrt{R^2 + \omega^2 L^2} \quad \boxed{\frac{\pi/2 - \tan^{-1} \frac{R}{\omega L}}{\times \omega C \sqrt{W^2}}} \quad \text{--- (2)}$$

$$= \sqrt{R^2 W^2 C^2 + \omega^4 L^2 C^2} \quad \boxed{\frac{\pi/4 - \pi/2 \tan^{-1} \frac{R}{\omega L}}{}}$$

$$= \sqrt{W^4 L^2 C^2 \left( \frac{R^2}{\omega^2 L^2} + 1 \right)} \quad \boxed{\frac{\pi/4 - \frac{\pi}{2} \tan^{-1} \frac{R}{\omega L}}{}}$$

$$= W^2 L C \sqrt{1 + \frac{R^2}{\omega^2 L^2}} + \boxed{\frac{\pi/4 - \frac{\pi}{2} \tan^{-1} \frac{R}{\omega L}}{}}$$

$$= W^2 L C \sqrt{1 + \frac{R^2}{\omega^2 L^2}} \quad \boxed{\frac{\pi/2 - \frac{\pi}{2} \tan^{-1} \frac{R}{\omega L}}{}}$$

If R is small w.r.t WL, the term  $\frac{R^2}{\omega^2 L^2}$  may be dropped & it becomes

$$\omega = \sqrt{LC} \left[ \frac{\pi}{2} - \frac{1}{2} \tan^{-1} \frac{R}{\omega L} \right] \quad \text{--- (3)}$$

$$\text{if } \theta = \frac{\pi}{2} - \frac{1}{2} \tan^{-1} \frac{R}{\omega L},$$

$$\cos \theta = \cos \left( \frac{\pi}{2} - \frac{1}{2} \tan^{-1} \frac{R}{\omega L} \right) = \sin \left( \frac{1}{2} \tan^{-1} \frac{R}{\omega L} \right)$$

for a small angle,

$$\sin \theta = \frac{\tan \theta}{\sqrt{1 + \tan^2 \theta}} \approx \tan \theta \quad \text{so that } \cos \theta \approx \frac{1}{\sqrt{1 + \tan^2 \theta}} \approx \frac{1}{\sqrt{1 + \sin^2 \theta}} \approx \frac{1}{\sqrt{1 + \sin^2(\frac{\pi}{2} - \frac{1}{2} \tan^{-1} \frac{R}{\omega L})}} \approx \frac{1}{\sqrt{1 + \sin^2(\frac{\pi}{2})}} = 1$$

$$\text{likewise, } \sin \theta = \sin \left( \frac{\pi}{2} - \frac{1}{2} \tan^{-1} \frac{R}{\omega L} \right) = 1 \quad \text{--- (4)}$$

$\therefore$  rewrite eqn (3)

$$\omega = \sqrt{LC} (\cos \theta + j \sin \theta) = \sqrt{LC} \left( \frac{R}{2\omega L} + j \frac{\sqrt{LC}}{2\omega L} \right)$$

$$\Rightarrow \frac{RW\sqrt{LC}}{2\omega L} + j\omega\sqrt{LC}$$

$\therefore$  for the uniformly loaded cable,  $\omega = \frac{R}{2\sqrt{CL}} + j\omega\sqrt{LC}$ .

$$\alpha = \frac{R}{2\sqrt{CL}}$$

$$= \alpha + j\beta$$

$$\beta = \omega\sqrt{LC}$$

$$\nu = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

\* Under the assumption of  $\alpha = 0$ , &  $\omega L$  large

w.r.t  $R$ ,   
 (i) the atten  $\alpha$  & velocity  $v$  are independent  
 of freq (no  $\omega$  term) & loaded cable will be distortionless.

$\text{Date: } \dots$   
 $d = \frac{R}{2} \sqrt{c_L}$  shows that the attn. may  
 be fixed by ring  $L$ , provided that  $R$  is  
 not also increased too greatly.  
 $\tan^{-1} \frac{R}{\omega L}$ )

$$= \frac{R}{2\omega L} - \textcircled{4}$$

$$= 1 - \textcircled{5}$$

$$= 8 \sin(\theta_2)$$

$$\frac{3}{\omega L} + j$$


$$\omega \sqrt{LC}$$

$$\omega \sqrt{LC}.$$

$L$  large  
 dependent  
 will be

\* Continuous or uniform loading is expensive and achieves only a small  $\text{Im } L$  per unit length.

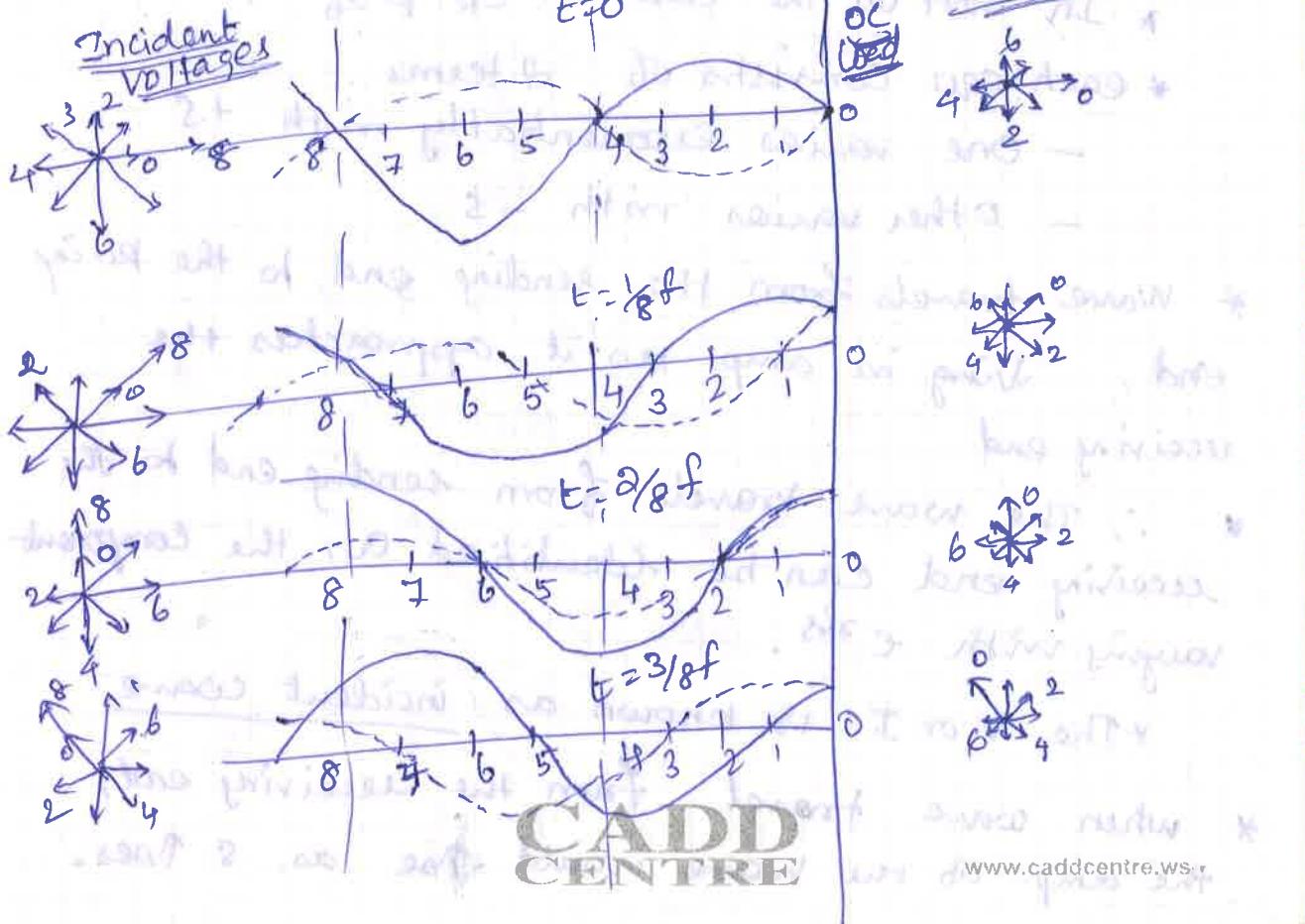\* Lumped loading is preferred as a means of trion treatment for cables.



## Reflection on a line, not terminated in $Z_0$

- \* The voltage and currents on the line, with  $s$  measured as positive from the receiving end,

eqns (24) & (25)

$$E = \frac{E_R (Z_R + Z_0)}{2Z_R} \left[ e^{s \cdot s} + \left( \frac{Z_R - Z_0}{Z_R + Z_0} \right) e^{-s \cdot s} \right]$$

$$I = \frac{I_R (Z_R - Z_0)}{2Z_0} \left[ e^{s \cdot s} - \left( \frac{Z_R - Z_0}{Z_R + Z_0} \right) e^{-s \cdot s} \right] \quad \begin{array}{l} (1) \\ (2) \end{array}$$

- \* In most ob. the cases,  $Z_R \neq Z_0$ .

- \* each equ consists of 2 terms.

- One varies exponentially with  $+s$

- Other varies with  $-s$ .

- \* Wave travels from the sending end to the Re-cip end, rising in amp as it approaches the receiving end

- \* : The wave travels from sending end to the receiving end can be identified as the component varying with  $e^{s \cdot s}$ .

\* The V or I is known as incident wave

- \* when wave travel from the receiving end, the amp. of the wave would ~~use~~ as  $s$  times.

The voltage or current is known as


Date:

reflected wave. & is represented by  $e^{-\gamma L}$ .

For Reflected voltage, the initial value equal to the incident voltage at the load (for OC)

\* The total instantaneous voltage at any pt. on the line is the vector sum of the voltage of the incident and reflected waves.

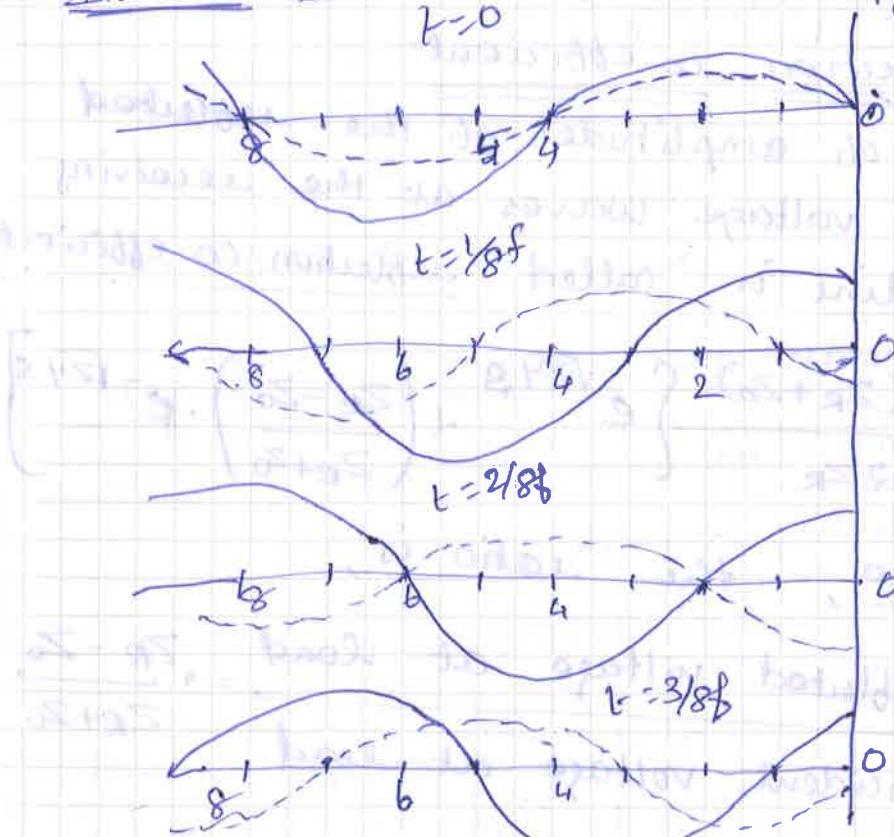Incident and reflected current waves open circuit



**CADD®  
CENTRE**

[www.caddcentre.ws](http://www.caddcentre.ws)

\* The only diff. b/w the curves for voltage and current ( $Z_R$  is infinite or  $\infty$ ) is in the reversed phase of the reflected current wave.

\* From the fig., It is seen that, the 2 ct. waves are equal and opp. phase at the OC'd receiving end.

\* The total instantaneous ct. at that point always being zero as required by the open ext.

### Reflection co-efficient

The ratio of amplitudes of the reflected and incident voltage waves at the receiving end of the line is called reflection co-efficient

$$E = \frac{E_R (Z_R + Z_0)}{2Z_R} \left\{ e^{\sqrt{2}Y_s} + \left( \frac{Z_R - Z_0}{Z_R + Z_0} \right) \cdot e^{-\sqrt{2}Y_s} \right\}$$

Sub-  $s = 0$ , the ratio is,

$$K = \frac{\text{reflected voltage at load}}{\text{incident voltage at load}} = \frac{Z_R - Z_0}{Z_R + Z_0}$$

The polarity of the reflected wave is dependent on the angles & magnitudes of  $Z_R + Z_0$ .

age and reversed  
the 2 ct.  
e OC'd

∴ For termination of  $Z_0$  (charac. imp.) the deflection co-efficient is zero.

from eqns (1) & (2)

$$E = \frac{ER(Z_R + Z_0)}{2Z_R} \left( e^{\sqrt{Z_0} \cdot s} + \frac{Z_R - Z_0}{Z_R + Z_0} e^{-\sqrt{Z_0} \cdot s} \right)$$

$$= \frac{ER(Z_R + Z_0)}{2Z_R} \left( e^{sL} + k e^{-sL} \right) \quad \text{--- (1)}$$

$$I = \frac{IR(Z_R + Z_0)}{2Z_0} \left\{ e^{\sqrt{Z_0} \cdot s} - \left( \frac{Z_R - Z_0}{Z_R + Z_0} \right) e^{-\sqrt{Z_0} \cdot s} \right\}$$

$$= IR \cdot \frac{Z_R + Z_0}{2Z_0} \left( e^{sL} - k e^{-sL} \right). \quad \text{--- (2)}$$

### Input and Transfer impedances

The 4pp imp of a transmission line is,

$$Z_s = Z_0 \left[ \frac{Z_R \cosh sL + Z_0 \sinh sL}{Z_0 \cosh sL + Z_R \sinh sL} \right] \quad \text{--- (1)}$$

$$= Z_0 \left[ \frac{e^{sL} + k e^{-sL}}{e^{sL} - k e^{-sL}} \right] \quad \text{--- (2)}$$

If the voltage at the sending-end is known, it is convenient to have the ffr impedance.

The sending end voltage is,  $E_s$

$$E_R = I_R Z_R$$

$$E_s = \frac{E_R (Z_R + Z_0)}{2Z_R} (e^{+sl} + k e^{-sl})$$

$$= \frac{I_R (Z_R + Z_0)}{2} (e^{sl} + k e^{-sl}) \quad \textcircled{3}$$

for which the transfer impedance is,

$$Z_T = \frac{E_s}{I_R} = \frac{(Z_R + Z_0)}{2} (e^{+sl} + k e^{-sl})$$

For substituting the value of  $k$ ,  $\textcircled{4}$  becomes,

$$\begin{aligned} Z_T &= \left( \frac{Z_R + Z_0}{2} \right) \left( e^{sl} + \left( \frac{Z_R - Z_0}{Z_R + Z_0} \right) e^{-sl} \right) \\ &= \left( \frac{Z_R + Z_0}{2} \right) \left( \frac{(Z_R + Z_0) e^{sl} + (Z_R - Z_0) e^{-sl}}{Z_R + Z_0} \right) \\ &= \frac{1}{2} [Z_R e^{sl} + Z_0 e^{-sl} + Z_R e^{-sl} - Z_0 e^{-sl}] \\ &= I_R \left[ \frac{e^{sl} + e^{-sl}}{2} \right] + Z_0 \left[ \frac{e^{sl} - e^{-sl}}{2} \right] \end{aligned}$$

$$Z_T = Z_R \cos h s l + Z_0 \sinh s l \quad \textcircled{5}$$

if the expression is derived in terms of the hyperbolic functions.

$$E_p = jk_z Z_R$$

## Open and short circuited lines Date:

A line is terminated with  $Z_R = \infty$  open circuit  
 $Z_R = 0$  short circuit.

→ ③

The IIP imp. of a line of length  $l$  is,

$$Z_S = Z_0 \left[ \frac{Z_R \cosh jkl + Z_0 \sinh jkl}{Z_0 \cosh jkl + Z_R \sinh jkl} \right] \quad \text{--- ①}$$

For the short circuit case  $Z_R = 0$ . so that,

$$Z_S = Z_0 \frac{Z_0 \sinh jkl}{Z_0 \cosh jkl} = \boxed{Z_{SC} = Z_0 \tanh jkl} \quad \text{--- ②}$$

Eqn ① may be rewritten as,

$$Z_S = Z_0 \left[ \frac{\cosh jkl + (Z_0/Z_R) \sinh jkl}{(Z_0/Z_R) \cosh jkl + \sinh jkl} \right]$$

The IIP imp. of the open circuited line of length  $l$ , with  $Z_R = \infty$  is,

$$Z_{OC} = Z_0 \coth jkl \quad \text{--- ③}$$

$$Z_0 = \coth jkl \quad \text{--- ③}$$

Multiplying eqns ② & ③ we have

**CADD**  
CENTRE®

[www.caddcentre.ws](http://www.caddcentre.ws)

$\frac{Z_0}{Z_{sc} \cdot Z_{oc}}$  → Experimentally determining the

value of  $Z_0$  of a line.


② →

$$\tanh \delta l = \frac{Z_{sc}}{Z_0} = \sqrt{\frac{Z_{sc} - Z_{oc}}{Z_{sc} + Z_{oc}}} = \sqrt{\frac{Z_{sc}}{Z_{oc}}}$$

$$2l = \tanh^{-1} \sqrt{\frac{Z_{sc}}{Z_{oc}}}$$

Reflection factor and reflection loss

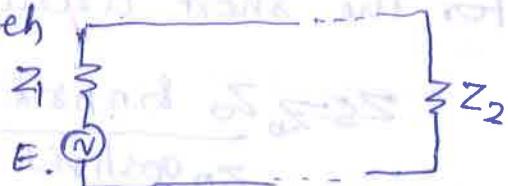\* Assume  $Z_1 \neq Z_2$ . Imp. mismatch will be the result.



\* It causes,

\* a change in the ratio of V to I and

\* Energy tried by the electric field is that tried by magnetic field.

\* Portion of the energy is reflected by the load.

\* The energy delivered to the load, may be less than would be delivered from source.

(Comparatively if the imp's matched.)

It is said to be reflection loss.

\* Impedance matching b/w a given gen & load might be obtained by insertion of an ideal transformer or a lossless phase shifter b/w source and load.

From the theory of ideal Transformer,

$$\frac{I_1}{I_2} = \sqrt{\frac{Z_2}{Z_1}} \quad \text{--- (1)}$$

For Imp. matching, \*  $Z_2$  may be adjusted to  $Z_1$  by choosing proper trfr. ratio.

\* The phase angle of  $Z_2$  may be adjusted to  $Z_1$  by operation of the phase shifter.

Under these conditions  $Z_2$  is imp. matched to  $Z_1$ .

Now the c.t. flow through the genr would be,

$$I_1 = \frac{E}{2Z_1} \quad \text{--- (2)}$$

Say  $I_2'$  - current flow thro' the load or secondary of the trfr.

Under imp. matching condn, eqn (1) & (2) may

be written as

$$I_2' = I_1 \sqrt{\frac{Z_1}{Z_2}}$$

$$I_2' = \frac{E}{2Z_1} \cdot \sqrt{\frac{Z_1}{Z_2}} = \frac{E}{2\sqrt{Z_1 Z_2}} \quad \text{--- (3)}$$

Without imp. matching the ct.  $I_2$  is given by,

$$|I_2| = \frac{|E|}{|Z_1 + Z_2|} \quad \text{--- (4)}$$

∴ The ratio of the ct. actually flowing in the load which might flow under imp. matched condition is,

$$\left| \frac{I_2}{I_2'} \right| = \frac{\frac{|E|}{|Z_1 + Z_2|}}{\left| \frac{|E|}{2\sqrt{Z_1 Z_2}} \right|} = \frac{2\sqrt{Z_1 Z_2}}{|Z_1 + Z_2|} \quad \text{--- (5)}$$

This ratio indicates the change in current in the load due to reflection at the mismatched

In (4) is called reflection factor k

$$k = \frac{2\sqrt{Z_1 Z_2}}{|Z_1 + Z_2|}$$

$$\frac{V_1}{V_2} = \frac{I_1}{I_2} = e^N$$

The Reflection loss is defined as the no. of repees or decibels by which the ct. in the load matched conditions would exceed the current actually flowing in the load.

$$N \text{ repees} = \ln \left| \frac{V_1}{V_2} \right| = \ln \frac{I_1}{I_2}$$

$$dB = 10 \log \frac{P_1}{P_2}$$

given by,

the load  
connected  
coming to the  
ended

$$\frac{z_1 z_2}{z_1 + z_2} \quad (5)$$

ment is  
matched

$$\frac{I_1}{I_2} = e^N$$
$$= \ln(V_1) - \ln \frac{I_1}{I_2}$$

$$0 \log \frac{P_1}{P_2}$$

ally

Reflection loss nepes =  $\ln \left| \frac{z_1 + z_2}{2\sqrt{z_1 z_2}} \right| \quad (6)$

reflection loss, dB =  $20 \log \left| \frac{z_1 + z_2}{2\sqrt{z_1 z_2}} \right| \quad (7)$

### Insertion Loss

At terminal 11',  
 $z_g \neq z_s$



The IL of a line or N/W is defined as the no. of nepes or decibels, by the ch. in the load is changed by the insertion.

The sending end ch. can be written as,

$$I_S = I_R \frac{(Z_R + Z_0)}{2Z_0} (e^{j\delta l} - k e^{-j\delta l}) \quad (1)$$

$$I_S = \frac{E}{Z_g + Z_s} \quad (2)$$

$$k = \frac{Z_R - Z_0}{Z_R + Z_0}$$

The up imp  $Z_s$  can be written as,

$$Z_s = Z_0 \left( \frac{e^{j\delta l} + k e^{-j\delta l}}{e^{j\delta l} - k e^{-j\delta l}} \right)$$

(3)

sub. (3) into (2)

$$\therefore I_S = \frac{E}{Z_g + Z_0 \left( \frac{e^{j\delta l} + k e^{-j\delta l}}{e^{j\delta l} - k e^{-j\delta l}} \right)}$$

$$I_s = \frac{E(e^{+rl} - ke^{-rl})}{Z_g(e^{+rl} - ke^{-rl}) + Z_0(e^{+rl} + ke^{-rl})} \quad (4)$$

Sub (4) into (1), we have

$$\frac{E(e^{+rl} - ke^{-rl})}{Z_g(e^{+rl} - ke^{-rl}) + Z_0(e^{+rl} + ke^{-rl})} = \frac{I_R(Z_R + Z_0)}{2Z_0} (e^{+rl} - ke^{-rl})$$

$$I_R = \frac{2Z_0 E}{(Z_R + Z_0)[Z_g(e^{+rl} - ke^{-rl}) + Z_0(e^{+rl} + ke^{-rl})]}$$

$$= \frac{2Z_0 E}{(Z_R + Z_0)[Z_g e^{+rl} - Z_g k e^{-rl} + Z_0 e^{+rl} + Z_0 k e^{-rl}]}$$

$$= \frac{2Z_0 E}{(Z_R + Z_0)[(Z_g + Z_0)e^{+rl} + k e^{-rl}[Z_0 - Z_g]]}$$

$$= \frac{2Z_0 E}{(Z_R + Z_0)(Z_g + Z_0)e^{+rl} + (Z_R + Z_0) \frac{(Z_R - Z_0)}{(Z_R + Z_0)} (Z_0 - Z_g) e^{-rl}}$$

$$= \frac{2Z_0 E}{(Z_R + Z_0)(Z_g + Z_0)e^{+rl} + (Z_0 - Z_g)(Z_R - Z_0)e^{-rl}} \quad (5)$$

Eqn ⑤ is the value of current actually flowing in the load  $Z_R$ .

Without the line present, the d.c.  $I_R'$  flowing in the load would be,  $I_R' = \frac{E}{Z_g + Z_0}$  → ⑥

The ratio of  $I_R'$  &  $I_R$  i.e. the d.c. flow in the load, if gen & load were directly connected, to that flowing with the line inserted is,

$$\frac{I_R'}{I_R} = \frac{\frac{E}{Z_g + Z_0}}{2 Z_0 E}$$

$$= \frac{(Z_R + Z_0)(Z_g + Z_0) e^{j\alpha l} + (Z_0 - Z_g)(Z_R - Z_0) e^{-j\alpha l}}{2 Z_0 (Z_g + Z_R)} \quad \text{→ ⑦}$$

If  $\alpha$  is large or the line is long, the second term in the numerator may be neglected w.r.t. 1st.

$$\frac{I_R'}{I_R} = \frac{(Z_R + Z_0)(Z_g + Z_0) e^{j\alpha l}}{2 Z_0 (Z_g + Z_R)}$$

both numerator & denominator  $\times$  by  $2\sqrt{ZgZ_R}$

$$\frac{|I_R'|}{|I_R|} = \frac{2\sqrt{ZgZ_R} \cdot (Z_R + Z_0) (Z_g + Z_0) e^{j\alpha l} e^{j\beta l}}{4\sqrt{ZgZ_R Z_0^2} \cdot (Z_g + Z_R)} \quad (8)$$

The IL is to be calculated as a fn. of g. magnitudes only.  $\therefore$  Taking absolute value & rearranging, phase angle may be neglected.

$$\left| \frac{I_R'}{I_R} \right| = \frac{2\sqrt{ZgZ_R}}{|(Z_g + Z_R)|} \cdot \frac{|Z_g + Z_0|}{2\sqrt{ZgZ_0}} \cdot \frac{|Z_R + Z_0|}{2\sqrt{Z_R Z_0}} \cdot e^{j\alpha l} \quad (9)$$

1

The reflection factor may be written as,

$$K_R = \frac{2\sqrt{ZgZ_R}}{|Z_g + Z_0|} \rightarrow \text{reflection factor at terminal } 11'$$

where the gen. may be mismatched at its junction with line

when  $\alpha$  = large, or line is long, its  $Z_p$  ends in  $Z_0$ .

$$\therefore K_R = \frac{2\sqrt{Z_R Z_0}}{|Z_R + Z_0|} = K_R' \quad \text{— reflection factor at terminal } 22'$$

2<sup>nd</sup> term in  $\frac{2\sqrt{ZgZ_R}}{|Z_g + Z_R|} = K_{SR}' \quad \text{— reflection factor occurring if the gen. were directly connected to load.}$

The fourth term is,  $e^{\alpha l} \rightarrow$  loss in the line.

Date:

The current ratio is,  $\left( \frac{I_R'}{I_R} \right) = \frac{k_{SR}}{k_s k_R} e^{\alpha l}$  — (10)

The Insertion loss may be obtained by taking the log of the current ratio,

$$IL \text{ (nepers)} = \ln \frac{1}{k_s} + \ln \frac{1}{k_R} - \ln \frac{1}{k_{SR}} + \alpha l$$
 — (11)

$$IL \text{ dB} = 20 \left[ \log \frac{1}{k_s} + \log \frac{1}{k_R} - \log \frac{1}{k_{SR}} + 0.43439l \right]$$
 — (12)

$\frac{1}{k_{SR}}$   $\rightarrow RL$  when gen directly connected to the load.

Hence this is subtracted,  $\therefore$  it is not due to insertion of the line.

$$\text{Insertion loss (dB)} = 10 \log \left( \frac{P_i}{P_o} \right)$$

$$\text{Tr. loss or attn. (dB)} = 10 \log \frac{P_i - P_r}{P_o}$$

$$\text{Reflection loss (dB)} = 10 \log \frac{P_i}{P_i - P_r}$$

$$\text{Return loss (dB)} = \text{CADD CENTRE} = 10 \log \left( \frac{P_i}{P_r} \right)$$

[www.caddcentre.ws](http://www.caddcentre.ws)

① A lossless line has a charac. imp. of  $400 \Omega$ . Determine the standing wave ratio at the receiving end impedance is  $800 + j0 \Omega$

$$Z_0 = 400 \Omega \quad Z_R = 800 + j0 \Omega$$

$$\text{Reflection Co-eff } K \text{ or } R = \frac{Z_R - Z_0}{Z_R + Z_0} = \frac{800 - 400}{800 + 400}$$

$$= \frac{1}{3} = 0.33$$

$$\text{SWR } S = \frac{1+R}{1-R} = \frac{1+0.33}{1-0.33} = 2 \quad (1.985)$$

2) A tr-con line has the following unit length parameters,  $L = 0.1 \mu H$ ,  $R = 5 \Omega$ ,  $G = 0.01 \mu V$ ,  $C = 300 \text{ pF}$ . calculate the charac. imp & propagation const at 500 MHz.

$$Z = R + j\omega L = 5 + j(2\pi \times 500 \times 10^6) \times (0.1 \times 10^{-6})$$

$$= 5 + j314.159 = 314.199 \angle 89.01^\circ$$

$$Y = G + j\omega C = 0.01 + j(2\pi \times 500 \times 10^6) \times 300 \times 10^{-12}$$

$$= 0.01 + j0.9424 = 0.9425 \angle 89.39^\circ$$

$$\text{charac. imp } Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{314.199 \angle 89.01^\circ}{0.9425 \angle 89.39^\circ}}$$

$$= 18.281 \angle -0.57^\circ \Omega$$

of  $400 \Omega$ .  
Lossy end

$$\text{prop-const} \quad \gamma_l = \sqrt{Zy} = \sqrt{314 \cdot 199} \underbrace{89.01}_{\text{Date}} \times 0.9425 \underbrace{89.39^\circ}_{}$$

$$\gamma_l = 17.201 \underbrace{89.24^\circ}_{}$$

- ③ The characteristic imp. of a uniform tr-ion line  
is  $2309.6 \Omega$  at a freq of  $800 \text{ MHz}$ . At this  
freq the propagation const is  $0.054$  ( $0.0366 + j0.99$ ).

Determine R and L.

$$\gamma_l = 0.054 (0.0366 + j0.99) = 0.053 \underbrace{87.88^\circ}_{}$$

$$\omega = 2\pi f = 50.24 \times 10^6$$

- ④ Find the attenuation and phase shift const. of a  
wave propagating along the line, whose prop. const.  
is  $1.048 \times 10^{-4} \underbrace{88.8^\circ}_{}$

$$\gamma_l = 1.048 \times 10^{-4} \underbrace{88.8^\circ}_{\text{Date}} = 2.19 \times 10^{-6} + j1.048 \times 10^{-4}$$

$$\gamma_l = \alpha + j\beta$$

CADD  
CENTRE

$$\alpha = 2.19 \times 10^{-6} \text{ Nepes/m}$$

$$\beta = 1.048 \times 10^{-4} \text{ radians/m}$$

⑤ Calculate the change. imp. of a transmission line, if the following measurements have been made on the line -  $Z_{oc} = 500 \angle -60^\circ \Omega$  &  $Z_{sc} = 500 \angle 30^\circ \Omega$

$$Z_0 = \sqrt{Z_{oc} \cdot Z_{sc}} = \sqrt{500 \angle -60^\circ \cdot 500 \angle 30^\circ}$$

$$= 526.404 \angle -30^\circ$$

⑥ A generator of  $110$  V,  $1000$  cycles supplies power to a  $100$  mile open wire line terminated in  $Z_0$  and having the following parameters.

$$R = 10.4 \Omega/\text{mile}, L = 0.00367 H/\text{mile},$$

$$G = 0.8 \times 10^{-8} \Omega^{-1}/\text{mile}, C = 0.00835 \mu\text{F}/\text{mile}.$$

Find out the received power and voltage.

The line constants are,

$$z = R + j\omega L = 10.4 + j23.0 = 25.2 \angle 66^\circ$$

$$y = G + j\omega C = (0.8 + j52.5) \times 10^{-6}$$

$$= 52.6 \times 10^{-6} \angle 90^\circ$$

$$Z_0 = \sqrt{\frac{z}{y}} = \sqrt{\frac{25.2 \angle 66^\circ}{52.6 \times 10^{-6} \angle 90^\circ}} = 692 \angle -12^\circ \Omega$$

$$st = \sqrt{zy} = \sqrt{25.2 \angle 66^\circ \times 52.6 \times 10^{-6} \angle 90^\circ} = 0.0363 \angle 78^\circ$$

line, if  
made on

$2^\circ \text{ N}$

$$\alpha = 0.0363 \cos 78^\circ = 0.00755 \text{ neper/mile.}$$

Date:

$$\beta = 0.0363 \sin 78^\circ = 0.0355 \text{ radian per mile}$$

$$v = \frac{\omega}{\beta} = \frac{6280}{0.0355} = 177,000 \text{ miles/second.}$$

$$\lambda = \frac{2\pi}{\beta} = 177 \text{ miles}$$

The line is terminated in  $Z_0$ , then  $Z_s = Z_0$ , so that

$$I_s = \frac{E_s}{Z_0} = \frac{1}{692 \angle -12^\circ} = 0.00145 \angle 12^\circ \text{ amp.}$$

$$\frac{I_R}{I_s} = e^{-\alpha l} = e^{-\alpha l} \cdot e^{j\beta l} = e^{-0.755} \cdot e^{j3.55}$$
$$e^{-j3.55} \rightarrow -3.55 \text{ radians.}$$

$$I_R = I_s \cdot e^{-0.755} \angle -203.8^\circ$$

$$= 0.00145 \angle 12^\circ \times 0.474 \angle -203.8^\circ$$

$$= 0.000685 \angle -191.8^\circ \text{ amp [ } E_s \text{ reference] }$$

The received voltage is,  $E_R = I_R Z_0$

$$= 0.000685 \angle -191.8^\circ \times 692 \angle -12^\circ$$

$$= 0.474 \angle -203.8^\circ \text{ V [ } E_s \text{ reference] }$$

CADD  
CENTRE

[www.caddcentre.ws](http://www.caddcentre.ws)

The received power is,

$$P_R = E_R I_R \cos \theta = 318 \times 10^{-6} \text{ watts.}$$

$$\therefore \sqrt{Z_2} = \sqrt{R^2 + w^2 L^2} \quad \boxed{\pi/2 - \tan^{-1} R/wL \times wC \sqrt{\pi/2}}$$

$$= \sqrt{w^2 L^2 \left( 1 + \frac{R^2}{w^2 C^2} \right)} \quad \boxed{\pi/2 - \tan^{-1} R/wL \cdot w^2 L \sqrt{\pi/2}}$$

$$= wL \sqrt{\left( 1 + \frac{R^2}{w^2 C^2} \right) (wC)} \quad \boxed{\pi/2 - \tan^{-1}(R/wL) \times \sqrt{\pi/2}}$$

$$= w \sqrt{LC} \cdot \sqrt{\left( 1 + \frac{R^2}{w^2 L^2} \right)} \quad \boxed{( \pi/2 + \pi/2 ) - \tan^{-1} \left( R/wL + \frac{1}{wL} \right)}$$

$$= w \sqrt{LC} \sqrt{\left( 1 + \frac{R^2}{w^2 L^2} \right)} \quad \boxed{\pi - \tan^{-1} \left( R/wL \right)}$$

$$= w \sqrt{LC} \sqrt{\left( 1 + \frac{R^2}{w^2 L^2} \right)} \quad \boxed{(\pi - \tan^{-1} R/wL)^2}$$

$$= \left( \begin{array}{l} \\ \end{array} \right) \quad \boxed{(\pi/2 - 1/2 \tan^{-1} R/wL)}$$

## Types of Modern Transmission Lines

- \* Modern TL's can be sub-divided into,
  - 1) Microstrip lines.
  - 2) Strip lines
  - 3) Slot lines


### Sub divided into

- 1) Balanced - Electric field distribution is symmetrical
- 2) UnBalanced - Electric field distribution is not uniform.


## Planar Transmission Line

- \* A conducting metal strip that lie entirely in  $11^{\text{th}}$  planes.
- \* One or more  $11^{\text{th}}$  metal strips placed on a dielectric substrate, adjacent to a conducting ground plane.
- \* Widely used in Strip line.


## Types of planar transmission line

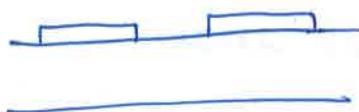


coupled strip  
line  
①

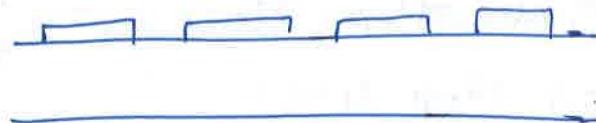

co-planar tr.-line  
⑤

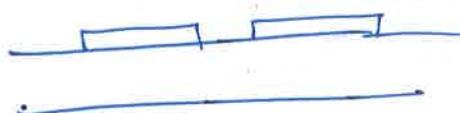


co-planar strip  
tr.-line ⑥

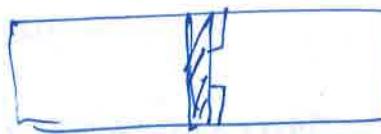

shield slot line  
⑦



slot line  
⑧

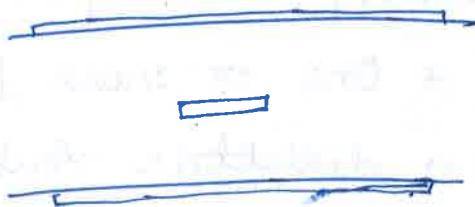

strip line  
⑨

① → used in directional couplers.

\* Used two modes of operation.


(i) even mode → Has the same voltage and at. on the two strips.

odd mode: Has opposite voltage and Date: currents on the two strips.

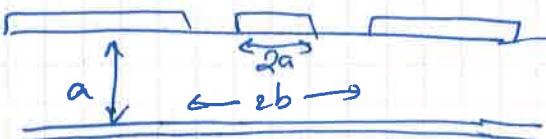(5) consists of single strip mounted b/w two ground planes on the same side of the dielectric substrate.

Adv. One metrip: shunt connection of components to the ground plane can be made on the same side of the substrate.

\* Also, allows series connection of component to be made with equal facility to that for microstrip lines.



\* ground plane & dielectric region exists.

\* On the dielectric region, along center

flat conductor, additionally there are two further metallic depositions separated from the center conductor by gaps.

The electric field pattern exists b/w the center conductor and the two co-planar gnd planes.

\*Used rarely.

- Q It is less desirable than co-planar lines.  
∴ it is not balanced w.r.t. to gnd plane